

TOPIC NAME : _____

DAY : _____

TIME : _____ DATE : / /

Mohsin Ibna Hassain
AIUB, IEC- Notes.

Introduction
To Electrical
Circuits

TOPIC NAME : _____

DAY : _____

TIME : _____

DATE : / /

Voltage, Current, Resistance
Ch: 2 and Ch: 3
Ohm's Law, power, Energy, Series Resistors
Ch: 4 and Ch: 5

Circuit:-

⇒ Circuit means a path way of electrical current due to applying a potential difference (or voltage) consisting of conductors or semi-conductors with suitable other components.

Current:-

⇒ Electrical current is defined as rate of charge or amount of charge per unit time.

$$\therefore \text{Current } I = \frac{\text{charge}}{\text{time}} = \frac{Q}{t}$$

Unit of current is Ampere (A)

Q:- 1A, what does it mean?

⇒ 1A means the capacity or rate of 1 Coulomb (1C) charge per unit second (s)

$$\therefore 1A = \frac{1C}{1\text{sec}} \text{ A or } C/\text{sec}$$

Note:-

⇒ Here, to carry the current means flow the charge or free electrons.

Order of Electron flow:-

1. Conductor $\rightarrow$ Cu $\rightarrow$ High tensile strength
2. Semi-Conductor $\rightarrow$ Si $\rightarrow$ Medium tensile strength
3. Insulator $\rightarrow$ Rubber $\rightarrow$ Low tensile strength

Voltage or potential Difference:-

⇒ It is defined as the work done to move 1 Coulomb (1C) charge from one point to another point with in the electric field.

1. Voltage or potential difference is always defined for one point with respect to another (or a reference point)

Reference point:-

⇒ As sum of all charges are zero at ground hence surface is always considered 0V and used as reference point.

TOPIC NAME : _____

DAY : _____

TIME : _____ DATE : / /

② For electrical charges:-

(i) Like charges will repel each other.

(ii) Opposite charges will attract each other.


Resistance:-

③ It is the ability to restrict the flow of current.


1. Due to free electrons, the electrical current is established in a circuit. These charges face restriction due to presence of other charges in the material.

Graph of Resistance vs Temperature:-

(i) For Conductors:-

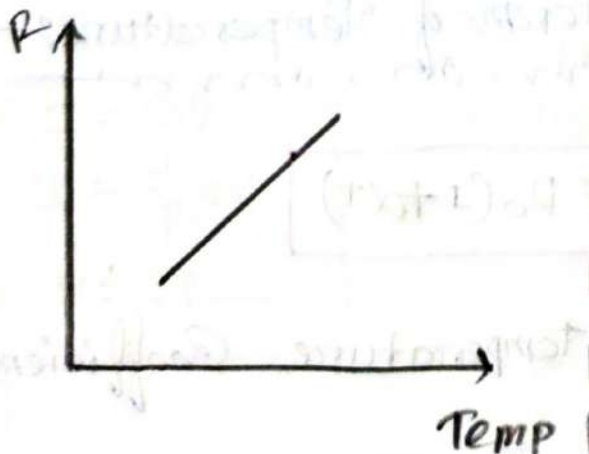

(ii) For Semiconductors:-

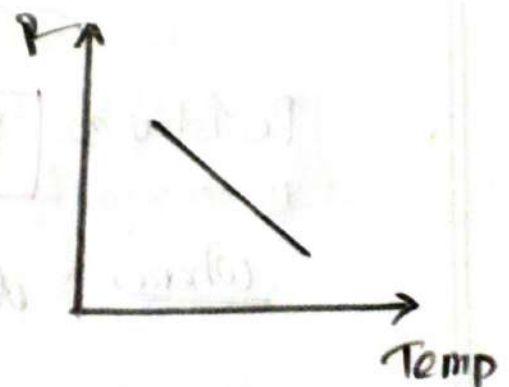

Order of Resistance:-

① For Conductors - Materials:-

⇒ Resistance is the lowest, (ρ is low), (G is high)

② For Insulators:-

⇒ Resistance is the Highest (ρ is high), (G is low)

Relationship between Resistance, Resistivity, Length & Area

$$\therefore \text{Resistance } R = \frac{\rho l}{A} \text{ } \Omega (\text{ohm})$$

Where, ρ = resistivity in $\Omega(\text{m})$

l = length of material (m)

A = Cross Section Area of material (m^2)

In terms of Temperature:-

$$\text{Resistance } R = R_0(1 + \alpha \Delta T)$$

Where, α = temperature coefficient

TOPIC NAME : _____

DAY : _____

TIME : _____

DATE : / /

Conductivity: — mon

⇒ It is the exact opposite of resistivity and conductance is the inverse of resistance, denote by G

$$G = \frac{1}{R} \text{ mho (ohm)} / \text{Siemens (S)}$$

① If there is more resistance —
mon

⇒ The conductance will be low and current will be low, or vice versa.

Ohm's Law: — mon

⇒ At a constant temperature current passing through a conductor is directly proportional to its potential difference between two points on it.

$$\therefore I \propto V$$

$$\Rightarrow I = GV$$

$$\Rightarrow I = \frac{1}{R} V$$

$$\Rightarrow V = IR$$

where,

G = Conductivity

R = Resistance

TOPIC NAME : _____

DAY : _____

TIME : _____ DATE : / /

Notes:

- ① Voltage and Current are active parameters.
- ② Resistance or Conductance is passive parameters.


Combination of Resistance:

⇒ Resistors can be combined as following

- ① Series Combination.
- ② Parallel Combination.

Source of Voltage, Current & Resistor


① Voltage Source (unit → Volt)

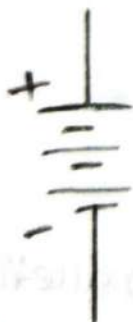

OR



Graph:

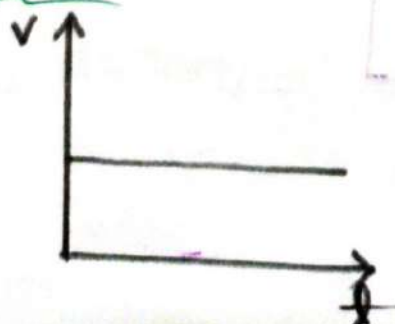


$$\begin{aligned} V_{OC} &= E \\ V_{R} &= E \\ E &= 10 \text{ V} \end{aligned}$$

TOPIC NAME : _____

DAY : _____

TIME : _____ DATE : / /


② Current Sources (Unit $\rightarrow$ A)

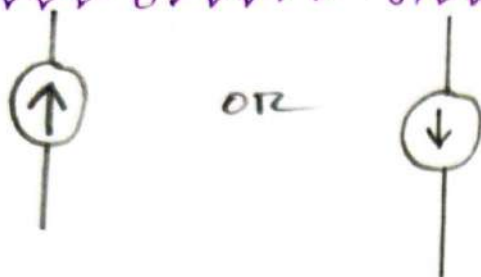

③ Resistor sources (Unit $\rightarrow \Omega$)




Ex

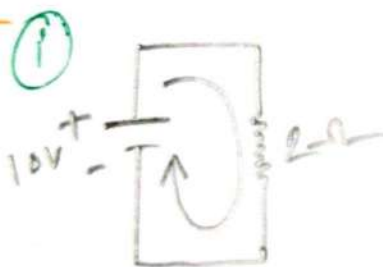


$$I = \frac{V}{R} = \frac{10}{2} = 5A$$

Ex II

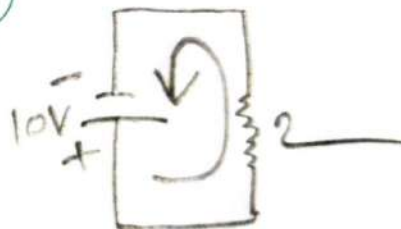

$$I = \frac{V}{R} = \frac{10}{2} = 5A$$

Series Combination:

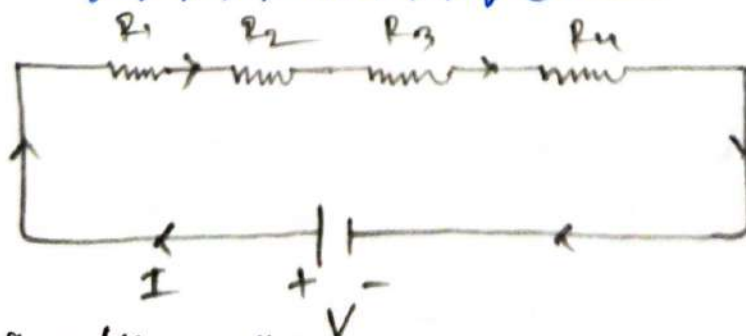


$\Rightarrow$ For Series: All resistors will carry the same current.
 $\therefore$ Total equivalent resistance

$$R_T = R_1 + R_2 + R_3 + R_4 + \dots$$

TOPIC NAME : _____

DAY : _____

TIME : _____ DATE : / /

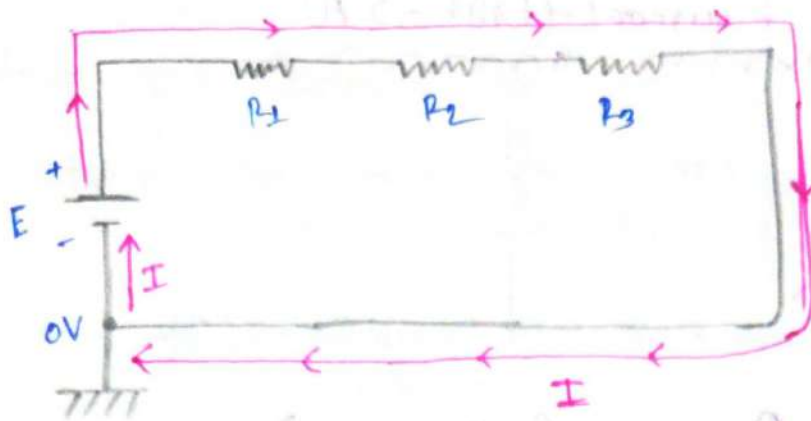

Here,

E = Battery or DC source voltage.



I = Source current in Amp

$\text{|||||} \propto \text{---}$ = Symbol for ground or Earthing represents '0'V.

How to Define Voltage:

- ① V_1 or V_a = Voltage with respect to ground (0V)
- ② V_{ab} = Voltage with respect to point 'b' of point 'a'
- ③ V_{12} = Voltage of point '1' with respect to point '2'

Ex:-

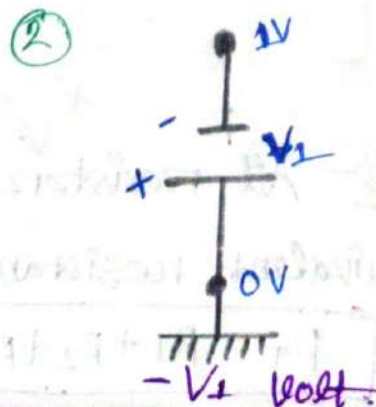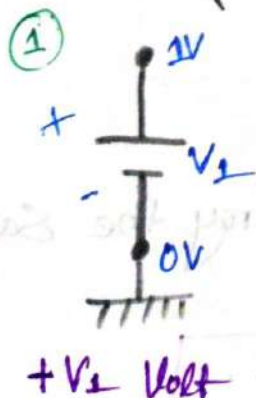


TOPIC NAME : _____

DAY : _____


TIME : _____

DATE : / /

Source of DC Current:-

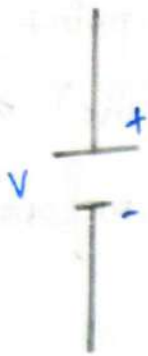

Symbol

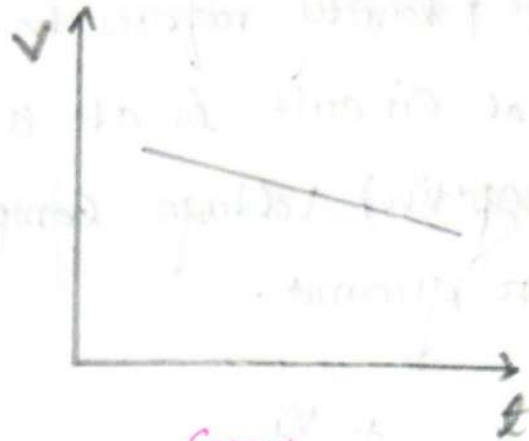

Graph

- ① One-Time batteries — Exs (AA, AAA, C type, D type, etc)
- ② Rechargeable batteries — Exs (Pb-acid, NiMH, Li-ion, etc)
- ③ DC generator (Rotary machine) — Exs (PV cells, fuel cell, etc)


Direction of electrical Current:-

⇒ Electrical Current Direction is always opposite to e^- flow direction

For Source/Battery:-

⇒ +ve terminal to -ve terminal.


Ex:-

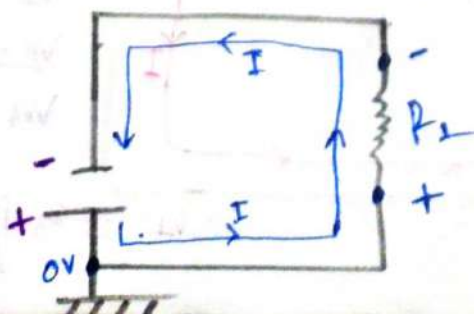


Voltage polarity:

⇒ Voltage polarity refers to whether a point in an electrical circuit is at a higher (positive) or lower (negative) voltage compared to a reference point or ground.


①

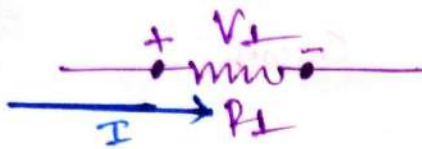


②

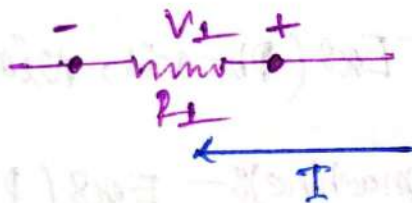

③

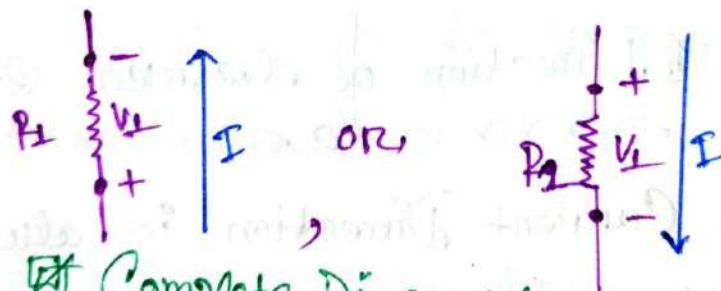

Complete Diagram:

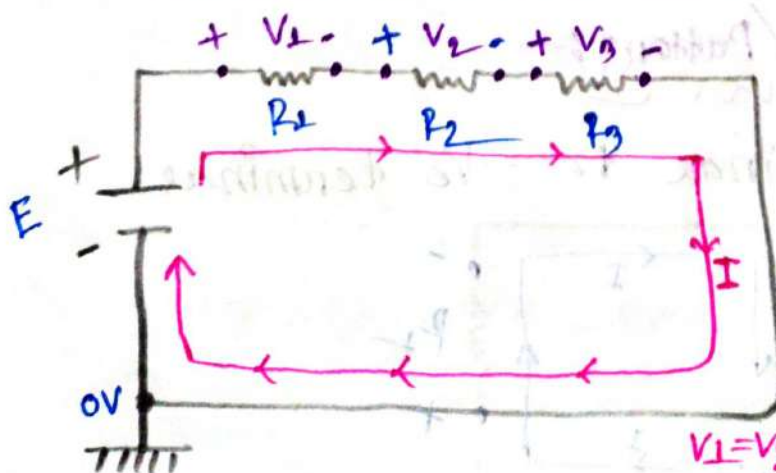

Where

$$V_1 = IR_1$$

$$V_2 = IR_2$$

$$V_3 = IR_3$$

$$V_1 = V_2 = V_3 \text{ if } R_1 = R_2 = R_3$$

#power! —

⇒ Rate of work done is defined as power, denote by P .
and unit W (watts).

$$\therefore P = \frac{W}{t} \text{ } \cancel{\text{m s}^{-1}}$$

Wort = Watt = 10^3

power with respect to electrical circuit:—

We know,
mom

$$V = \frac{W}{Q}$$

$$I = \frac{\Phi}{\theta}$$

$$I = \frac{V}{R} \text{ or } V = IR$$

$$\therefore P = \frac{\omega}{t} = \frac{qV}{t} = VI = I^2 R = \frac{V^2}{R}$$

Where,
mom

$\phi = \text{charge.}$

$V = \text{Voltage}$

$I = \text{Current}$

$R = \text{Resistance}$

TOPIC NAME : _____

DAY : _____

TIME : _____ DATE : / /

Power delivered by the Source!—

$$P = VI$$


Power consumed by a resistor/load!—

$$P = I^2 R = V^2 / R$$

Note:

Resistor convert consumed electrical energy to heat.

Problem: 5.1!—

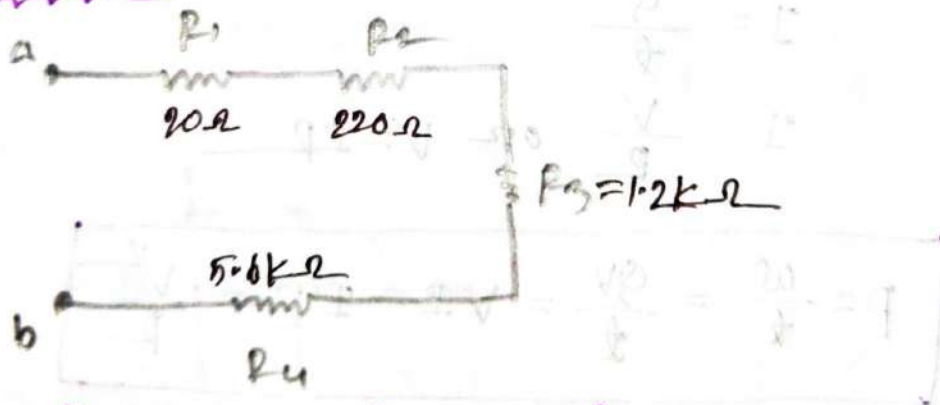

⇒ Determine the total resistance of the Series Connection in the Fig. Note that all the resistors appearing in this network are standard values.

TOPIC NAME : _____

DAY : _____

TIME : _____ DATE : / /

➔ In given:-
not

$$R_1 = 20\ \Omega$$

$$R_2 = 220\ \Omega$$

$$R_3 = 1200\ \Omega$$

$$R_4 = 5600\ \Omega$$

We know,
not

For Series Connections:-
not

$$R_T = R_1 + R_2 + R_3 + R_4$$


$$= (20 + 220 + 1200 + 5600)\ \Omega$$

$$= 7040\ \Omega$$

$$= 7.04\ k\Omega$$

Ans:-

Problem No. 5.7
not

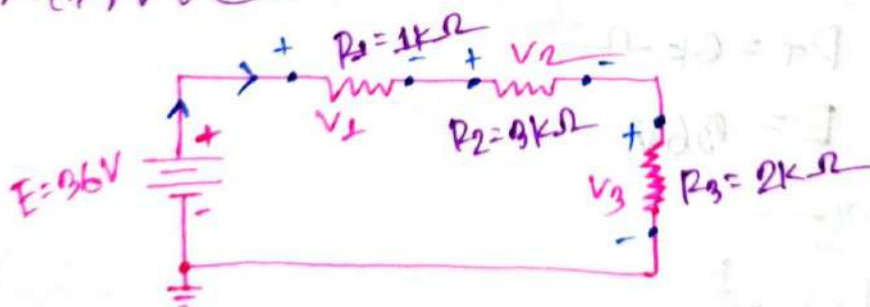

- ① Determine the total Resistance R_T .
- ② Calculate the Current I_s .
- ③ Determine the Voltage across each resistor.
- ④ Find the power - Supplied by the battery.
- ⑤ Determine the power dissipated by each resistor.
- ⑥ Prove that the total power supplied equals the total power dissipated.

(1)

In given:-
nom

$$R_1 = 1000 \Omega = 1k\Omega$$

$$R_2 = 3000 \Omega = 3k\Omega$$

$$R_3 = 2000 \Omega = 2k\Omega$$

We know:-
nomFor Series Connection:-
nom nom nom

$$R_T = R_1 + R_2 + R_3$$

$$= (1000 + 3000 + 2000) \Omega$$

$$= 6000 \Omega$$

$$= 6k\Omega$$

(2)

We have:-
nom

$$R_T = 6k\Omega$$

$$E = 36V$$

We know:-
nom

$$I_s = \frac{E}{R_T}$$

$$= \frac{36}{6 \times 10^3} A$$

$$= 6 \times 10^{-3} A$$

$$= 6mA$$

(3)

We have:-
now

$$I_s = 6 \times 10^{-3} \text{ A}$$

$$R_1 = 1 \text{ k}\Omega$$

$$R_2 = 3 \text{ k}\Omega$$

$$R_3 = 2 \text{ k}\Omega$$

We know:-
now

$$V = IR$$

$$\therefore V_1 = I_s R_1 = 6 \times 10^{-3} \times 1 \times 10^3$$
$$= 6 \text{ Volt}$$

$$V_2 = I_s R_2 = 6 \times 10^{-3} \times 3 \times 10^3$$
$$= 18 \text{ Volt}$$

$$V_3 = I_s R_3 = 6 \times 10^{-3} \times 2 \times 10^3$$
$$= 12 \text{ Volt}$$

Ans:-

(4)

We have:-
now

$$E = 36 \text{ V}$$

$$I_s = 6 \times 10^{-3} \text{ A}$$

We know:-
now

power supplied by the battery

$$P = EI$$

$$= 36 \times 6 \times 10^{-3}$$

$$= 0.216 \text{ W}$$

$$= 216 \text{ mW}$$

Ans:-

(5)

We have:—

$$E = 36V$$

$$R_1 = 1k\Omega$$

$$R_2 = 3k\Omega$$

$$R_3 = 2k\Omega$$

$$I_S = 6 \times 10^{-3} A$$

We know:—

power dissipated by resistor:—

$$P = \frac{V_R^2}{R_R} = I_S^2 R_R = V_R I_S$$

$$\therefore P_1 = I_S^2 R_1 = (6 \times 10^{-3})^2 \times 1000 = 0.036 W = 36 mW$$

Now,

$$\begin{aligned} V_2 &= I_S R_2 \\ &= 0.006 \times 3000 \\ &= 18 \text{ Volt} \end{aligned}$$

$$\therefore P_2 = \frac{V_2^2}{R_2} = \frac{(18)^2}{3000} = 0.108 W = 108 mW$$

Again:—

$$\begin{aligned} V_3 &= I_S R_3 \\ &= 6 \times 10^{-3} \times 2000 \\ &= 12 \text{ Volt} \end{aligned}$$

$$\therefore P_3 = V_3 I_S = 12 \times 6 \times 10^{-3} = 0.072 W = 72 mW$$

Ans:—

(6)

we found:-Power supplied by the battery = 216 mW

Power dissipated by the resistors :-

$$P_1 = 96 \text{ mW}$$

$$P_2 = 108 \text{ mW}$$

$$P_3 = 72 \text{ mW}$$

$$\therefore P_E = P_1 + P_2 + P_3$$

$$216 = 96 + 108 + 72$$

$$216 = 216$$

$$\text{L.H.S} = \text{R.H.S}$$

So, (Proved)Ans:-# Problem 4.1:- $\Rightarrow$ Determine the current resulting from the application of a 9 V battery ~~and~~ with a resistance of 2.2Ω $\Rightarrow$ Is given:-

$$V = 9 \text{ V}$$

$$R = 2.2 \Omega$$

we know:-

$$I = \frac{V}{R} = \frac{9}{2.2} = 4.09 \text{ A}$$

Ans:-

Problem 4.2: —
mon

⇒ Calculate the resistance of a 60W bulb if a current of 500mA result from an applied voltage of 120V

⇒ Is given: —
mon

$$P = 60W$$

$$I = 500mA = 500 \times 10^{-3}A$$

$$V = 120V$$

we know: —
mon

$$P = I^2 R$$

$$\therefore R = \frac{P}{I^2}$$

$$= \frac{60}{(500 \times 10^{-3})^2}$$

$$= 240 \Omega$$

Ans —


Problem 4.6: —
mon

(i)

⇒ Find the power delivered by the source.

(ii)

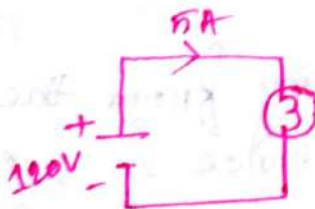⇒ What is the power dissipated by a 5Ω resistor if the current is 4A?



(i)

Is given:-

$$V = 120V$$

$$I = 5A$$

We know:-

power delivered by the Source:-

$$P = VI$$

$$= 120 \times 5$$

$$= 600W$$

Ans:-

(ii)

Is given:-

$$R = 5\Omega$$

$$I_s = 4A$$

We know:-

Power dissipated by the resistor:-

$$P = I^2 R$$

$$= (4)^2 \times 5$$

$$= 80W$$

Ans:-

problem 20: —
non

⇒ If 420 J of energy are absorbed by a resistor in 4 min. What is the power of resistor?

⇒ Is given: —
non

$$W = 420 \text{ J}$$

$$t = 4 \text{ min}$$

$$= 4 \times 60 \text{ sec}$$

$$= 240 \text{ sec}$$

$$= 240 \text{ sec}$$

We know: —
non

$$P = \frac{W}{t}$$



$$= \frac{420}{240} \text{ (ii)}$$

$$= 1.75 \text{ W}$$

Ans: —

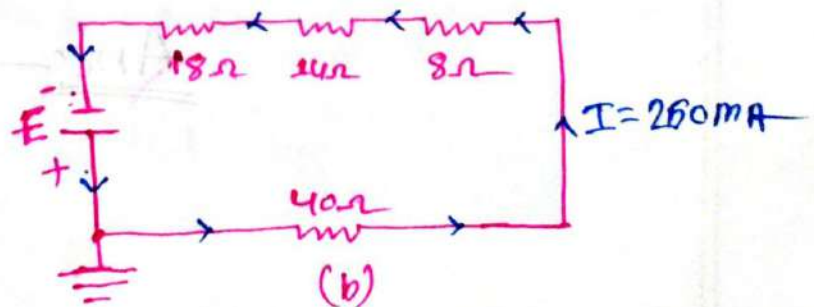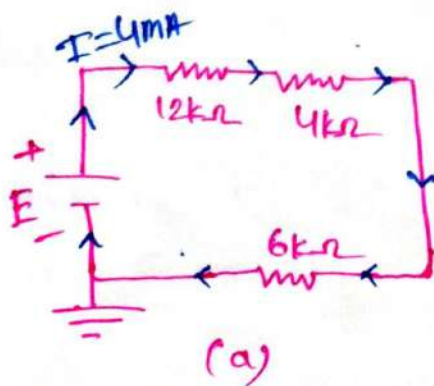problem 9: —
non

⇒ Find the applied voltage necessary to develop the current specified in each circuit



(a)

In given:-
normLet:-

$$R_1 = 12k\Omega$$

$$R_2 = 4k\Omega$$

$$R_3 = 6k\Omega$$

$$I_s = 4mA = 4.0 \times 10^{-3}A$$

We know:-
norm

$$R_s = R_1 + R_2 + R_3$$

$$= (12 + 4 + 6)k\Omega$$

$$= 22k\Omega$$

$$E = V = I_s R_s$$

$$= (4.0 \times 10^{-3}) \times 22k\Omega$$

$$= 4 \times 10^{-3} \times 22 \times 10^3$$

$$= 88 \text{ Volt}$$

Ans:-

(b)

In given:-
normLet:-

$$R_1 = 18\Omega$$

$$R_2 = 14\Omega$$

$$R_3 = 8\Omega$$

$$R_4 = 40\Omega$$

$$I_s = 250mA = 250 \times 10^{-3}A$$

TOPIC NAME : _____

DAY : _____

TIME : _____ DATE : / /

We know:-

$$R_s = R_1 + R_2 + R_3 + R_4$$

$$= 18 + 14 + 8 + 40$$

$$= 80 \Omega$$

$$E = V = I_s R_s$$

$$= 80 \times 250 \times 10^{-3}$$

$$= 20 \text{ Volt}$$


Ans:-

problem!

⇒ A 10V DC source is connected in series with ten $2M\Omega$ resistor, Find

- (i) Total resistance
- (ii) Current
- (iii) Voltage for each resistance.

⇒

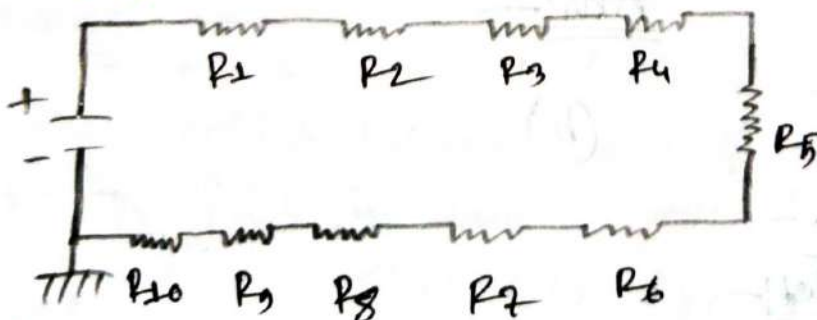

It is given:-

$$R_1 = R_2 = R_3 = R_4 = R_5 = R_6 = R_7 = R_8 = R_9 = R_{10} = 2M\Omega$$

We know:-

$$R_T = R_1 + R_2 + R_3 + R_4 + R_5 + R_6 + R_7 + R_8 + R_9 + R_{10}$$

$$= 2 \times 10 = 20M\Omega$$

TOPIC NAME : _____

DAY : _____

TIME : _____

DATE : / /

(ii)

We have:-

$$R_T = 20 \text{ M}\Omega$$

$$E = 0 \text{ V}$$

We know:-

$$E = IR_T$$

$$I = \frac{E}{R_T}$$

$$= \frac{0}{20 \text{ M}}$$

$$= \frac{0}{20 \times 10^6}$$

$$= 4.5 \times 10^{-7} \text{ A}$$

(iii)

We have:-

$$R_T = 20 \text{ M}\Omega$$

$$E = 0 \text{ V}$$

$$I = 4.5 \times 10^{-7} \text{ A}$$

Since, All resistors are same value.

So, Voltage for each resistor are same.

\therefore we know:-

$$V_L = IR_L$$

$$= 4.5 \times 10^{-7} \times 20 \times 10^6$$

$$= 0.9 \text{ Volt}$$

\therefore Voltage for each resistor = 0.9 Volt.


Ans:-

Kirchhoff's Voltage Law (KVL)

⇒ In an enclosed circuit, sum of all voltages are zero. or Sum of Voltage rise equals Sum of Voltage drop.

① For KVL, calculation should start from ground to source, to each resistor and other components and back to ground.

Ex:-

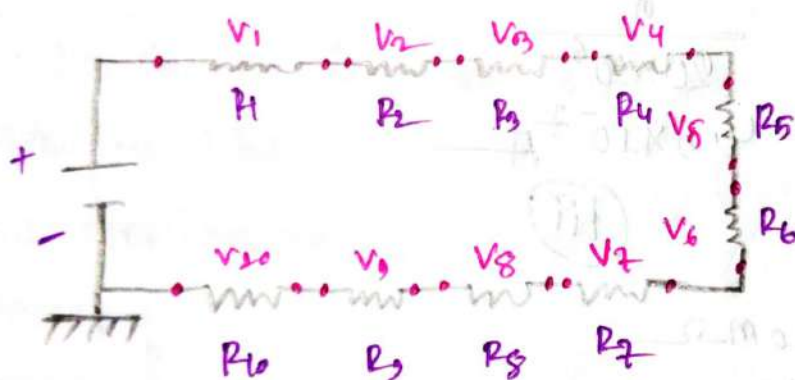

✱ Assuming clock-wise Approach: (ACWA)!

① 'e-' to 'e+' → Indicates Voltage rise

② 'e+' to 'e-' → Indicates Voltage Drop

✱ Assuming Anti-clock-wise Approach: (AACWA)!

① 'e-' to 'e+' → Indicates Voltage Drop

② 'e+' to 'e-' → Indicates Voltage rise.

TOPIC NAME : _____

DAY : _____

TIME : _____ DATE : / /

Note:-

⇒ The voltage of the battery/source will always rise.

From the KVL Law:-


$$\therefore E + V_1 + V_2 + V_3 + V_4 + V_5 + V_6 + V_7 + V_8 + V_9 + V_{10} = 0$$

$$E = -(V_1 + V_2 + V_3 + V_4 + V_5 + V_6 + V_7 + V_8 + V_9 + V_{10}) \quad \left[\text{'-' sign indicate Voltage drop} \right]$$

From the Last Law of KVL:-

$$E = V_1 + V_2 + V_3 + V_4 + V_5 + V_6 + V_7 + V_8 + V_9 + V_{10}$$

Problem:- 5.11:-

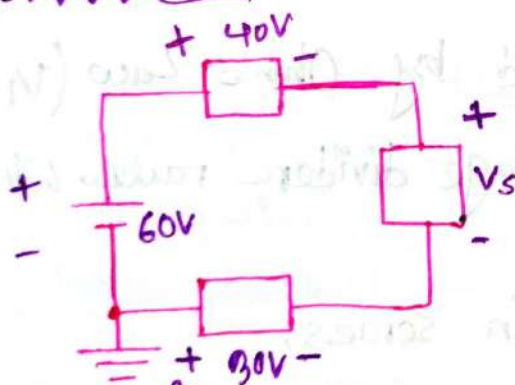

⇒ Using Kirchhoff's Voltage law, determine the unknown voltage for the circuit.

is given:-

$$E = 60V$$

$$V_1 = 40V$$

$$V_s = ?$$

$$V_2 = 30V$$

we know:-

$$\Rightarrow E - V_1 - V_s + V_2 = 0 \quad [\text{from KVL Law}]$$

$$\Rightarrow V_s = E - V_1 + V_2$$

$$= 60 - 40 + 30$$

$$= 50V$$

$$\therefore V_s = 50V$$

Ans:-

Voltage Divider rule (VDR)

$\Rightarrow$ For a series circuit, the current remains same through all components but the voltage of each component can be found by Ohm's Law ($V_1 = IR_1$, $V_2 = IR_2$ etc)

$\Rightarrow$ Another option is Voltage divider rule, which is the follows:-

- For n^{th} resistor in series,
Voltage for n^{th} resistor

$$V_n = \frac{R_n}{R_T} \times E$$

R_T = Equivalent total resistance for series circuit.


TOPIC NAME : _____

DAY : _____

TIME : _____

DATE : / /

#problem—
nom

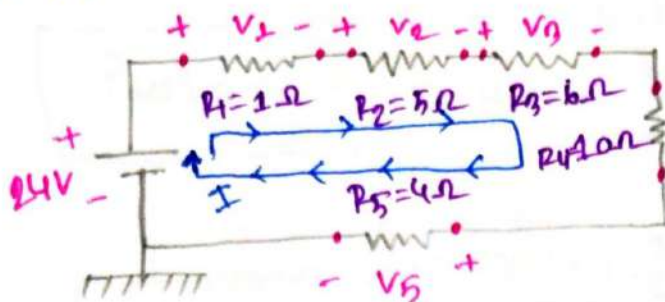

① Find the voltage Drops for 6-Ω and 4-Ω Resistor

② Find the total Current

③ Find the rest of the Voltage drop and verify KVL

Is given—
nom

①

$$R_1 = 1\Omega, R_2 = 5\Omega, R_3 = 6\Omega$$

$$R_4 = 10\Omega, R_5 = 4\Omega, E = 24V$$

we know—
nom

$$R_T = R_1 + R_2 + R_3 + R_4 + R_5$$

$$= 1 + 5 + 6 + 10 + 4$$

$$= 26\Omega$$

Voltage Drops for 6-Ω:—
nom

$$V_3 = \frac{R_3}{R_T} \times E$$

$$V_3 = \frac{6}{26} \times 24$$

$$= 5.538 \text{ Volt}$$

Voltage Drops for 4-Ω:—
nom

$$V_5 = \frac{R_5}{R_T} \times E$$

$$= \frac{4}{26} \times 24 = 3.692 \text{ Volt}$$

(Ans)

(2)

we have:-
non

$$E = 24 \text{ V}$$

$$R_T = 26 \Omega$$

we know:-
non

$$E = V = IR$$

$$\therefore I_s = \frac{E}{R_T}$$

$$= \frac{24}{26}$$

$$= 0.923 \text{ A}$$

Ans:-

(3)

we have:-
non

$$V_3 = 5.538 \text{ Volt}$$

$$V_5 = 3.692 \text{ Volt}$$

we know:-
non

$$V_n = IR_n$$

$$\therefore V_1 = I_s R_1 = (0.923) \times 1 = 0.923 \text{ Volt}$$

$$\therefore V_2 = I_s R_2 = (0.923) \times 5 = 4.615 \text{ Volt}$$

$$\therefore V_4 = I_s R_4 = (0.923) \times 10 = 9.23 \text{ Volt}$$

From KVL:-
non

$$E = V_1 + V_2 + V_3 + V_4 + V_5$$


$$24 \text{ V} = (0.923 + 4.615 + 5.538 + 9.23 + 3.692) \text{ V}$$

$$24 \text{ V} = 24 \text{ V (verified)}$$

Ans:-

Tellegen's Law (for power):

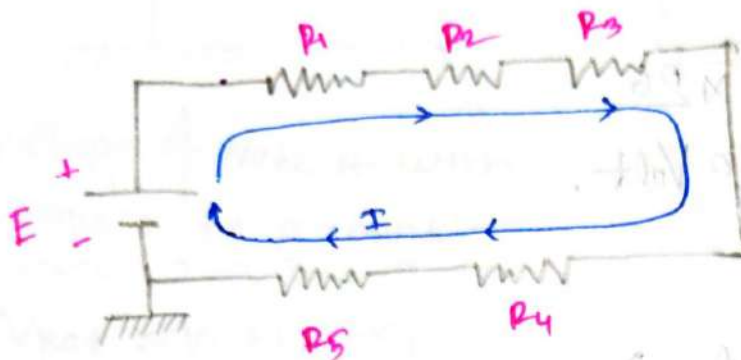
$$P_{\text{delivered}} = P_{\text{consumed}}$$



$\therefore P = EI$ = power delivered by the source

$$P = I^2 R_1 + I^2 R_2 + I^2 R_3 + I^2 R_4 + I^2 R_5 \rightarrow \text{power consumed}$$

Problem:

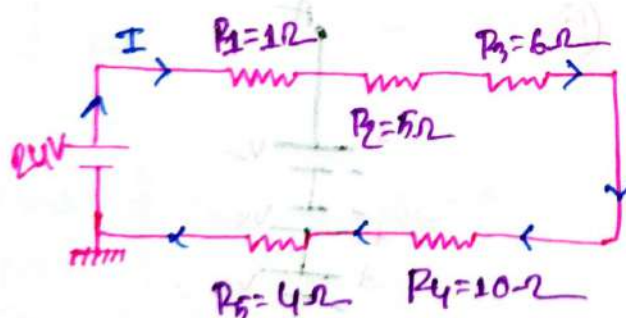

① Verify the Tellegen's Law?

→ We know,

$$R_T = R_1 + R_2 + R_3 + R_4 + R_5 \\ = 1 + 5 + 6 + 10 + 4 \\ = 26 \Omega$$

$$I_s = \frac{E}{R_T} = \frac{24}{26} = 0.923 \text{ A}$$

$\therefore$ Power delivered

$$P = EI = 24 \times 0.923 = 22.152 \text{ W}$$

Power Consumed:-

$$\begin{aligned}
 P_c &= I^2 R_1 + I^2 R_2 + I^2 R_3 + I^2 R_4 + I^2 R_5 \\
 &= I^2 (R_1 + R_2 + R_3 + R_4 + R_5) \\
 &= I^2 R_T \\
 &= (0.223)^2 \times 26 \\
 &= 22.150 \text{ Volt.}
 \end{aligned}$$

$$P_d = P_c$$

(verified)

Voltage Source in Series:-


①



$$\therefore V_{net} = V_3 + V_2 + V_1$$

Voltage of node A
with respect to ground

②

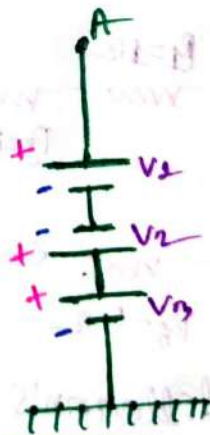


$$V_{net} = V_3 - V_2 + V_1$$

TOPIC NAME : _____


DAY : _____

TIME : _____ DATE : / /

Ex-
①

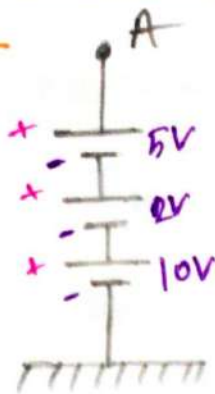



Dominating battery/Source

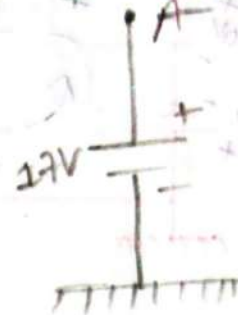

∴ Voltage of Node A with respect to ground:—

$$\begin{aligned} V_{\text{net}} &= V_1 + V_2 + V_3 \\ &= 10 + 5 + 2 \\ &= 17V \end{aligned}$$


②

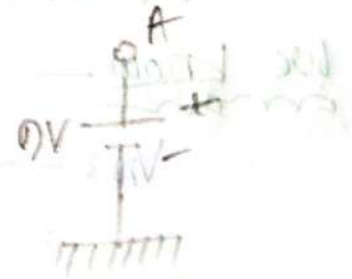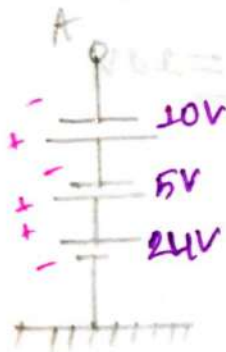

∴ Voltage of Node A with respect to ground:—

$$\begin{aligned} V_{\text{net}} &= (24 - 5 - 10)V \\ &= 9V \end{aligned}$$

problems

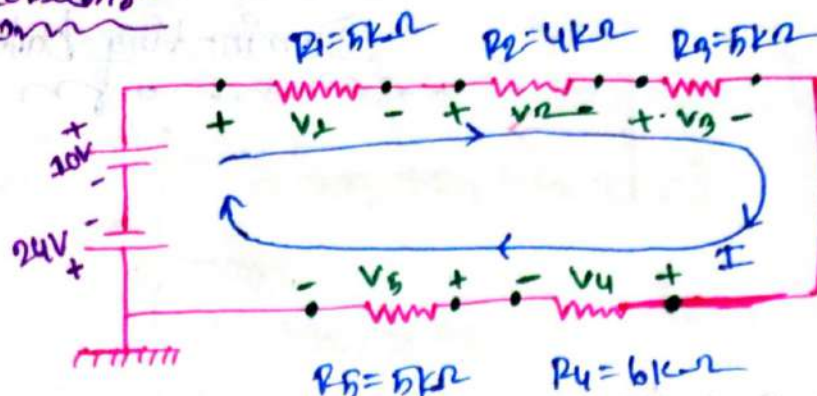

① Find the total current

② Voltage drops for R_3 & R_4 using VDR

⇒ In given: ①

$$R_1 = 5k\Omega, R_2 = 4k\Omega, R_3 = 5k\Omega$$

$$R_4 = 5k\Omega, R_5 = 6k\Omega, E_1 = 24V, E_2 = 10V$$

We know—


$$V_{net} = -24 + 10$$

$$= -14V$$

$$R_T = R_1 + R_2 + R_3 + R_4 + R_5$$

$$= 5 + 4 + 5 + 5 + 6$$

$$= 25k\Omega$$

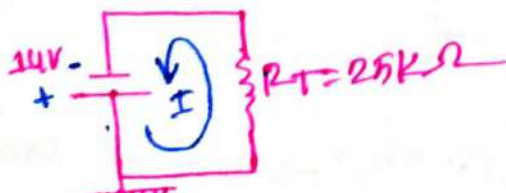Re Draw the circuit

$$\therefore I = \frac{|V_{net}|}{R_T} = \frac{14}{25 \times 10^3} = 5.6 \times 10^{-4} A$$

Ans—

(11)

We know

$$I_n = \frac{|V_{net}|}{R_T} = \frac{14}{25 \times 10^3} = 5.6 \times 10^{-4} \text{ A}$$

$$V_n = \frac{R_n}{R_T} \times E$$

$$\therefore V_3 = \frac{R_3}{R_T} \times |E|$$

$$= \frac{5 \text{ k}\Omega}{25 \text{ k}\Omega} \times 14 \text{ V}$$

$$= 2.8 \text{ V}$$

$$V_4 = \frac{R_4}{R_T} \times |E|$$


$$= \frac{6 \text{ k}\Omega}{25 \text{ k}\Omega} \times 14$$

$$= 3.36 \text{ V}$$

Note

⇒ If Direction of Current is opposite to the battery/Source Voltage polarity it will be -ve otherwise +ve.

problem:-

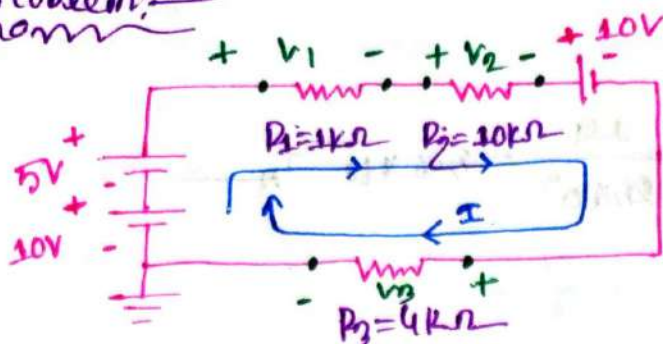

① Find the total current

ii) Find the each of voltage drops and verify the KVL

⇒ Is given:-

$$\begin{array}{l} V_1 = 10V \\ V_2 = 5V \\ V_3 = 10V \end{array} \quad \left\{ \begin{array}{l} R_1 = 1k\Omega \\ R_2 = 10k\Omega \\ R_3 = 4k\Omega \end{array} \right.$$

①

we know:-

$$E_{net} = V_1 + V_2 - V_3$$

$$= 10 + 5 - 10$$

$$= 5V$$

$$R_T = R_1 + R_2 + R_3$$

$$= (1 + 10 + 4)k\Omega$$

$$= 15k\Omega$$

$$I_s = \frac{E_{net}}{R_T} = \frac{5V}{15 \times 10^3 \Omega}$$

$$= 3.33 \times 10^{-4} A$$

Ans:-

(11)

we know,
now

$$V_n = IR_n$$

$$\begin{aligned} \therefore V_1 &= IR_1 \\ &= 1 \times 10^{-3} \times 3.33 \times 10^{-4} \\ &= 0.333 \text{ Volt} \end{aligned}$$

$$\begin{aligned} V_2 &= IR_2 \\ &= 3.33 \times 10^{-4} \times 10 \times 10^3 \\ &= 3.33 \text{ Volt} \end{aligned}$$

$$\begin{aligned} V_3 &= IR_3 \\ &= 3.33 \times 10^{-4} \times 4 \times 10^3 \\ &= 1.332 \end{aligned}$$

from KVL:-
now

$$E = V_1 + V_2 + V_3$$

$$5 = 1.332 + 3.33 + 0.333$$

$$5V = 5V \text{ (verified)}$$

Ans:-

problem 2.1:—

⇒ Find the voltage between 2 points if 60 J of energy are required to move a charge of 20 C between two points.

⇒ Is given!—

$$W = 60 \text{ J}$$

$$Q = 20 \text{ C}$$

we know, —

$$V = \frac{W}{Q}$$

$$= \frac{60}{20}$$

$$= 3 \text{ Volt.}$$

Ans:-

problem 2.2:—

⇒ Determine the Energy expended moving a charge of $20 \mu\text{C}$ between 2 points if the voltage is 6V.

⇒ Is given:—

$$Q = 20 \times 10^{-6} \text{ C}$$

$$V = 6 \text{ V}$$

we know, —

$$V = \frac{W}{Q}$$

$$\therefore W = VQ = 6 \times 20 \times 10^{-6} = 120 \times 10^{-6} \text{ J}$$

$$= 120 \mu\text{J}$$

TOPIC NAME : _____

DAY : _____

TIME : _____

DATE : / /

Problem : 2.3.1 :-

⇒ Find the charge that requires 120 J of energy to be moved through a potential difference of 20 V.

⇒ Is given :-

$$W = 120 \text{ J}$$

$$V = 20 \text{ V}$$

we know :-

$$V = \frac{W}{Q}$$

$$\therefore Q = \frac{W}{V} = \frac{120}{20} = 6 \text{ C}$$

Ans:-

Problem : 2.3 :-

⇒ The charge flowing through the imaginary surface is 0.16 C every 64 μs. Determine current in Amperes.

⇒ Is given :-

$$Q = 0.16 \text{ C}$$

$$t = 64 \times 10^{-6} \text{ s}$$

we know :-

$$I = \frac{Q}{t}$$

$$= \frac{0.16}{64 \times 10^{-6}}$$

$$= 2.5 \text{ A}$$

Ans:-

TOPIC NAME : _____

DAY : _____

TIME : _____ DATE : / /

Example 8.4 —

⇒ Determine how long it will take $4 \times 10^{16} e^-$ to pass through the imaginary surface if the current is 5 mA .

Is given —

$$e^- = 4 \times 10^{16}$$

$$I = 5 \text{ mA} = 5 \times 10^{-3} \text{ A}$$

we know —

$$1e = \frac{1}{1.602 \times 10^{19}} = 6.24 \times 10^{18} e^-$$

$$\therefore 6.24 \times 10^{18} e^- = 1e$$

$$\begin{aligned} \text{So, } 4 \times 10^{16} e^- &= \frac{1 \times 4 \times 10^{16}}{6.24 \times 10^{18}} e \\ &= 6.41 \times 10^{-3} e \end{aligned}$$

Again —

$$I = \frac{Q}{t}$$

$$\therefore t = \frac{Q}{I} = \frac{6.41 \times 10^{-3}}{5 \times 10^{-3}}$$

$$= 1.282 \text{ Sec}$$

Ans —

TOPIC NAME : _____

DAY : _____

TIME : _____ DATE : / /

Problem 2.4.1: —
non

⇒ If a current of 100 mA exists for 1.5 min. How many

(i) Coulomb of charge, and

(ii) Electrons have passed through the wire?

⇒ Is given: —
non

$$I = 100 \text{ mA} = 100 \times 10^{-3} \text{ A}$$

$$t = 1.5 \text{ Sec} = 90 \text{ Sec}$$

We know: —
non

$$I = \frac{Q}{t}$$

$$Q = It = 100 \times 10^{-3} \times 90$$

$$= 9 \text{ C}$$

Again: —
non

$$1 \text{ C} = 6.24 \times 10^{18} e^{-}$$

$$\therefore 9 \text{ C} = 9 \times 6.24 \times 10^{18}$$

$$= 56.16 \times 10^{18} e^{-}$$

Ans: —

Problem 2.4.2: —
non

⇒ If a conductor with a current of 120 mA passing through it converts 20 J of electrical energy into heat in 20 s. What is the drop of potential across the conductor?

⇒ Is given:-

$$I = 120 \text{ mA} = 120 \times 10^{-3} \text{ A}$$

$$W = 20 \text{ J}$$

$$t = 20 \text{ Sec}$$

We know:-

$$I = \frac{Q}{t}$$

$$\therefore Q = It$$

$$= 120 \times 10^{-3} \times 20$$

$$= 2.4 \text{ C}$$

Again:-

$$V = \frac{W}{Q}$$

$$= \frac{20}{2.4}$$

$$= 8.33 \text{ Volt}$$

Ans:-

Problem: 2.4.3:-

⇒ charge is flowing through a Conductor at the rate of 200 C/min. If 750 J of electrical Energy are converted to heat in 45 s, what is the potential difference across the Conductor?

⇒ Is given:-

$$I = 200 \text{ C/min} = (200/60) \text{ C/s or A}$$

$$= 3.33 \text{ C/s or A}$$

TOPIC NAME : _____

DAY : _____

TIME : _____ DATE : / /

$$W = 7500$$

$$t = 45 \text{ sec}$$

we know

$$I = \frac{Q}{t}$$

$$\therefore Q = It = 9.33 \times 45 = 149.85 \text{ C}$$

Again

$$V = \frac{W}{Q}$$

$$V = \frac{7500}{149.85} = 50.05 \text{ V}$$

Ans:-

Problem: 2.4.4:-

⇒ The potential difference between two points in an electric circuit is 48V. if 1.2J of energy were dissipated in a period of 1ms. what would be the current?

Is given:-

$$V = 48 \text{ Volt}$$

$$W = 1.2 \text{ J}$$

$$t = 1 \text{ ms} = 1 \times 10^{-3} \text{ Sec}$$

we know

$$V = \frac{W}{Q}$$

$$\therefore Q = \frac{W}{V} = \frac{1.2}{48} = 0.025 \text{ C}$$

Again

$$I = \frac{Q}{t}$$

$$= \frac{0.025}{1 \times 10^{-3}} = 1.667 \text{ A}$$

Ans:-

TOPIC NAME : _____

DAY : _____

TIME : _____ DATE : / /

Problem: 9.7:-

⇒ Determine the resistance of 100 ft Copper telephone wire if the diameter is 0.0126 in. where $\rho = 1.723 \times 10^{-6} \Omega\text{-cm}$

Is given:-

$$l = 100 \text{ ft} = 100 \times 0.3048 = 30.48 \text{ m}$$

$$d = 0.0126 \text{ in} = 0.0126 \times 0.0254 = 3.2004 \times 10^{-4} \text{ m}$$

$$\rho = 1.723 \times 10^{-6} \Omega\text{-cm} = 1.723 \times 10^{-6} \times 10^{-2} = 1.723 \times 10^{-8} \Omega\text{-m}$$

We know:-

$$\text{Area of circle } A = \pi r^2 \quad \left\{ \begin{array}{l} r = \frac{d}{2} \\ = \pi \left(\frac{d}{2} \right)^2 \end{array} \right.$$

$$= \pi \left(\frac{3.2 \times 10^{-4}}{2} \right)^2$$

$$= 8.04 \times 10^{-8} \text{ m}^2$$

Again:-

$$R = \rho \times \frac{l}{A}$$

$$= 1.723 \times 10^{-8} \times \frac{30.48}{8.04 \times 10^{-8}}$$

$$= 6.532 \Omega$$

Ans:-

TOPIC NAME : _____

DAY : _____

TIME : _____

DATE : / /

problem: 3.2.11

⇒ Determine the value of resistance of an aluminum conductor if the area is increased by a factor of 3. The original resistance was $12\ \Omega$.

⇒ In given:-

$$R_i = 12\ \Omega$$

Let:-

$$\rho_i = \rho_f = \rho$$

$$\text{Area } A_i = A$$

$$A_f = 3A$$

$$\text{Length } l_i = l_f = l$$

We know:-

$$R = \rho \frac{l}{A}$$

$$\therefore \frac{R_1}{R_2} = \frac{l_i \rho_i / A_i}{l_f \rho_f / A_f}$$

$$= \frac{l \rho / A}{l \rho / 3A}$$

$$= \frac{l \rho}{A} \times \frac{3A}{l \rho}$$

$$= 3$$

$$\therefore R_f = \frac{1}{3} \times R_i$$

$$= \frac{1}{3} \times 12$$

$$= 4\ \Omega$$

Ans:-

problem 8.2.21

⇒ Determine the value of resistance of a silver Conductor if the length is doubled, the Original resistance was 5Ω .

⇒ In given:-

$$R_i = 5\Omega$$

Let:-

$$\rho_i = \rho_f = \rho$$

$$A_i = A_f = A$$

$$l_i = l$$

$$l_f = 2l$$

we know:-

$$R = \rho \frac{l}{A}$$

$$\therefore \frac{R_f}{R_i} = \frac{\rho A_f / A_f}{\rho l_i / A_i}$$

$$= \frac{\rho l_f}{A_f} \times \frac{A_i}{\rho l_i}$$

$$= \frac{\rho 2l}{A} \times \frac{A}{\rho l}$$

$$R_f = 2 \times R_i$$

$$= 2 \times 5$$

$$= 10\Omega$$

Ans:-

TOPIC NAME : _____

DAY : _____

TIME : _____ DATE : / /

#problem: 9.9:-

⇒ If the resistance of a copper wire is 50Ω at 50°C what is the resistance at 100°C where $T_c = 234.5^\circ\text{C}$

⇒ In given:-

$$\begin{aligned} R_1 &= 50\Omega \\ R_2 &=? \end{aligned} \quad \left\{ \begin{aligned} T_1 &= 50^\circ\text{C} \\ T_2 &= 100^\circ\text{C} \\ T_c &= 234.5^\circ\text{C} \end{aligned} \right.$$

we know:-

$$\frac{T_c + T_1}{R_1} = \frac{T_c + T_2}{R_2}$$

$$\begin{aligned} \therefore R_2 &= \frac{R_1(T_c + T_2)}{T_c + T_1} \\ &= \frac{50(234.5 + 100)}{(234.5 + 50)} \\ &= 58.78\Omega \end{aligned}$$

#problem: 9.10:-

⇒ If the resistance of a copper wire at freezing (0°C) is 30Ω what is the resistance at -40°C ? $T_c = 234.5^\circ\text{C}$

⇒ In given:-

$$\begin{aligned} R_1 &= 30\Omega \\ R_2 &=? \end{aligned} \quad \left\{ \begin{aligned} T_1 &= 0^\circ\text{C} \\ T_2 &= -40^\circ\text{C} \\ T_c &= 234.5^\circ\text{C} \end{aligned} \right.$$

we know:-

$$\frac{T_c + T_1}{R_1} = \frac{T_c + T_2}{R_2}$$

$$\therefore R_2 = \frac{R_1(T_c + T_2)}{T_c + T_1} = \frac{30(234.5 + (-40))}{234.5 + 0} = 24.88\Omega$$

Ans:-

Problem 9.9.1:-

→ Determine the Conductance of 3048 cm length of copper telephone wire which resistivity is $\rho = 1.723 \times 10^{-6} \Omega\text{-cm}$ and there area is $8.04 \times 10^{-4} \text{cm}^2$.

→ Is given:-

$$l = 3048 \text{ cm}$$

$$\rho = 1.723 \times 10^{-6} \Omega\text{-cm}$$

$$A = 8.04 \times 10^{-4} \text{cm}^2$$

We know:-

$$R = \rho \times \frac{l}{A}$$

$$= 1.723 \times 10^{-6} \times \frac{3048}{8.04 \times 10^{-4}}$$

$$= 6.532 \Omega$$

Again:-

$$G = \frac{1}{R}$$

$$= \frac{1}{6.532}$$

$$= 0.153 \text{ mho (or) } \Omega^{-1}$$

Problem 9.15:-

→ Determine the Conductance of 1- Ω , 50k Ω , 100m Ω resistor.

→ We know:-

$$G = \frac{1}{R}$$

$$\therefore G_1 = \frac{1}{R_1} = \frac{1}{1} = 1 \text{ S}$$

$$G_2 = \frac{1}{R_2} = \frac{1}{50 \text{ k}} = 0.02 \text{ mS}$$

$$G_3 = \frac{1}{R_3} = \frac{1}{100 \text{ m}} = 0.01 \text{ uS}$$


Ans:-

TOPIC NAME : _____

DAY : _____

TIME : _____ DATE : / /

problem 4.3:-

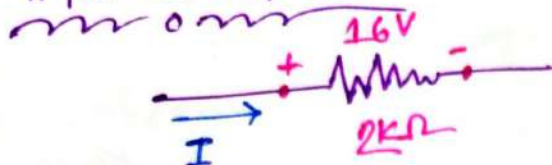

⇒ Calculate the current I .

⇒ In given:-

$$E = 16V$$

$$R = 2k\Omega = 2 \times 10^3 \Omega$$

we know:-

$$E = V = IR$$

$$\therefore I = \frac{V \text{ or } E}{R}$$

$$= \frac{16}{2 \times 10^3}$$

$$= 0.008 A$$

$$= 8 mA$$

problem 4.4:-

⇒ Determine the current through a $5k\Omega$ resistor when the power dissipated by the element is $20 mW$.

⇒ In given:-

$$R = 5k\Omega = 5 \times 10^3 \Omega$$

$$P = 20 mW = 20 \times 10^{-3} W$$

we know:-


$$P = I^2 R$$

$$\therefore I = \sqrt{\frac{P}{R}} = \sqrt{\frac{20 \times 10^{-3}}{5 \times 10^3}} = 0.022 A$$

$$= 22 mA$$

Ans:-

problem 8.2

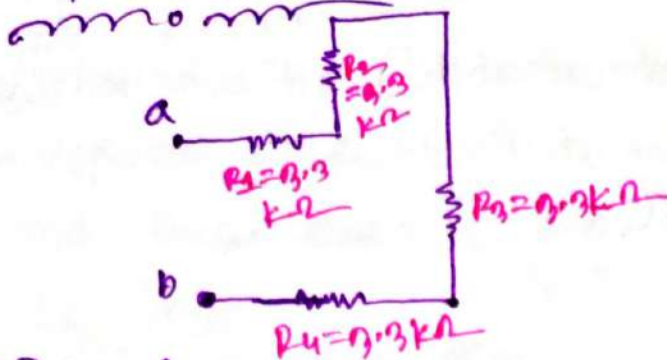

⇒ Determine the total resistance.

⇒ Is given:—

$$R_1 = R_2 = R_3 = R_4 = 3.3 \text{ k}\Omega$$


We know:—

$$R_T = R_1 + R_2 + R_3 + R_4$$

$$\begin{aligned} \therefore R_T &= 4R_1 \\ &= 4 \times 3.3 \text{ k}\Omega \\ &= 13.2 \text{ k}\Omega \end{aligned}$$

Ans:

Problem: 41!—

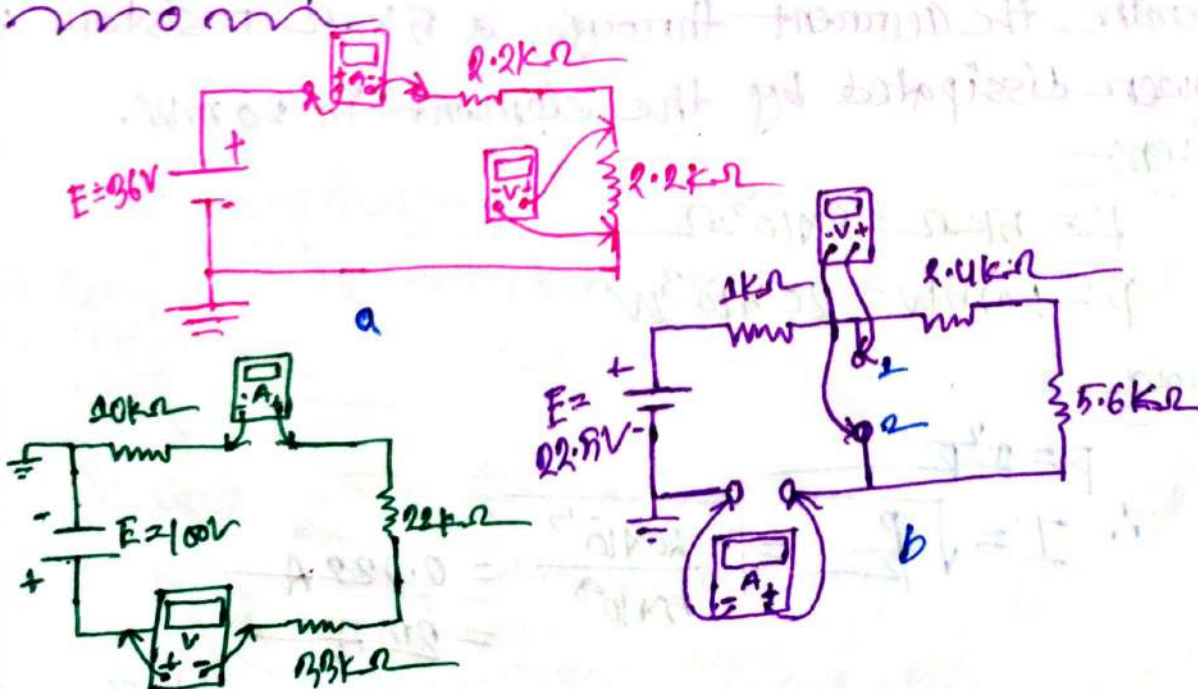

$$R_{\text{net}} = 10 \text{ M}\Omega$$

⇒ Find the Current And Voltage?

(a)

Is given:-
now

$$E = 36V$$

$$R_1 = 2.2k\Omega$$

$$R_2 = 2.2k\Omega$$

we know:-
now

$$R_T = R_1 + R_2$$

$$= 2.2 + 2.2 = 4.4k\Omega$$

$$I_s = \frac{E}{R} = \frac{36}{4.4k} = 8.18 \times 10^{-3} A$$

$$= 8.18 mA$$

$$V_s = I_s R_2 = (8.18 \times 10^{-3} \times 2.2 \times 10^3)$$

$$= 18V$$

Ans:-

(b)

Is given:-
now

$$E = 22.5V$$

$$R_1 = 1k\Omega$$

$$R_2 = 2.4k\Omega$$

$$R_3 = 5.6k\Omega$$

we know:-
now

$$R_T = R_1 + R_2 + R_3$$

$$= 1 + 2.4 + 5.6 = 9k\Omega$$

$$I_s = \frac{E}{R_T} = \frac{22.5}{9k} = 2.5mA$$

$$V_{s2} = I_s R' = (2.5m \times 8k) = 20V$$

Ans:-

③

Is given:-

$$\begin{array}{l} E = 100V \\ R_{net} = 10m\Omega \end{array} \left\{ \begin{array}{l} R_1 = 10k\Omega \\ R_2 = 22k\Omega \\ R_3 = 33k\Omega \end{array} \right.$$

we know:-

$$\begin{aligned} R' &= R_1 + R_2 + R_3 \\ &= (10 + 22 + 33)k\Omega \\ &= 65k\Omega \\ &= 65 \times 10^3 k\Omega \end{aligned}$$




$$\begin{aligned} \therefore R &= R' + R_{net} \\ &= 10 \times 10^6 + 65 \times 10^3 \\ &= 10.065m\Omega \end{aligned}$$

$$\begin{aligned} I &= \frac{E}{R} \\ &= \frac{100}{10.065m} \\ &= 9.935\mu A \end{aligned}$$

$$\begin{aligned} V &= IR_{net} \\ &= (9.935\mu) \times (10m) \\ &= 99.354 \text{ Volt} \end{aligned}$$

Ans:-

problems :-

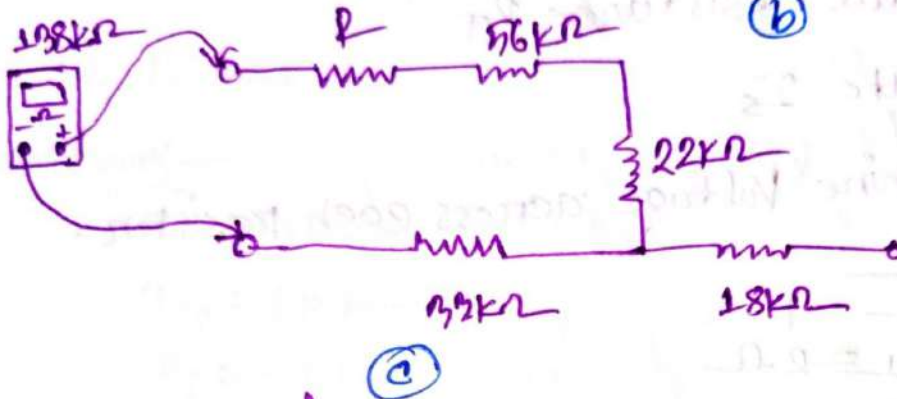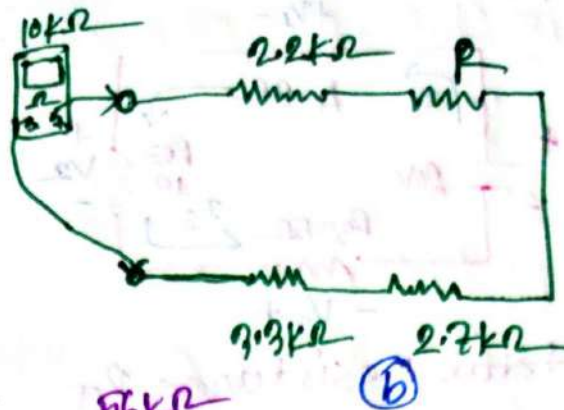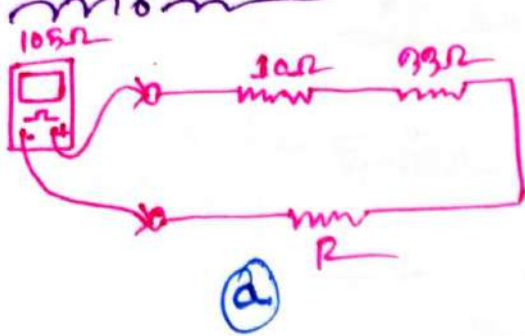

Find the value of R

(a)

$$R_T = R_1 + R + R_2$$

$$R = R_T - R_1 - R_2$$

$$= 105 - 10 - 33 = 62 \Omega$$

(b)

$$R_T = R_1 + R_2 + R_3 + R$$

$$\therefore R = 10k - (2.2k + 3.3k + 2.7k)$$

$$= 10k - 8.2k$$

$$= 1.8k$$

(c)

Is given :-

$$R_1 = 56k\Omega$$

$$R_2 = 22k\Omega$$

$$R_3 = 18k\Omega$$

$$R_4 = 33k\Omega$$


we know

$$R_T = R + R_1 + R_2 + R_4$$

$$\therefore R = 138k - (56k + 22k + 33k)$$

$$= 27k$$

problem: 5.4:-

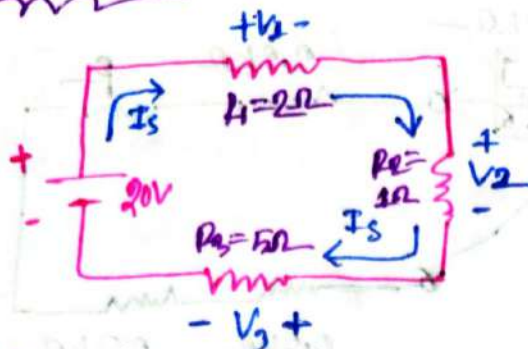

- ① Find total resistance R_T
- ② Calculate I_s
- ③ Determine Voltage across each resistor.

⇒ I_s given:-

$$R_1 = 2\Omega$$

$$R_2 = 1\Omega$$

$$R_3 = 5\Omega$$

$$E = 20V$$

①

we know:-

$$R_T = R_1 + R_2 + R_3$$

$$= 1 + 2 + 5 = 8\Omega$$

②

we know:-

$$I_s = \frac{E}{R_T} = \frac{20}{8} = 2.5A$$

③

we know:-

$$V_1 = I_s R_1 = 2.5 \times 2 = 5V$$

$$V_2 = I_s R_2 = 2.5 \times 1 = 2.5V$$

$$V_3 = I_s R_3 = 2.5 \times 5 = 12.5V$$


TOPIC NAME: _____

DAY: _____

TIME: _____

DATE: / /

#problem 5.6! —
~~~~~

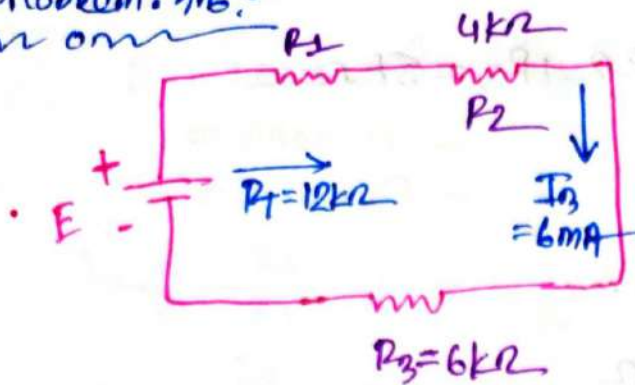

① Find the E and  $R_1$

⇒ we know —  
~~~~~

$$R_T = 12k\Omega$$

$$I_3 = 6mA = I_s$$

$$R_2 = 4k\Omega$$

$$R_3 = 6k\Omega$$

we know —
~~~~~

$$R_T = R_1 + R_2 + R_3$$

$$\therefore R_1 = (12 - 4 - 6)k = 2k\Omega$$


$$E = I_s R_T$$

$$= 6mA \times 12k\Omega$$

$$= 72V$$

Ans: —

#problem 5.16! —  
~~~~~

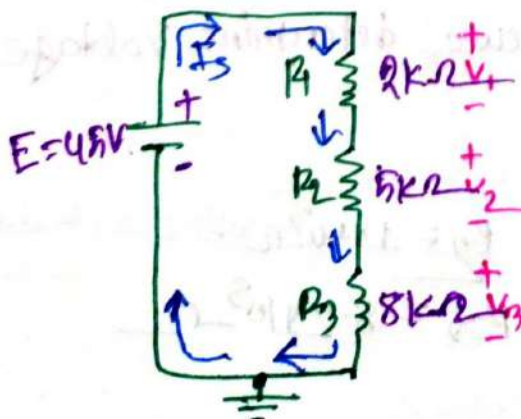

⇒ using the Voltage divider rule; determine voltage V_1 , V_2 , V_3 for the circuit.

TOPIC NAME: _____

DAY: _____

TIME: _____

DATE: / /

We have:-

$$R_1 = 2k\Omega, R_2 = 5k\Omega, R_3 = 8k\Omega$$

$$E = 45V$$

We know:-

$$R_T = R_1 + R_2 + R_3$$

$$= (2 + 5 + 8) k\Omega$$

$$= 15k\Omega$$


$$V_1 = \frac{R_1}{R_T} \times E = \frac{2k \times 45}{15k} = 6V$$

$$V_2 = \frac{R_2}{R_T} \times E = \frac{5k \times 45}{15k} = 15V$$

$$V_3 = \frac{R_3}{R_T} \times E = \frac{8k \times 45}{15k} = 24V$$

Ans:-

problem 5.7.1:-

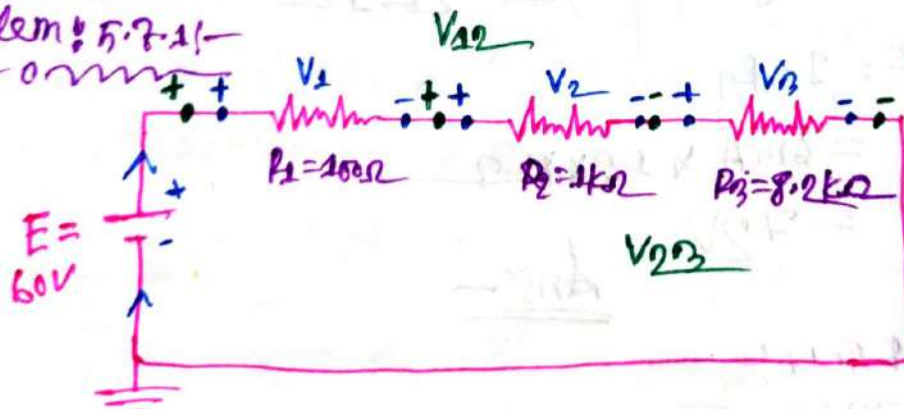

⇒ Using voltage divider rule determine voltage V_1, V_2, V_3, V_{23} and V_{23} .

⇒ Is given:-

$$\begin{aligned} E &= 60V \\ R_1 &= 100\Omega \end{aligned} \quad \begin{aligned} R_2 &= 1 \times 10^3 \Omega \\ R_3 &= 8.2 \times 10^3 \Omega \end{aligned}$$

TOPIC NAME : _____

DAY : _____

TIME : _____

DATE : / /

we know,
now

$$R_T = 100 + 1 \times 10^3 + 8.2 \times 10^3$$

$$= 9300 \Omega$$

$$= 9.3 k\Omega$$

$$V_1 = \frac{R_1}{R_T} \times E = \frac{100 \times 60}{9300} = 0.6451 V$$

$$V_2 = \frac{R_2}{R_T} \times E = \frac{1k \times 60}{9.3k} = 6.451 V$$

$$V_3 = \frac{R_3}{R_T} \times E = \frac{8.2k \times 60}{9.3k} = 52.903 V$$

Now,

$$R_{12} = R_1 + R_2 = 100 + 1000 = 1100 \Omega$$


$$R_{23} = R_2 + R_3 = 1000 + 8200 = 9200 \Omega$$

$$V_{12} = \frac{R_{12}}{R_T} \times E = \frac{1100 \times 60}{9300} = 7.096 V$$

$$V_{23} = \frac{R_{23}}{R_T} \times E = \frac{9200 \times 60}{9300} = 59.354 V$$

Ans:-

Problem 5.8:-

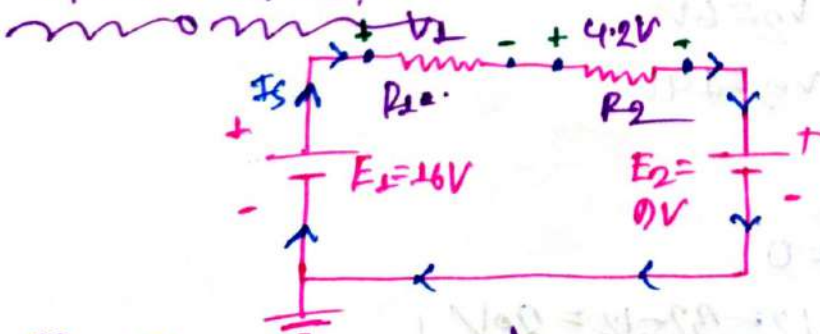

① Find the value of V_1

①

we have

$$E_1 = 16V$$

$$E_2 = 0V$$

$$V_2 = 4.2V$$


we know

$$E_1 - V_1 - V_2 - E_2 = 0$$

$$\begin{aligned} \therefore V_1 &= E_1 - V_2 - E_2 \\ &= 16 - 4.2 - 0 \\ &= 11.8V \end{aligned}$$

Ans:-

#problem 5.9:-

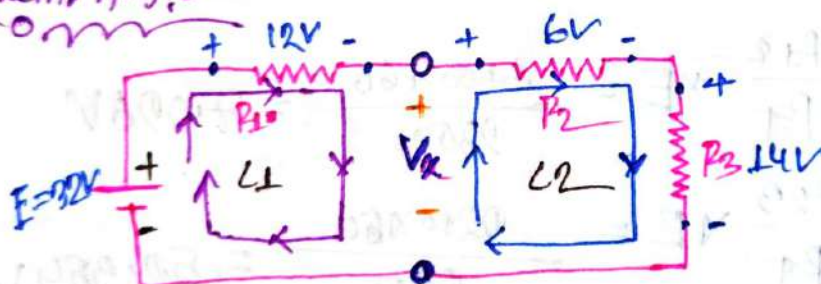

⇒ Determine the unknown voltage V_x .

⇒ It is given

$$\begin{aligned} E &= 32V, \quad \begin{cases} V_2 = 6V \\ V_3 = 14V \end{cases} \\ V_1 &= 12V \end{aligned}$$

From 1st loop

$$E - 12 - V_x = 0$$

$$\therefore V_x = E - 12 = 32 - 12 = 20V$$

Ans:-

From 2nd loop


$$V_x + 6 - 14 = 0$$

$$\therefore V_x = 14 - 6 = 8V$$

Ans:-

#problem:- 5.6.1:-

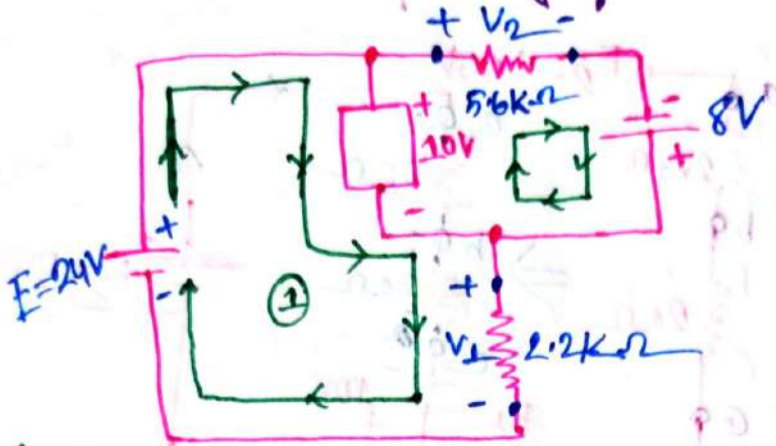1) Determine the unknown voltage for the following circuit



2) In given:-

$$E = 24V$$

$$R_1 = 2.2k\Omega$$

$$R_2 = 5.6k\Omega$$

We know:-

from 1st loop:-

$$24 - 10 - V_1 = 0$$

$$V_1 = 14V$$


from 2nd loop:-

$$8V + 10V - V_2 = 0$$

$$\therefore V_2 = 18V \quad \underline{\underline{\text{Ans:-}}}$$

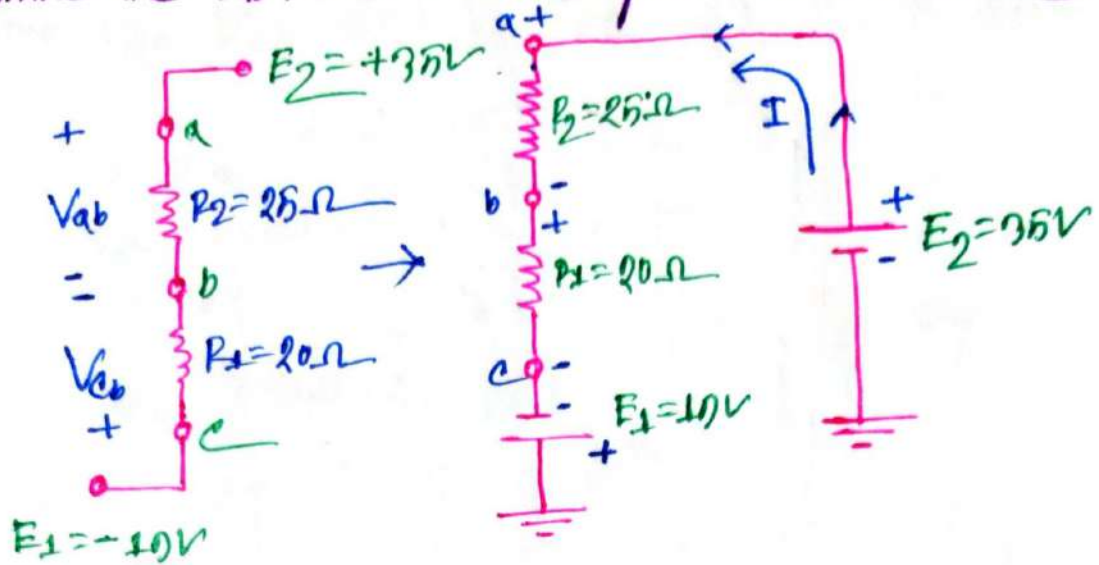problem 8.26:-

⇒ Determine the V_{ab} , V_{cb} , and V_c for the network.



we have—

$$\begin{matrix} E_2 = 35V \\ E_1 = 10V \end{matrix} \int \begin{matrix} R_1 = 25\Omega \\ R_2 = 20\Omega \end{matrix}$$

we know—

$$E_{net} = E_1 + E_2 = 35 + 10 = 54V$$

$$R_T = R_1 + R_2 = 25 + 20 = 45\Omega$$

$$\therefore I = \frac{E}{R} = \frac{54}{45} = 1.2A$$

$$V_{ab} = IR_2 = 1.2 \times 25 = 30V$$

$$V_{cb} = -IR_1 = 1.2 \times 20 = -24V$$

$$V_c = E_1 = -10V$$

TOPIC NAME : _____

TIME : _____

DATE : / /


#Ch#6
Parallel DC
Circuit

Parallel Circuit!—

⇒ For parallel Connection, the end of one circuit component is connected to two or more than two terminals of other components (like +ve end of battery is connected to end of R_1, R_2, R_3 & R_4).

- ① The Voltage of component in parallel remains same.
- ② The Current changes for each branch depending on the value of resistors.


Note— Opposite to a Series Circuit.

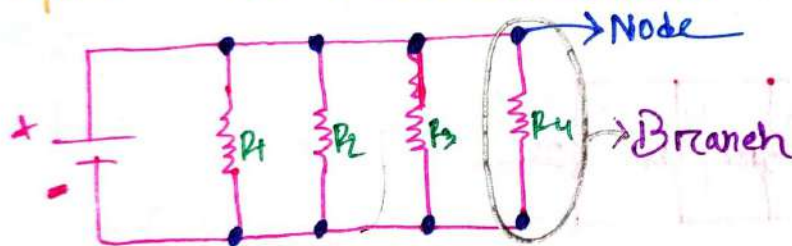

Parallel Resistance!—

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4}$$


Let, Say 2 resistors in parallel!—

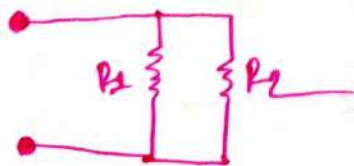

$$\therefore \frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} = \frac{R_1 + R_2}{R_1 R_2}$$

$$\therefore R_T = \left(\frac{R_1 + R_2}{R_1 R_2} \right)^{-1}$$


* n' equal resistor in parallel:-

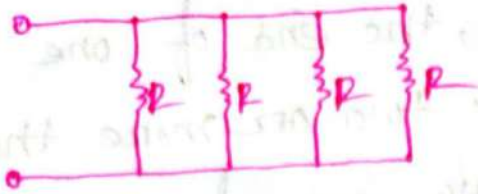

$$\begin{aligned} \therefore \frac{1}{R_T} &= \frac{1}{R} + \frac{1}{R} + \frac{1}{R} + \frac{1}{R} \\ &= \frac{1}{R} (1+1+1+1) \\ &= \frac{4}{R} \end{aligned}$$

$$\boxed{\therefore R_T = \frac{R}{4}}$$

#problem:-

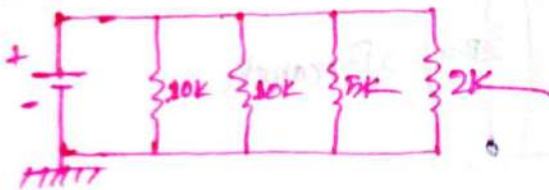

⇒ Find the value of R_T

⇒ Is given:-

$$\begin{aligned} R_1 &= 10k\Omega & R_3 &= 5k\Omega \\ R_2 &= 10k\Omega & R_4 &= 2k\Omega \end{aligned}$$

we know:-


$$R' = \frac{R}{2} = \frac{10k}{2} = 5k$$

$$R' = \frac{5}{2} = 2.5k$$

$$R_T = \frac{R' \times R_4}{R' + R_4} = \frac{2.5 \times 2}{2.5 + 2} = 1.111k\Omega$$

Ans:-

Problem:-
non

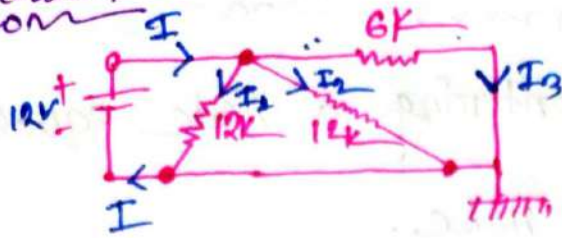

⇒ ① Find R_T

② Find I , I_1 , I_2 , I_3

⇒ Is given:-
non

$$\left. \begin{array}{l} E = 12V \\ R_1 = 12k\Omega \\ R_2 = 12k\Omega \end{array} \right\} R_3 = 6k\Omega$$

we know:-
non

①

$$\begin{aligned} R_T &= \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)^{-1} \\ &= \left(\frac{1}{12k} + \frac{1}{12k} + \frac{1}{6k} \right)^{-1} \\ &= 3k\Omega \end{aligned}$$

we know:-
non

②

$$I = \frac{E}{R_T} = \frac{12}{3 \times 10^3} = 4 \times 10^{-3} A = 4mA$$

$$I_1 = \frac{E}{R_1} = \frac{12}{12k} = 1mA$$

$$I_2 = \frac{E}{R_2} = \frac{12}{12k} = 1mA$$


$$I_3 = \frac{E}{R_3} = \frac{12}{6k} = 2mA$$

Ans:-


Kirchhoff's Current Law (KCL)

⇒ The ~~same~~ ^{Sum} of Currents entering a node equals Sum of Currents exiting the node.

$$\therefore I = I_1 + I_2 + I_3$$
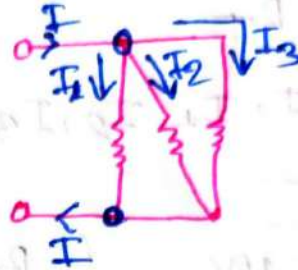
# Current Divider rule: (CDR):—


For 2 resistor:—

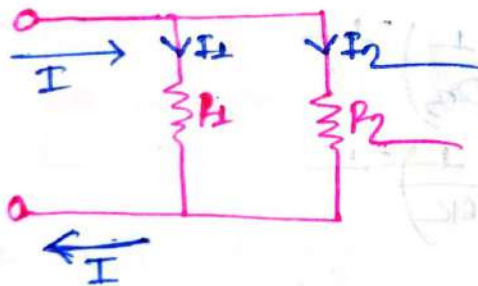

$$\therefore I_1 = \frac{R_2}{R_1 + R_2} \times I$$

$$I_2 = \frac{R_1}{R_1 + R_2} \times I$$


For Multiple resistors—

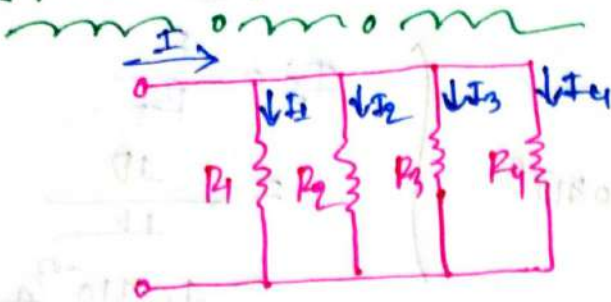

$$I_k = \frac{R_T}{R_k} \times I$$

I_k = 'X' th resistor current.

problem!—

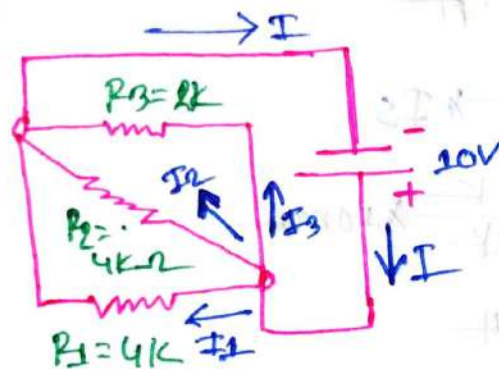

- ① Find the R_T
- ② Find the branch current using CDR
- ③ Find the I_s
- ④ verify KCR

⇒ I_s given!—

$$R_3 = 2k\Omega, R_2 = 4k\Omega, R_1 = 4k\Omega$$

$$E = 10V$$

We know!—

①

$$R_T = \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)^{-1} = \left(\frac{1}{4k} + \frac{1}{4k} + \frac{1}{2k} \right)^{-1} = 1k$$

Ans:-

(ii)

We know:-

$$I_1 = \frac{R_T}{R_1} \times I_S$$

$$I_1 = \frac{1k}{4k} \times 10 \times 10^{-3}$$

$$= 2.5 \text{ mA}$$

$$I_2 = \frac{R_T}{R_2} \times I_S$$

$$= \frac{1k}{4k} \times 10 \text{ mA}$$

$$= 2.5 \text{ mA}$$

$$I_3 = \frac{R_T}{R_3} \times I_S$$

$$= \frac{1k}{2k} \times 10 \text{ mA}$$

$$= 5 \text{ mA}$$

(iii)

$$I_S = \frac{E}{R_T}$$

$$= \frac{10}{1k}$$

$$= 10 \times 10^{-3} \text{ A}$$

$$= 10 \text{ mA}$$

(iv)

The Value of total Entering Current = I
 $= 10 \text{ mA}$

The Value of "Exiting Current" = $I_1 + I_2 + I_3$
 $= 2.5 + 2.5 + 5$
 $= 10 \text{ mA}$

$$\therefore I = I_1 + I_2 + I_3$$

(Verified)


TOPIC NAME : _____

DAY : _____

TIME : _____


DATE : / /

#Voltage Source in Parallel:-

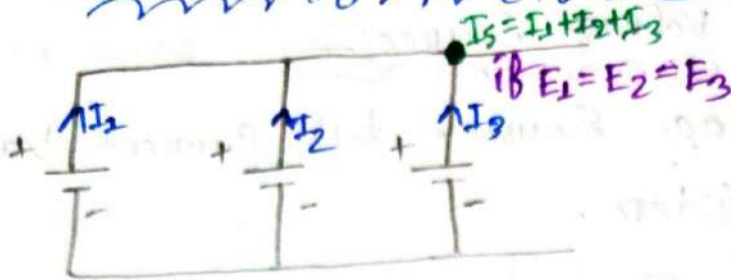


⇒ If Voltage Source are connected as above (all the terminal connected together and -ve terminal also connected together) Sources must be of similar value, hence voltage across will remain same.

Not Recommended Circuit:-

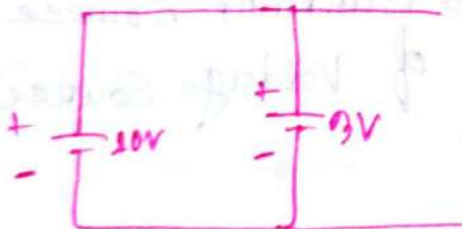

⇒ Not recommended in this type of circuit because in this case the low voltage battery will be destroyed by the current from the high voltage battery.

but:-

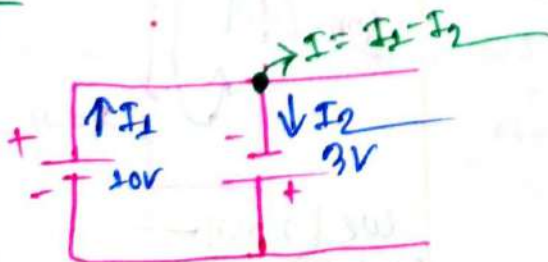

In this case the total current ~~decreases~~ increases.


Current Source in Parallel?

We know:- from Voltage Source:-

⇒ Constant Voltage Source but Current Varies due to Connected resistor.

And the ^{Current} Voltage Source:-

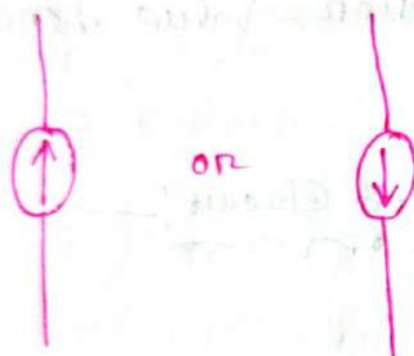⇒ Constant current Source but Voltage Varies due to Connected resistor.




Symbol of Current Source.

→ The arrow sign indicate the direction of Current.

→ Current Source is a dual of Voltage Source.

problem 1

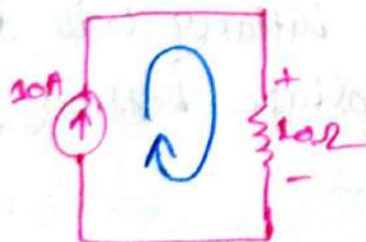


Q → Find the Voltage

⇒ We know -

$$\begin{aligned} V &= IR \\ &= 10A \times 10\Omega \\ &= 100V \end{aligned}$$

problem 2

Find the Voltage?

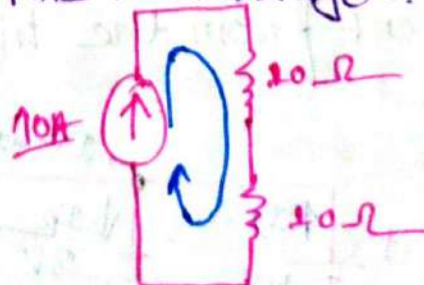


We know -

$$\begin{aligned} V &= IR \\ &= 10(10 + 10) \\ &= 200V \end{aligned}$$

problem: 3

⇒ find the voltage:- also find I_1, I_2

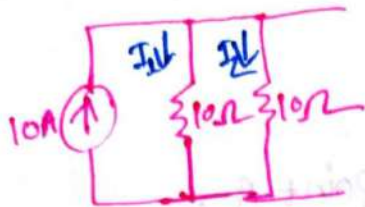

⇒ we know:-

$$V = IR$$

$$= 10 \times 5$$

$$= 50V$$

we know:-


$$R_T = \left(\frac{1}{10} + \frac{1}{10} \right)^{-1}$$

$$= 5\Omega$$

$$I_1 = \frac{R_T}{R_1} \times I_S = \frac{5}{10} \times 10 = 5A$$

$$I_2 = \frac{R_T}{R_2} \times I_S = \frac{5}{10} \times 10 = 5A$$

problem: 4

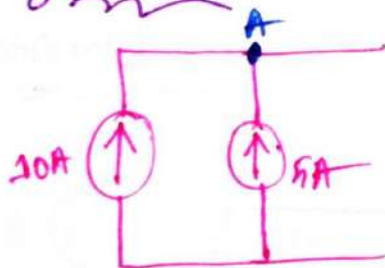

⇒ Find the value of current at point A

⇒ Since

The direction of arrows are same side

So, $I = I_1 + I_2$ at point A

$$= 10 + 5$$


$$= 15A$$

TOPIC NAME : _____

DAY : _____

TIME : _____ DATE : / /

problem:-

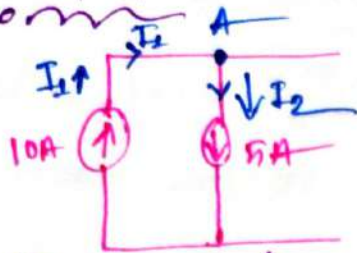

⇒ Find the value of current at point A.


⇒ Since, The direction of arrows are opposite each other

$$\begin{aligned} \text{So, } I &= I_1 - I_2 \\ &= 10 - 5 \\ &= 5A \end{aligned}$$


Note:-

⇒ It is not possible to connect two or more than two current sources in series. (as current should be same in series)


That means:-

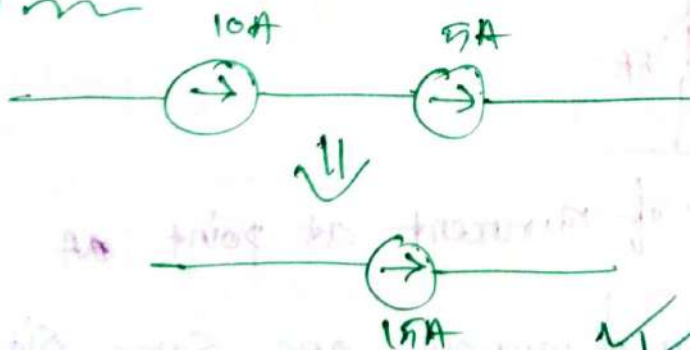


But:-

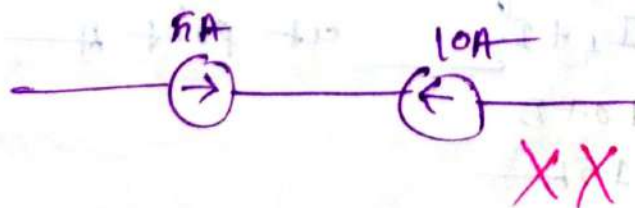


Source Transformation! —

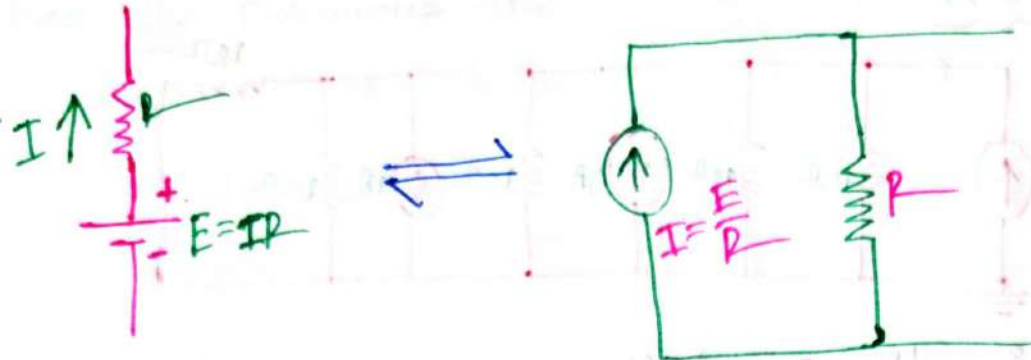


Ex-8 —

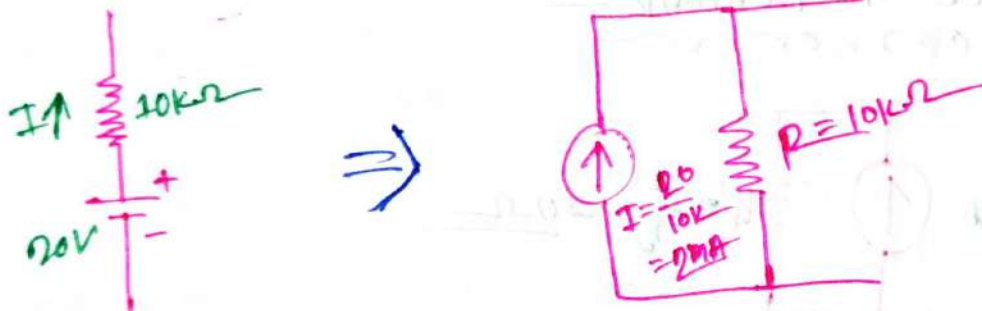

Problem 1: —

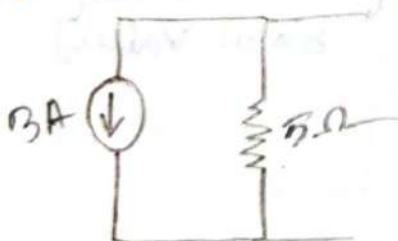

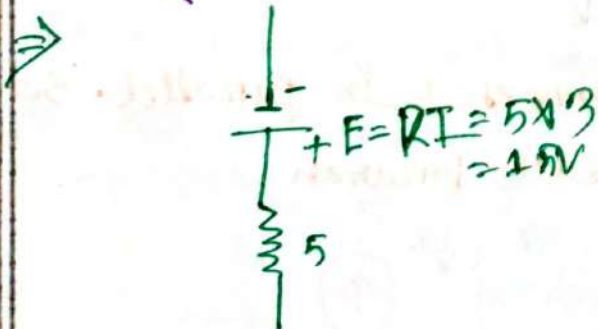⇒ Convert the circuit into a Voltage Source.




TOPIC NAME : _____

DAY : _____

TIME : _____ DATE : / /


Problem Solⁿ :-

problem 1 :-

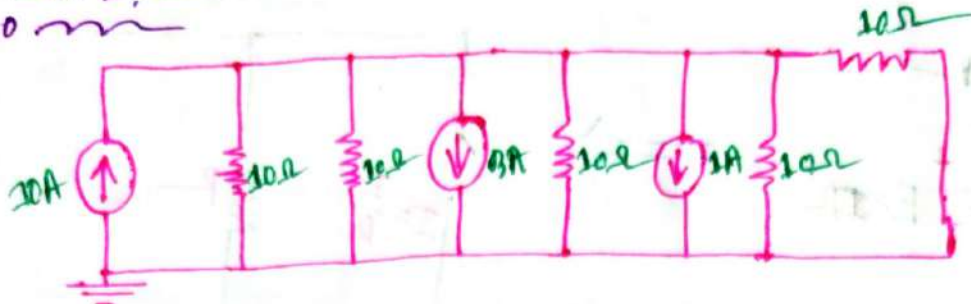

- i) Determine the R_T , Voltage across each Branch, Current for each resistor.

⇒ 1st reduce the Network :-

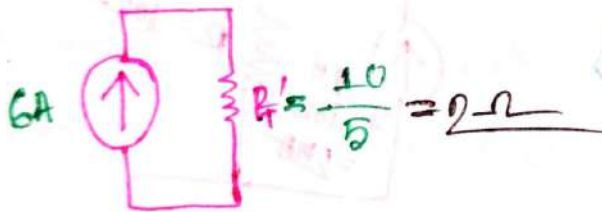

We know :-

$$R_T = \frac{R}{5} \Omega$$

$$= \frac{10}{5} \Omega$$

$$= 2 \Omega$$

[Since every resistor contain same value]

for voltage :-

$$I = \frac{V}{R}$$

$$\therefore V = I R_T = 6 \times 2 = 12V$$

Hence every resistor are connected in parallel. So, The voltage are same each Branch.

TOPIC NAME : _____

DAY : _____

TIME : _____ DATE : / /

For each resistor Current:-

⇒ Since, The resistors are Contained Same value. So Current for each resistor will be Same.

$$\therefore V = IR$$

$$\therefore I = \frac{V}{R} = \frac{12}{10} = 1.2A$$

OR


$$I' = \frac{R_1}{R_1} \times I_1$$

$$= \frac{2}{10} \times 6$$

$$= 1.2A$$

$$\therefore I_1 = I_2 = I_3 = I_4 = I_5 = 1.2A$$

Problem: 2

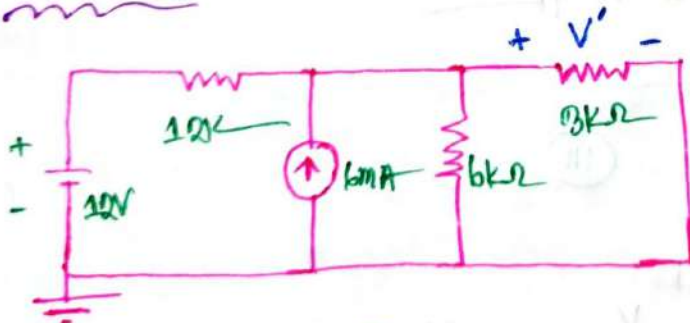


- ① Determine the total Current.
- ② Find V'
- ③ Current through each resistor.

⇒ 1st transform the circuit:-



Now, Reduce the circuit

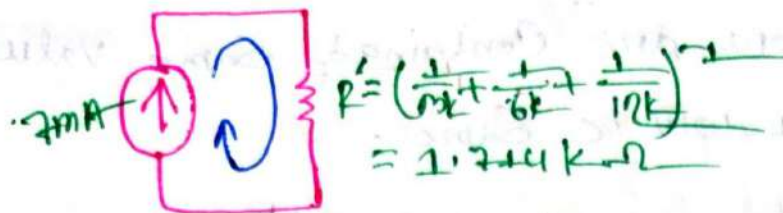

(i)

The total current $I = 6mA + 1mA$
 $= 7mA$

(ii)

Since, Every resistor are connected in parallel so the Voltage of every resistor will be equal.

$$\therefore V' = IR_T$$

$$= 7mA \times 1.714k$$

$$= 12V$$

(iii)

We know

$$V = IR$$

$$\therefore I_1 = \frac{V}{R_1} = \frac{12}{12} = 1A$$

$$I_2 = \frac{V}{R_2} = \frac{12}{6} = 2A$$

$$I_3 = \frac{V}{R_3} = \frac{12}{3} = 4A$$


TOPIC NAME : _____

DAY : _____

TIME : _____

DATE : / /

Series Parallel Network

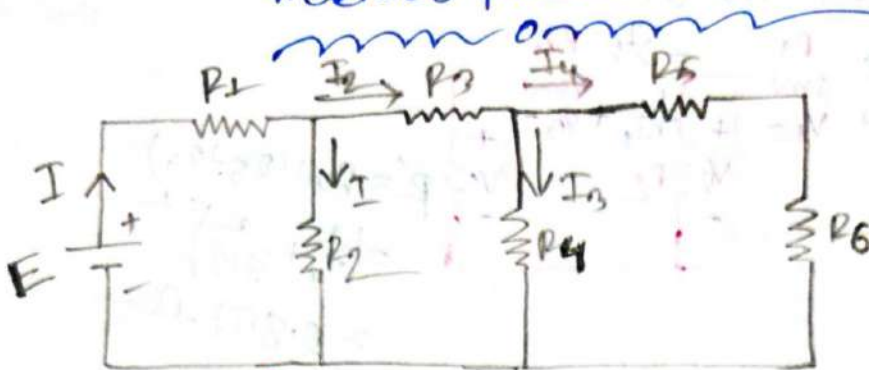


Ladder Network

⇒ To solve the network/circuit, reduce the ~~current~~ circuit from the other end of the source, find I_T and R_T then return.

$$R_T = R_1 + \left[R_2 \parallel \left[R_3 + \left\{ R_4 \parallel (R_5 + R_6) \right\} \right] \right]$$


$$\therefore I_S = \frac{E}{R_T}$$

Problem 1

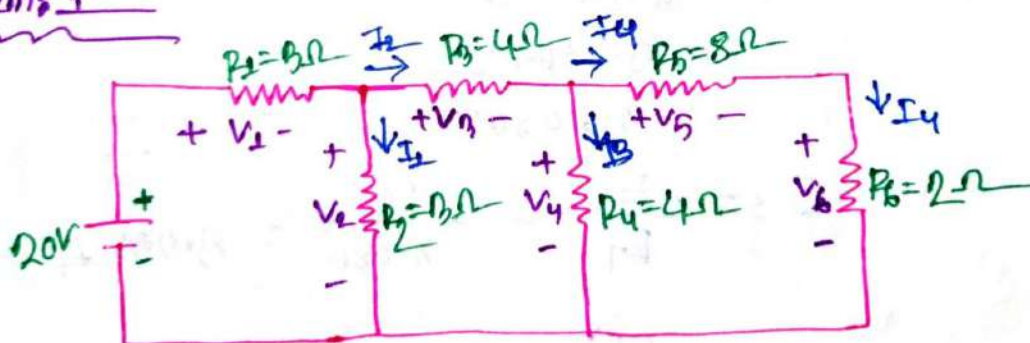


- ① Find R_T and I_S .
- ② Voltage across each Branch
- ③ Current for each resistor.

→ 1st reduce the network

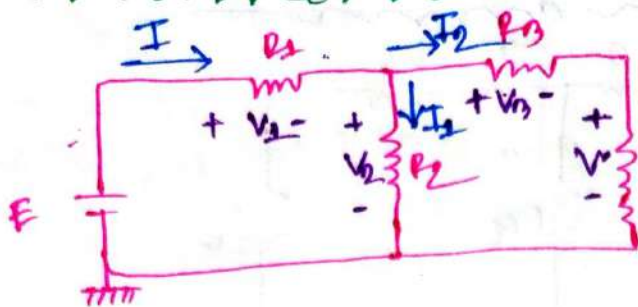

$$R' = R_{\text{all}} (R_3 + R_4) \\ = \left(\frac{1}{4} + \frac{1}{8+2} \right)^{-1} \\ = 2.857 \Omega$$

Again:-

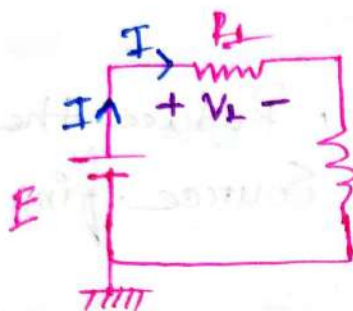

$$R'' = R_{\text{all}} (R_2 + R') \\ = \left(\frac{1}{3} + \frac{1}{2.857+4} \right)^{-1} \\ = 2.086 \Omega$$

we know:-

$$R_T = R_1 + R'' \\ = 2.086 + 3 \\ = 3.086 + 2 \\ = 5.086 \Omega$$

$$I_s = \frac{E}{R_T} = \frac{20}{5.086} = 3.932 \text{ A}$$

②

we know:-

$$V_1 = I R_1 \\ = 3.932 \times 3 \\ = 11.796 \text{ V}$$

$$V_2 = I_2 R_2 \\ = 2.734 \times 3 \\ = 8.202 \text{ V}$$

TOPIC NAME : _____

DAY : _____

TIME : _____ DATE : / /

$$V_3 = I_3 R_3$$

$$= 1.106 \times 4$$

$$= 4.784V$$

$$V_4 = I_4 R_4$$

$$= 0.854 \times 4$$

$$= 3.416V$$

$$V_6 = I_4 R_6$$

$$= 0.341 \times 2$$

$$= 0.684V$$

$$V_8 = I_4 R_8$$

$$= 0.341 \times 8$$

$$= 2.728V$$

iii

We know, -
now

$$I_1 = \frac{R''}{R_2} \times I$$

$$= \frac{2.086}{3} \times 3.032$$

$$= 2.734A$$

$$I_2 = \frac{R''}{R_3 + R_6} \times I$$

$$= \frac{2.086}{4 + 2.857} \times 3.032 \quad \text{OR}$$

$$= 1.106A$$

from KCL:-
now

$$I = I_1 + I_2$$

$$\therefore I_2 = I - I_1$$

$$= 3.032 - 2.734$$

$$= 1.108A$$

$$I_s = \frac{V}{R_T} = \frac{10}{6.22} = 1.6072$$

TOPIC NAME : _____

DAY : _____

TIME : _____ DATE : / /

$$\therefore V_2 = \frac{R'' \times E}{R'' + 4} = \frac{22.2}{6.22} = 3.560V$$

Since V_1 and V_2 parallel connected, so voltage of V_1 and V_2 are equal.


$$\begin{aligned} \therefore V' &= \frac{4}{4+6} \times V_2 \\ &= \frac{4}{10} \times 3.560 \\ &= 1.4276 \text{ Volt.} \end{aligned}$$

Ans:-

Open Circuits

⇒ open circuit is when any of the connections are kept open in a closed circuit.

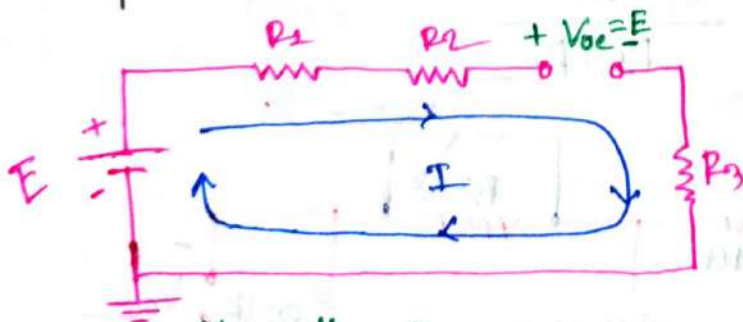For open circuit $I_{oc} = 0$, $R_{oc} = \infty$



As $I = 0$ voltage drops in R_1 , R_2 and R_3 are $= 0$ hence open circuit voltage $V_{oc} = E$

Normally I would be the total current here

If terminal A, B is open, the $I_{oc} = 0$, $R_{oc} = \infty$


TOPIC NAME : _____

DAY : _____

TIME : _____ DATE : / /

Short Circuit:

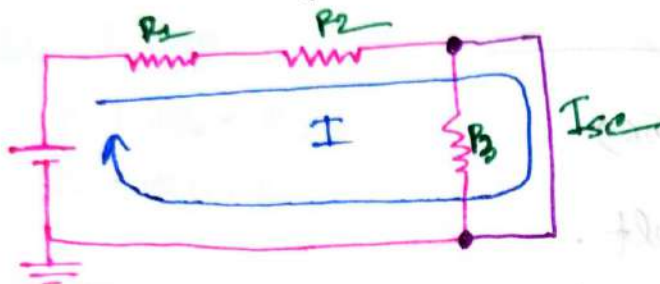- ⇒ It occurs when a circuit component is shorted across.
- ⇒ As current always exist in the least resistive path, short current path always carry the current as $R_{sc} = 0, V_{sc} = 0$



Normally $I = \frac{E}{R_1 + R_2 + R_3}$


But:

Due to R_3 being shorted current I_{sc} will exist in the shorted path as $R_{sc} = 0$. Hence, R_3 won't carry any current

Sol:

$$I = \frac{E}{R_1 + R_2}$$

problem: 1:

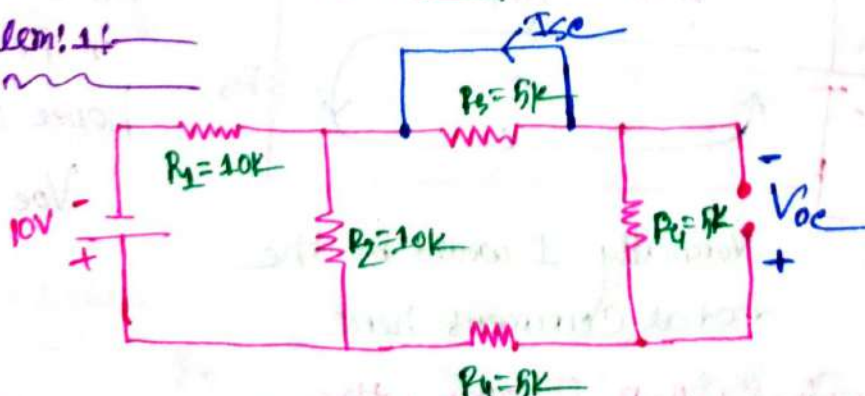

- ⇒ Determine the short circuit current I_{sc} and open circuit voltage, V_{oc} .


TOPIC NAME : _____

DAY : _____


TIME : _____

DATE : / /

⇒ not reduce the circuit

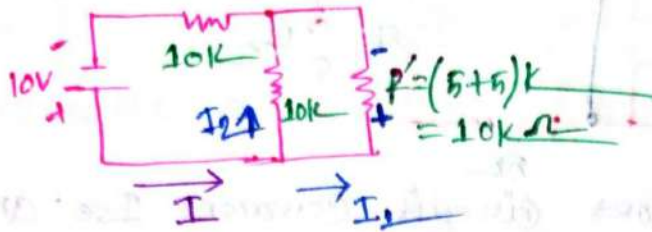

Again:-

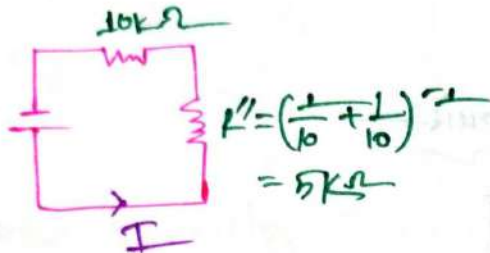

$$\therefore R_T = 10k + 10k - 5k \\ = 20k - 5k \\ = 15k$$

$$\therefore I = \frac{E}{R_T} = \frac{10}{15k} = 0.667mA$$

So, from QDP:-

$$I_1 = \frac{R''}{R'} \times I = \frac{5k}{10k} \times 0.667mA \\ = 0.333mA$$

Here, for this circuit:-

$$I_1 = I_{se} = 0.333mA$$

and, Voltage V_{oe} is:-

$$V_{oe} = I_1 R_4 \\ = 0.333mA \times 5k \\ = 1.667V$$


TOPIC NAME : _____

DAY : _____

TIME : _____

DATE : / /

problem 2:-

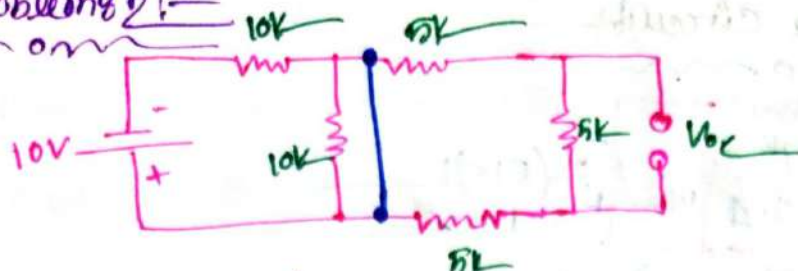

⇒ Determine the short circuit current I_{sc} and Voltage of open circuit.

⇒ 1st reduce the circuit:-



$$\therefore I_{sc} = \frac{10}{10k} = 1mA$$

and Voltage of V_o is:-

$$\begin{aligned} V_o &= V_{oc} = I_{sc} R_5 \\ &= 0.001 \times 5 \\ &= 0.005 \text{ Volt} \end{aligned}$$

Ans:-

TOPIC NAME : _____

DAY : _____

TIME : _____ DATE : / /

#Network Theorems!

Pho 00 00 00

TOPIC NAME : _____


DAY : _____

TIME : _____

DATE : / /

Superposition theorem:-

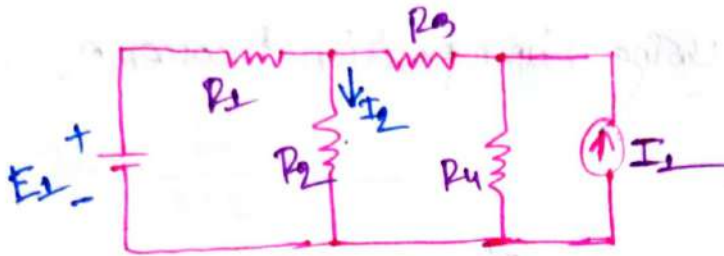⇒ useful for Solving a particular Current or Voltage with circuits of multiple source.



To Determine I_2 using Super position principle we have to do,

- (i) I_2 (for E_1 only) → Deactivating other Source.
- (ii) I_2 (for I_1 only) → " " " "

∴ $I_2 = I_2 \text{ for } E_1 + I_2 \text{ for } I_1$ (if the direction I_2 for E_1 & I_2 for I_1 are same as given I_2 Direction)

or, $I_2 = I_2 \text{ for } E_1 - I_2 \text{ for } I_1$ (If the Direction I_2 for E_1 is same as given I_2 Direction but I_2 for I_1 direction is opposite of given I_2 direction).

for Deactivating Source rule:-

- (1) Voltage Source are short circuited.
- (2) Current Source are open circuited.


TOPIC NAME: _____

DAY: _____

TIME: _____


DATE: / /

Problem 2

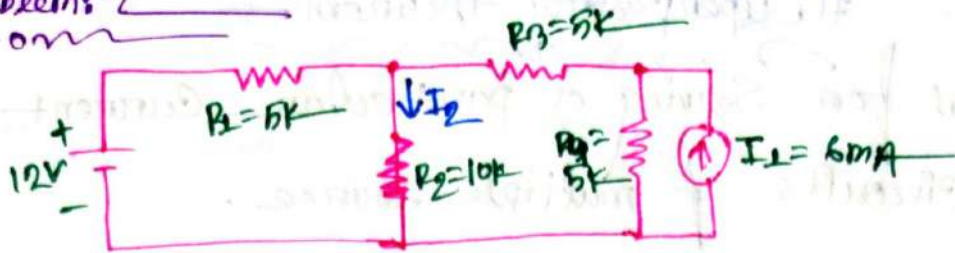


⇒ Determine I_2 using Superposition theorem.

⇒ For E_1 only:—

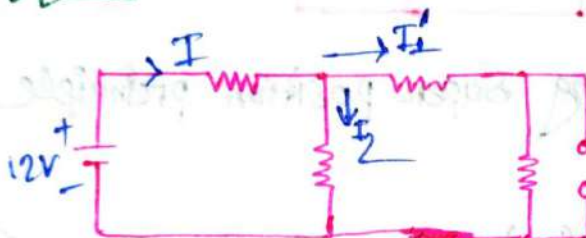


Now Reduce the circuit:—

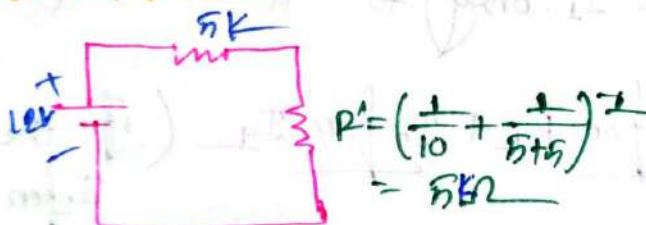

$$\therefore I = \frac{12}{10k} = 1.2mA$$

$$I_2 = \frac{R'}{R_2} \times I = \frac{5k}{10k} \times 1.2mA = 0.6mA$$

⇒ For I_1 only:—


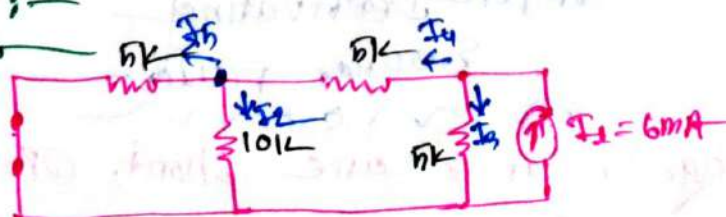


TOPIC NAME : _____

DAY : _____

TIME : _____ DATE : / /

Now Reduce the Circuit!—
no no

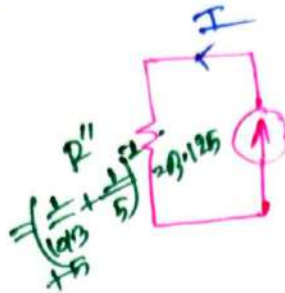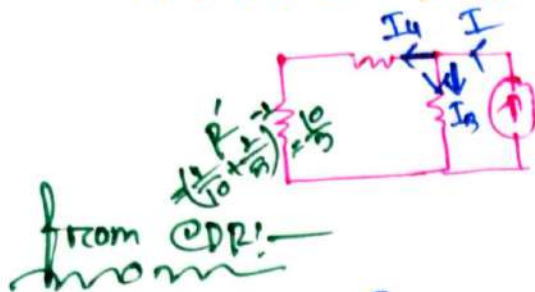

$$I_4 = \frac{R_1}{R_1 + 5} \times I$$

$$= \frac{0.125}{\frac{10}{3} + 5} \times 6 \text{ mA}$$

$$= 2.25 \text{ mA}$$

$$\therefore I_2 = \frac{R_1}{R_2} \times I_4$$

$$= \frac{10/3}{10} \times 2.25 \text{ mA}$$

$$= 0.75 \text{ mA}$$


$$\therefore I_2 = I_2 \text{ for } E_1 + I_2 \text{ for } E_2$$

$$= 0.6 \text{ mA} + 0.75 \text{ mA}$$

$$= 1.35 \text{ mA}$$

Ans!—


Problem!

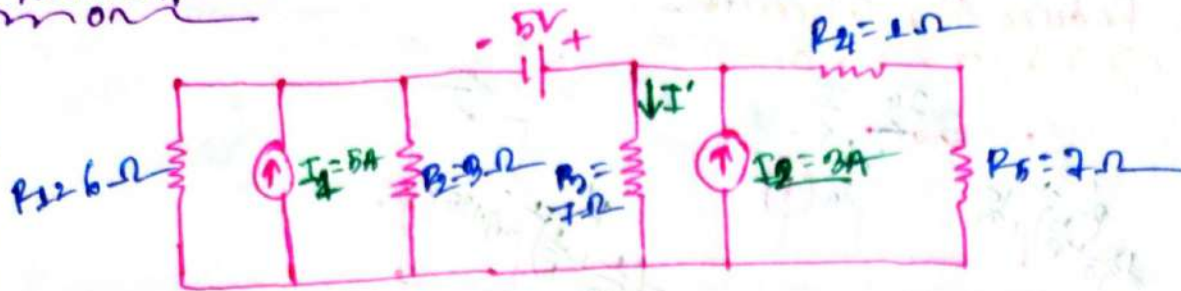



⇒ Determine the current I'

⇒ Using Super position:-

For E_1 only:-

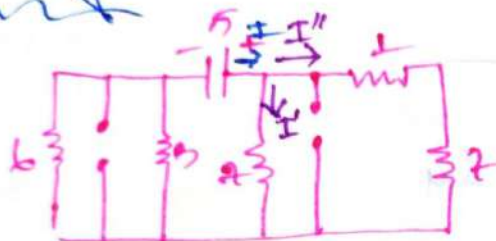

Reduce the circuit:-

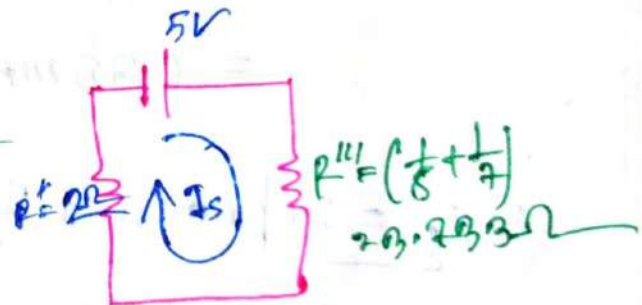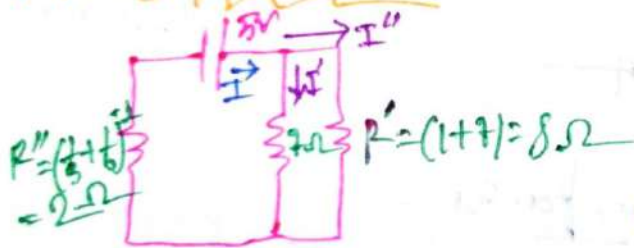

$$\therefore I_S = \frac{E}{R_T} = \frac{5}{2 + 0.793} = 0.872 \text{ A}$$

$$\therefore I' = \frac{R''}{R_3} \times I_S$$

$$= \frac{7.793}{7} \times 0.872$$


$$\boxed{I' = 0.465 \text{ A}}$$

TOPIC NAME : _____



DAY : _____

TIME : _____ DATE : / /

For I_1 Only:-

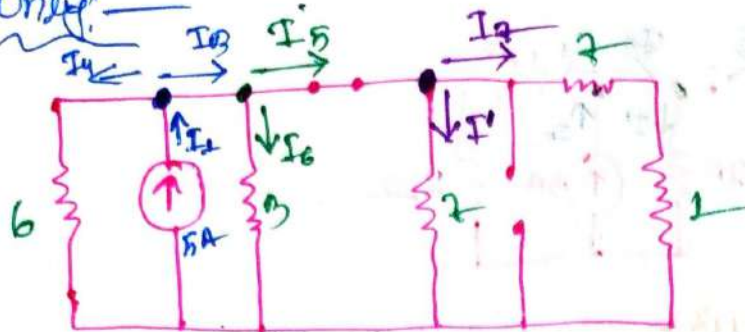

Reduce the circuit:-

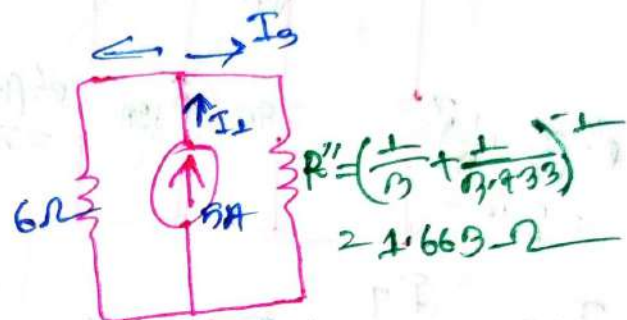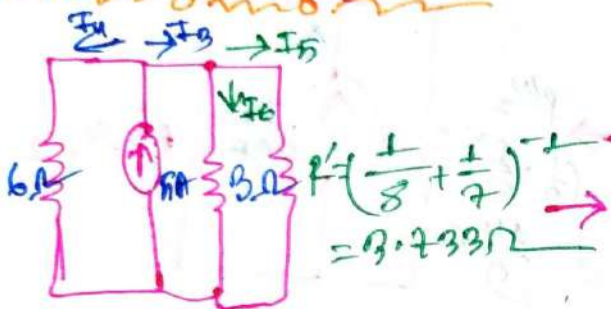

Now,

$$I_3 = \frac{R_T}{R''} \times I_1$$

$$= \frac{1.302}{1.663} \times 5$$

$$= 3.914A$$

$$\therefore R_T = \left(\frac{1}{6} + \frac{1}{1.663} \right)^{-1}$$

$$= 1.302\Omega$$

$$I_5 = \frac{R''}{R'} \times I_3$$

$$= \frac{1.663}{1.2} \times 3.914$$


$$= 5.43A$$

$$I' = \frac{R'}{R_3} \times I_5$$



$$= \frac{1.2}{2} \times 5.43$$

$$I' = 0.326A$$

for I_2 only:

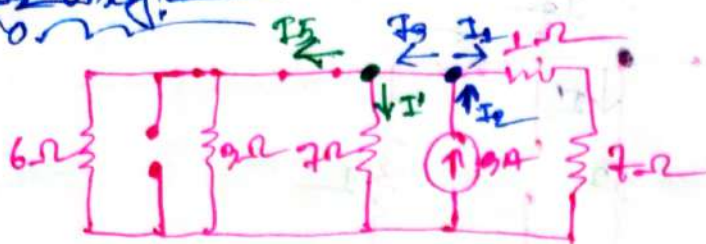

Reduce the circuit:

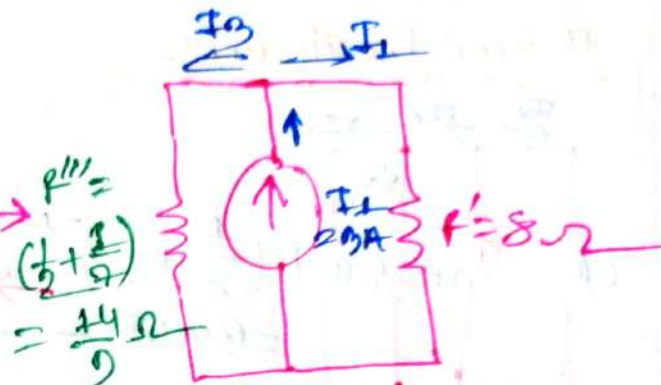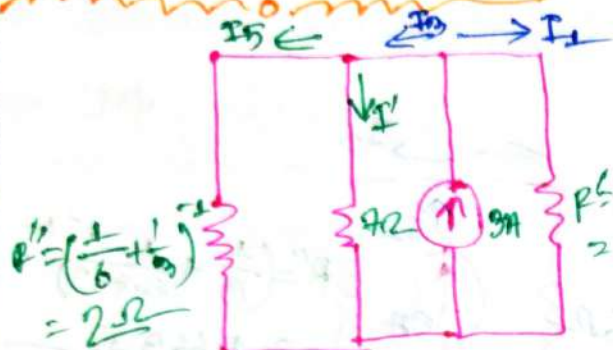

$$I_3 = \frac{P_T}{P_{111}} \times I_1$$

$$= \frac{1.302}{14/9} \times 3$$

$$= 2.511 \text{ A}$$

$$\therefore P_T = \left(\frac{1}{8} + \frac{1}{14/9} \right)^{-1}$$

$$= 1.302 \Omega$$

$$I' = \frac{P_{111}}{P_3} \times I_3$$

$$= \frac{14/9}{7} \times 2.511 \text{ A}$$

$$I' = 0.558 \text{ A}$$

$$\therefore I_{\text{net}} = \text{for } E_1(I') + \text{for } I_1(I') + \text{for } I_2(I')$$

$$= 0.465 \text{ A} + 0.222 \text{ A} + 0.558 \text{ A}$$



$$= 1.245 \text{ A}$$

Ans: _____

THEVENIN'S Theorem! —

⇒ Any two terminal circuit network can be reduced into —

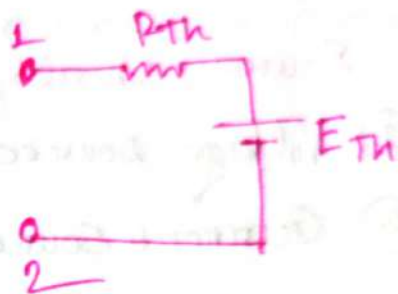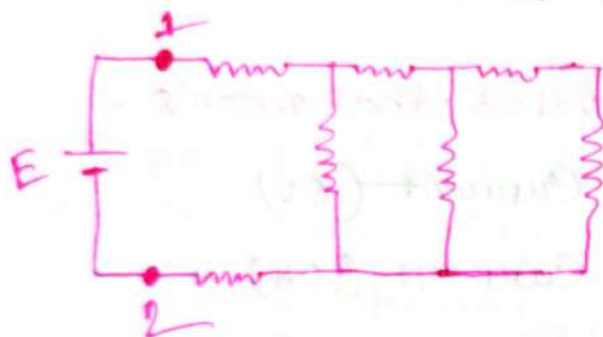① According to thevenin's theorem → a series resistance and an emf (voltage) source.



Thevenin's Equivalent.

where,

R_{Th} = Thevenin's equivalent resistance.

E_{Th} = Thevenin's equivalent Voltage.

Note:-

For the two terminals present: —

① The open circuit Voltage = E_{Th}

② The short circuit Current = I_N

And:-

Total $P_T = R_{Th} = R_N$


TOPIC NAME : _____

DAY : _____

TIME : _____

DATE : / /

Problem:-

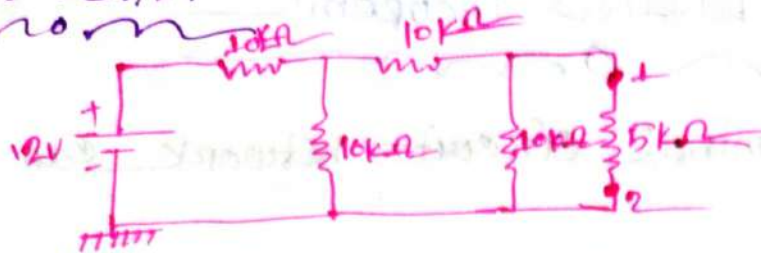

⇒ For the terminal 1 and 2 Find the thevenins equivalent

Note:-


For find $R_T = (R_{Th} \text{ or } R_N)$

⇒ Source should be deactivated that means .


① Voltage source → short Current (0V)

② Current Source → Open Current (0A)

⇒ Redraw the circuit:-

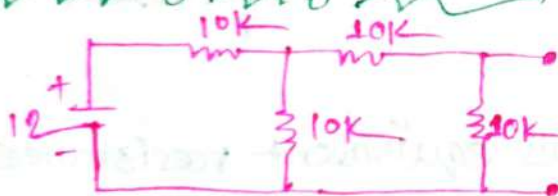


Now for R_T Short the voltage sources:-

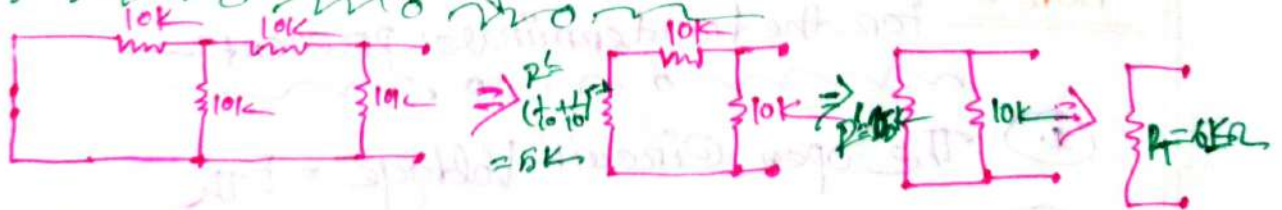

∴ $R_T = 6k\Omega$

Now for R_{Th} :-

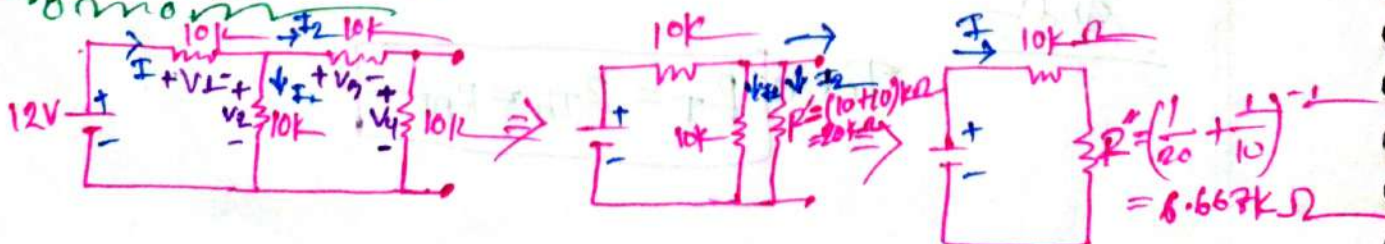


$$\therefore I = \frac{E}{R'' + R} = \frac{12V}{(6.667 + 10)k} = 0.7109mA$$


$$I_2 = \frac{R''}{R'} \times I = \frac{6.667k}{20k} \times 0.7109mA = 0.24mA$$

$$\therefore V_4 = E_{th} = V_{oc} = I_2 R_4 = 0.24mA \times 10k = 2.4V$$

$\therefore$ Thevenin Equivalent circuit

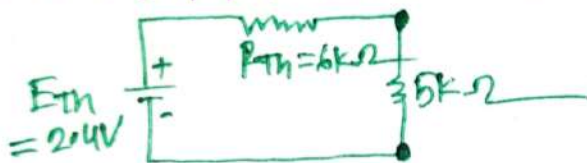

problem 0.6:-

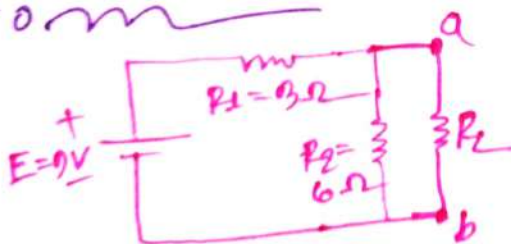

$\Rightarrow$ Find the thevenin equivalent circuit:-

$\Rightarrow$ For R_{th} :-



$$\therefore R_{th} = 2\Omega$$


TOPIC NAME : _____

DAY : _____

TIME : _____

DATE : / /


For E_{th} :-

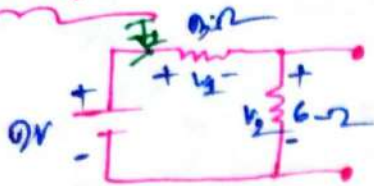


$$\therefore I_1 = \frac{E}{R_1 + R_2} = \frac{9}{6 + 3} = 1A$$

$$\therefore V_2 = V_{oc} = E_{th} = IR_2 = 1 \times 6 = 6V$$

The thevenin equivalent:-

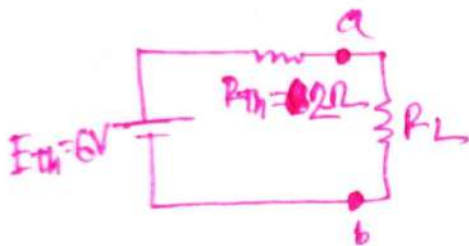


Problem: Q. 8:-

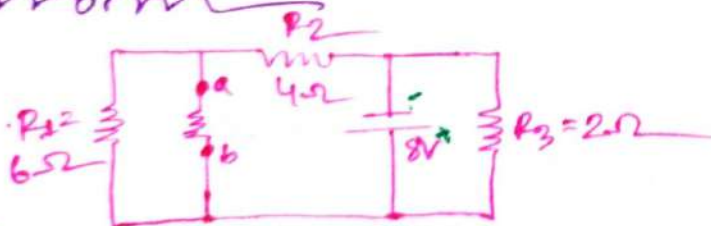


⇒ For the terminal a and b Find the thevenin equivalent.

⇒ Redraw the circuit:-

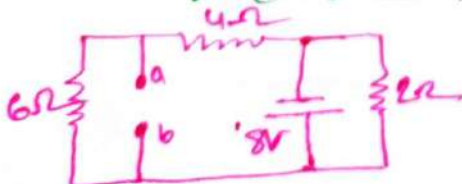

For R_{th} :-

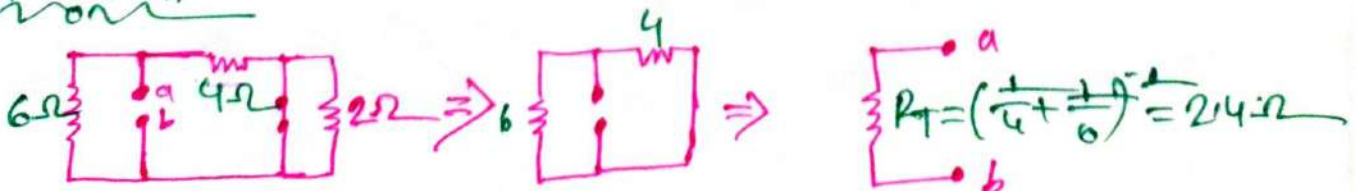




TOPIC NAME : _____

DAY : _____

TIME : _____ DATE : / /

$$\therefore R_{Th} = 2.4 \Omega$$

for E_{Th} —
~~mon~~

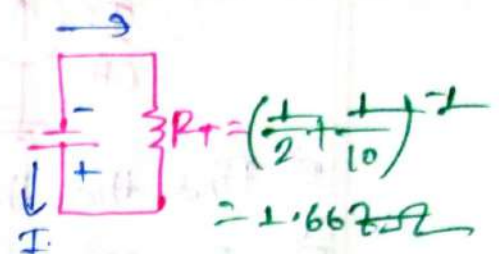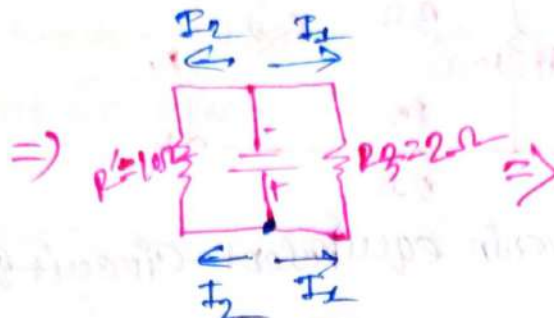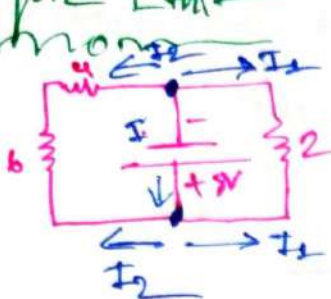


$$I = \frac{E}{R_T} = \frac{8}{1.667} = 4.8 \text{ A}$$

$$I_2 = -\frac{R}{R'} \times I = -\frac{1.667}{10} \times 4.8 \text{ A} = -0.80016 \text{ A}$$

$$V_1 = V_{oc} = I_2 R_2 = 0.800 \times 6 = 4.8 \text{ Volt}$$

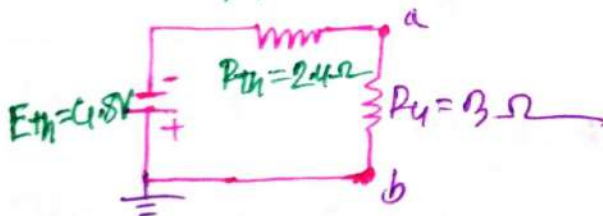$\therefore$ Thevenin equivalent: —
~~mon~~



(ii) Calculate the current passing through the R_L
 $\Rightarrow$ We have: —
~~mon~~


$$E_{Th} = 4.8 \text{ V}$$

$$R_{Th} = 2.4 \Omega$$


$$\therefore I_L = \frac{E_{Th}}{R_{Th} + R_L} = \frac{4.8}{2.4 + 3} = 0.889 \text{ A}$$

Ans: —


#problem 8 Q.3.1

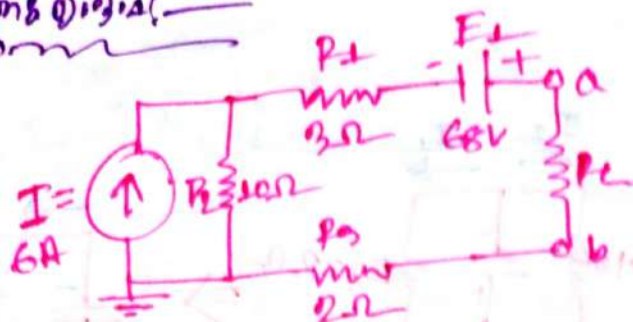

⇒ Find the thevenin equivalent circuit

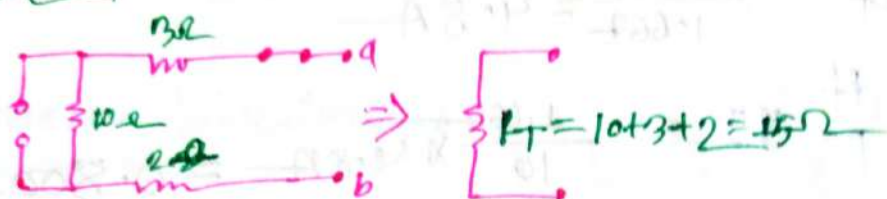⇒ For R_{th} :

$$\therefore R_{th} = 15\Omega$$

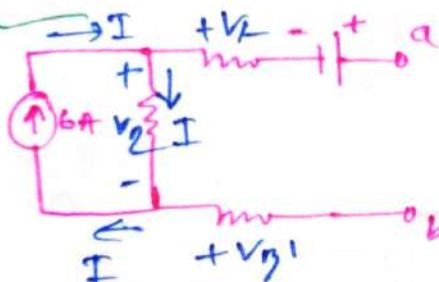⇒ for E_{th} :

$$\therefore V_2 = IR_2 = 6 \times 10 = 60V$$


Applying KVL:

$$E_{th} = V_2 + E_L$$

$$= (60 + 68)V$$

$$= 128V$$

∴ Thevenin equivalent:

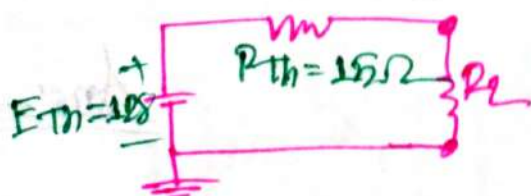

TOPIC NAME : _____


DAY : _____

TIME : _____

DATE : / /
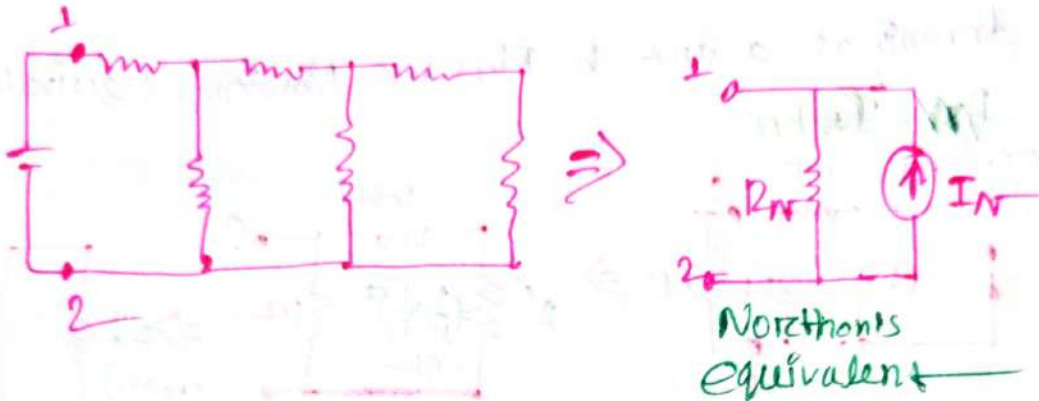
#Northon's Theorem:-

⇒ According to Northon's theorem → A parallel resistance with a current source.



R_N = Northon's equivalent resistance

I_N = Northon's equivalent current.

$$\text{Total } P_t = R_N = R_{th}$$

✱ For the two terminal presents:-

- ① The Short circuit current = I_N
- ② The Open circuit Voltage = E_{th}

✱ For R_t (R_{th} or R_N):

⇒ Sources should be deactivated that means

- ① Voltage source → Short circuit (0V)
- ② Current source → open circuit (0A)


TOPIC NAME : _____

DAY : _____

TIME : _____


DATE : / /

Problem 4

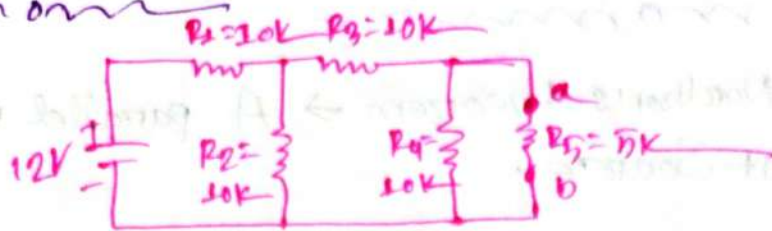


⇒ For terminal a and b Find the Norton's equivalent?

⇒ For R_N / R_{Th}

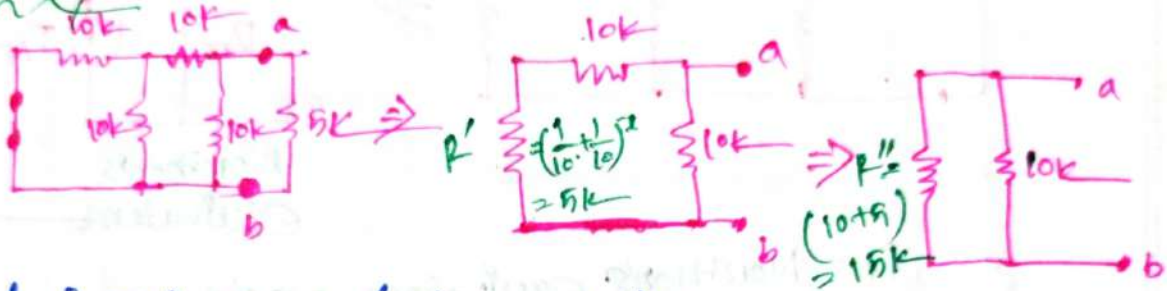

$$\therefore R_T = R_N = R_{Th} = \left(\frac{1}{15k} + \frac{1}{10k} \right)^{-1} = 6k$$

⇒ For I_N

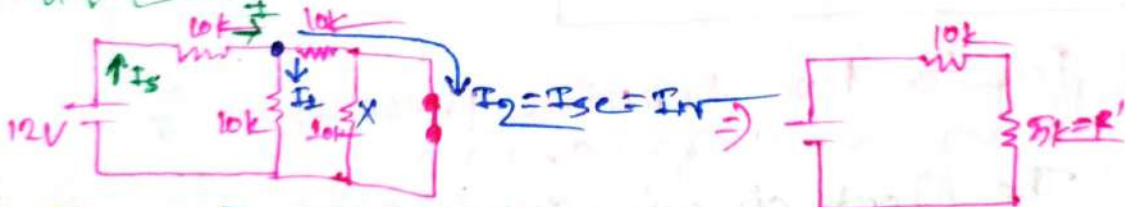


$$\begin{aligned} \therefore I_S &= \frac{E}{R_1 + R_2} \\ &= \frac{12}{10k + 10k} \\ &= \frac{12}{20k} \\ &= 0.6 \text{ mA} \end{aligned}$$


$$\begin{aligned} I_2 &= \frac{5k}{10k} \times 0.6 \text{ mA} \\ &= 0.3 \text{ mA} \end{aligned}$$

$$\therefore I_N = I_2 = I_{Sc} = 0.3 \text{ mA}$$


∴ Norton equivalent

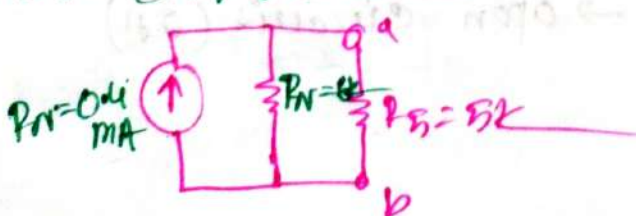

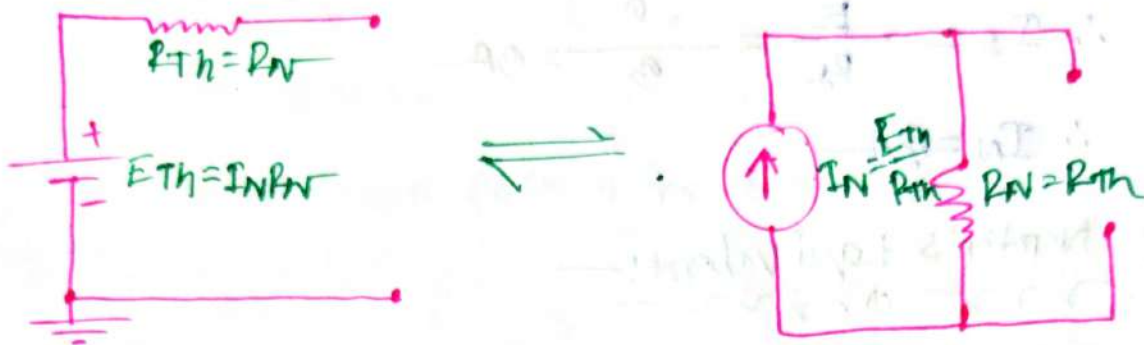Conversion Between Thevenin and Norton's Equivalent Circuit




Problem: Draw! —

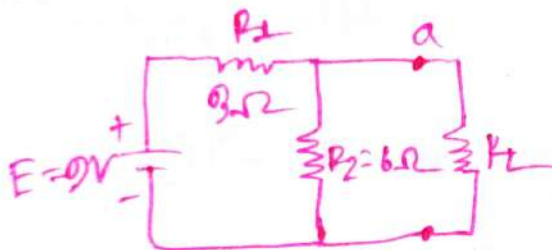


⇒ Find the Norton equivalent circuit at point a, b.

⇒ 1st draw the new circuit

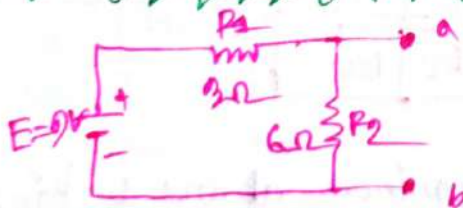


⇒ Now, for R_N : —

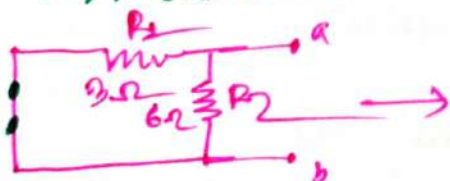

$$R_N = \left(\frac{1}{3} + \frac{1}{6} \right)^{-1} = 2\Omega$$

$$\therefore R_N = 2\Omega$$


Now, for I_N :-

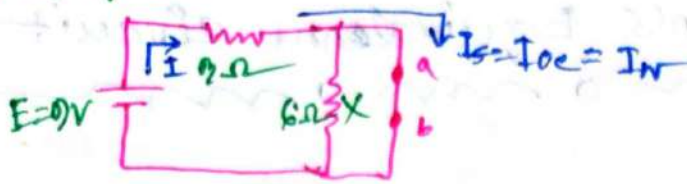


$$\therefore I_S = \frac{E}{R_2} = \frac{9}{3} = 3A$$

$$\therefore I_N = 3A$$

So, Norton's Equivalent:-

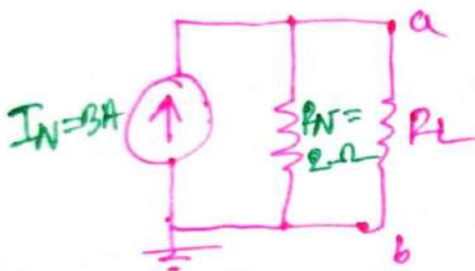


problem: 9.10:-

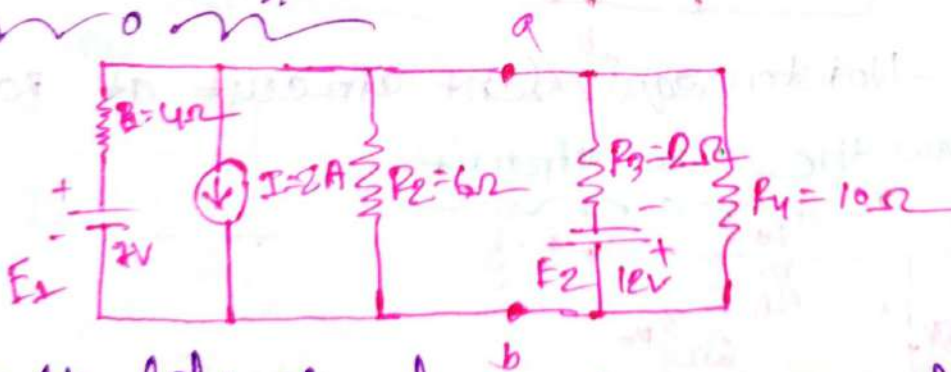

→ For the left side of terminals a and b find the Norton equivalent circuit.

→ 1st step:-

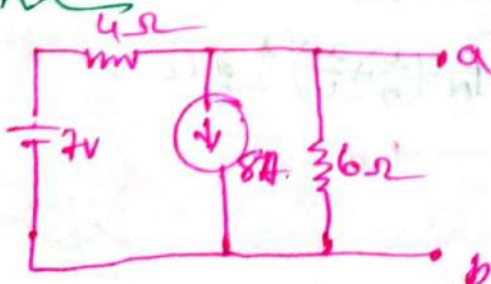


TOPIC NAME : _____

DAY : _____

TIME : _____

DATE : / /

for R_N : —


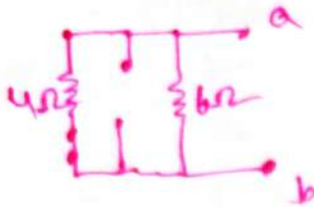


$$R_N = \left(\frac{1}{4} + \frac{1}{6} \right)^{-1} = 2.4 \Omega$$

$$\therefore R_N = 2.4 \Omega$$

for I_N : (using Super position theorem) : —


I only

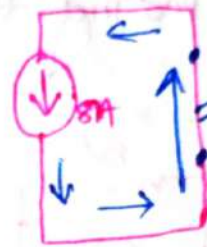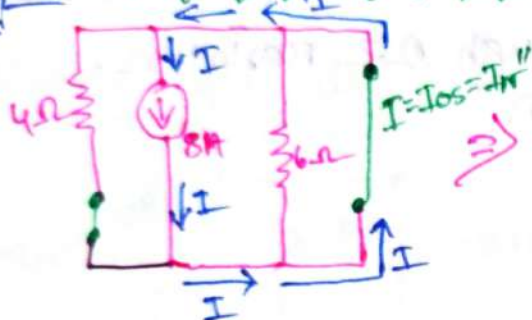

(Due to short circuit)

$$\therefore I_N' = 8A \text{ Anticlockwise}$$

E only

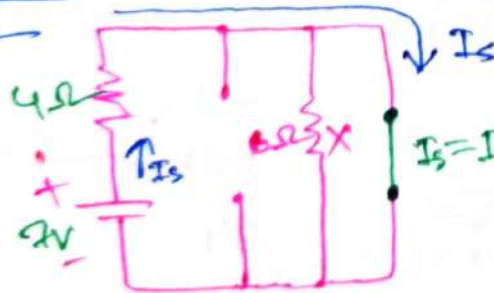

$$\therefore I_s = \frac{E}{R_s} = \frac{2}{4} = 0.5A$$


$$\therefore I_N'' = 0.5A \text{ clockwise}$$

So


$$I_N = I_N' - I_N'' = (8 - 0.5)A = 7.5A$$

So

Norton equivalent : —

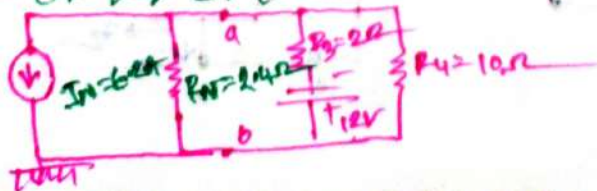


problems 9, 12:

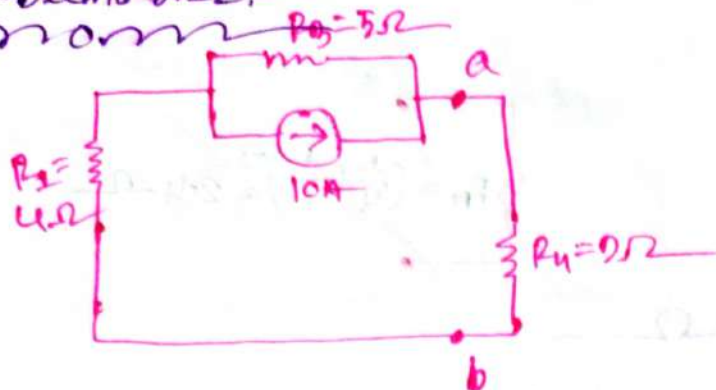


- ① for the terminal a & b Find the Norton equivalent
- ② Current passing through 2Ω resistor.

①


1st step!

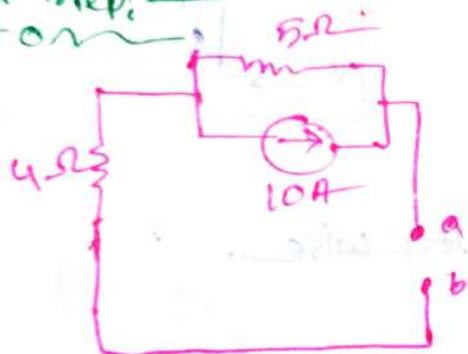

For R_N !

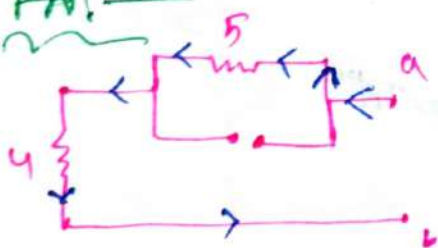


$\Rightarrow$

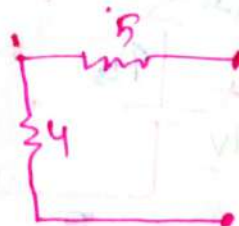


$$\therefore R_N = 5 + 4 = 9\Omega$$


for I_N :-

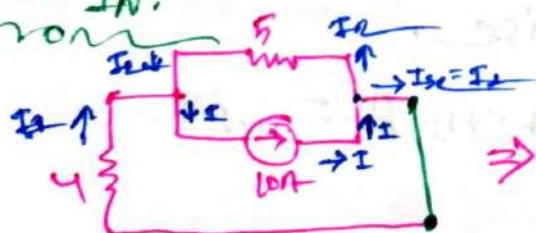

$\Rightarrow$

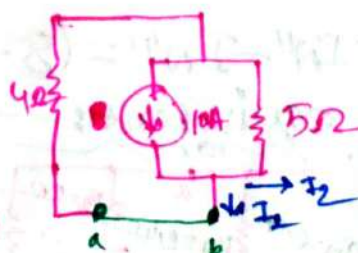

$\Rightarrow$

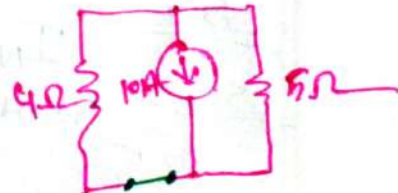

TOPIC NAME : _____

DAY : _____

TIME : _____

DATE : / /

$$\therefore R_T = \left(\frac{1}{5} + \frac{1}{4} \right)^{-1}$$

$$= 2.222 \Omega$$


$$I_1 = \frac{R_T}{R_1} \times I$$

$$= \frac{2.222}{4} \times 10$$

$$= 5.555 A$$

$$\therefore I_1 = I_o = I_N = 5.555 A$$

So, Norton Equivalent:-

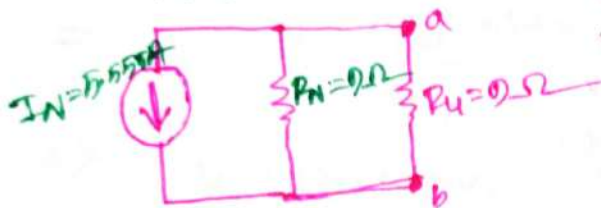

$$\therefore R_T = \left(\frac{1}{R_N} + \frac{1}{R_L} \right)^{-1} = \left(\frac{1}{0} + \frac{1}{0} \right)^{-1} = 4.5 \Omega$$

$$\therefore I_{R_L} = \frac{R_T}{R_L} \times I_N$$

$$= \frac{4.5}{0} \times 5.555$$

$$= 2.777 A$$

Ans:-


TOPIC NAME : _____

DAY : _____

TIME : _____


DATE : / /

problem 28:—

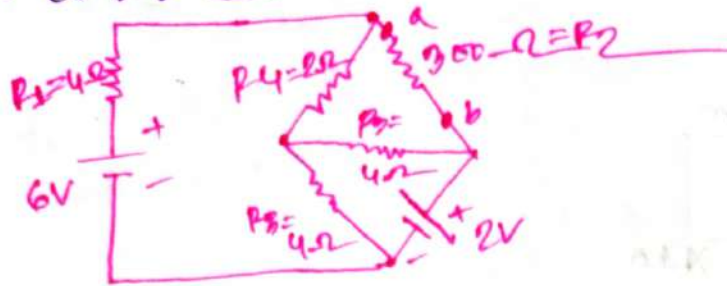


⇒ For the terminals a and b find the Norton equivalent.

⇒ 1st step:—

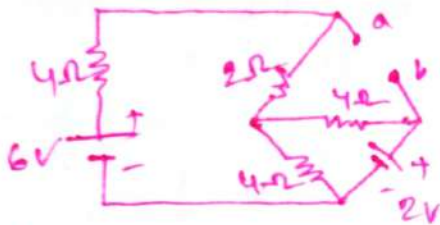


⇒ for R_N :—

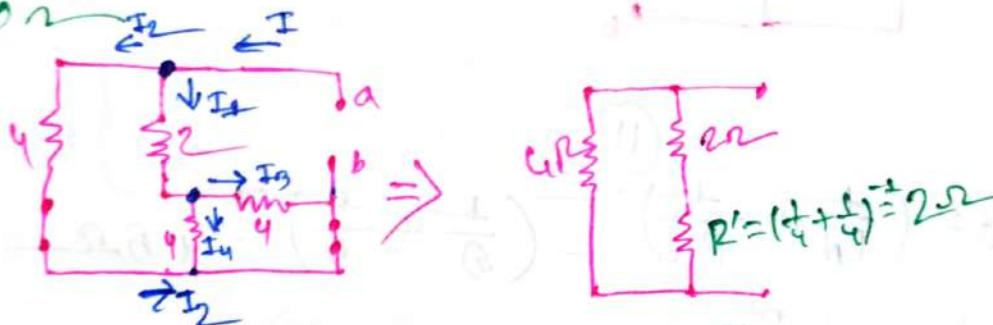

$$\therefore R_N = \left(\frac{1}{4} + \frac{1}{4} \right)^{-1} = 2\Omega = R_N$$

⇒ for I_N : Using Superposition theorem:—

For E_1 only:—

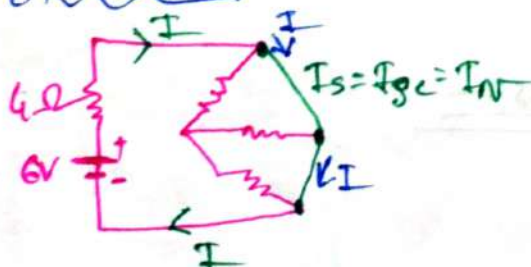

$$I_S = I_{Sc} = I_N' = \frac{E}{R_T} = \frac{6}{4} = 1.5A \text{ clockwise.}$$


TOPIC NAME : _____

DAY : _____

TIME : _____

DATE : / /

For E_2 only! —
 ~~~~~

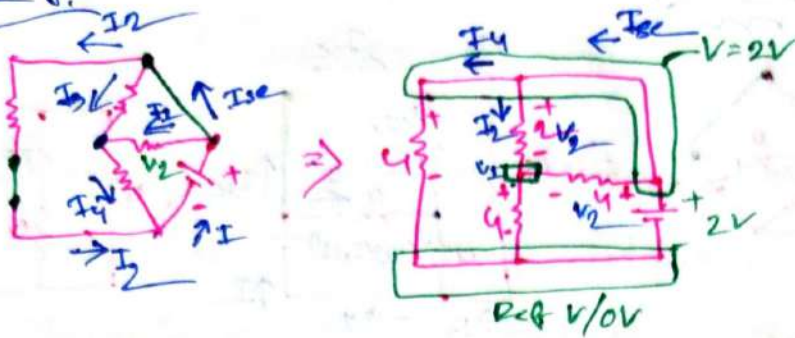

$$\therefore I_4 = \frac{2-0}{4} = 0.5A$$

$$V_1 \Rightarrow \frac{V_1-0}{4} + \frac{V_1-2}{2} + \frac{V_1-2}{4} = 0$$

$$\Rightarrow \frac{V_1 + 2(V_1-2) + V_1-2}{4} = 0$$

$$\Rightarrow V_1 + 2V_1 - 4 + V_1 - 2 = 0$$

$$\Rightarrow 4V_1 = 6$$

$$\therefore V_1 = \frac{6}{4} = 1.5 \text{ Volt}$$


So,  $V_2 = (2 - 1.5) = 0.5 \text{ Volt}$

$$\therefore I_2 = \frac{V_2}{R_4} = \frac{0.5}{2} = 0.25A$$

$$I_N'' \therefore I_{se} = I_4 + I_2 = (0.5 + 0.25) = 0.75A \text{ Anticlockwise}$$

$$\begin{aligned} \therefore I_N &= I_N' - I_N'' \\ &= (1.5 - 0.75) \\ &= 0.75A \end{aligned}$$

So, the Norton Equivalent: —  
 ~~~~~

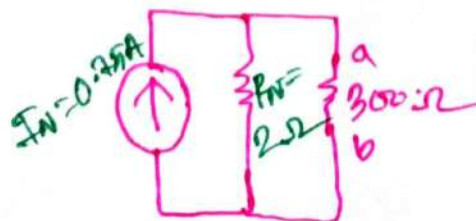


Maximum Power Transfer

Theorem:

For thevenin

⇒ A load will receive/consume/absorb maximum power from a network when its resistance is exactly equal to the Thevenin resistance for the network applied to the load.

$$R_L = R_{Th}$$

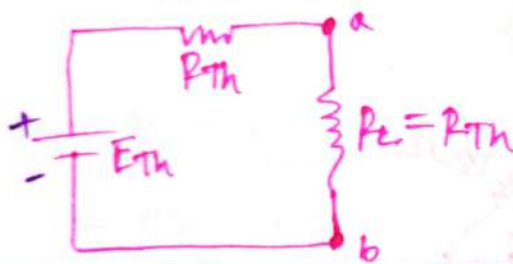

$$\therefore I_L = \frac{E_{Th}}{R_{Th} + R_L} = \frac{E_{Th}}{R_{Th} + R_{Th}} = \frac{E_{Th}}{2R_{Th}}$$


$$\therefore \text{Power } P_{L_{max}} = I_L^2 R_L = \frac{(E_{Th})^2}{(2R_{Th})^2} \times R_{Th} = \frac{E_{Th}^2 \times R_{Th}}{4R_{Th}^2}$$

$$\therefore P_{L_{max}} = \frac{E_{Th}^2}{4R_{Th}}$$

For Norton:-


⇒ Maximum power will be delivered to the load when

$$R_L = R_N$$

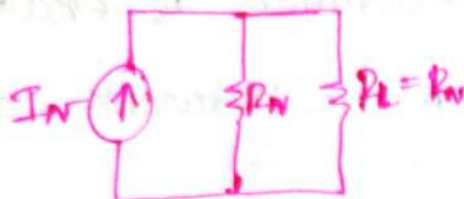


$$\therefore P_{\text{max}} = \frac{I_N^2 R_N}{4}$$

problem: 0.6.1:-

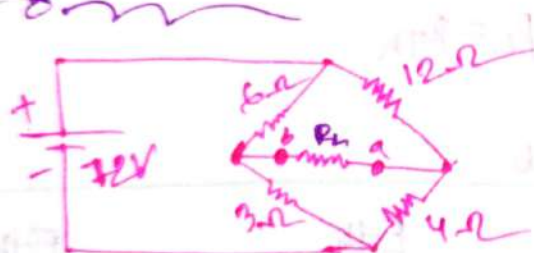

⇒ Find the value of R_L for maximum power to R_L and determine the maximum power to R_L

⇒ 1st Step:-

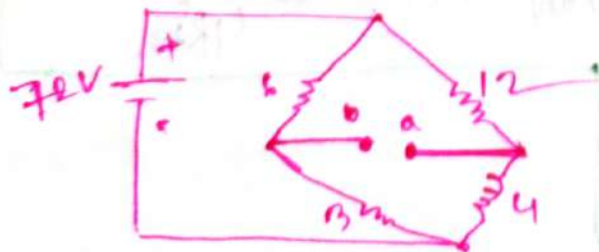

For R_{Th} :-



TOPIC NAME : _____


DAY : _____

TIME : _____

DATE : / /

$$\therefore R_{Th} = 3 + 2 = 5 \Omega$$

For E_{Th} :—

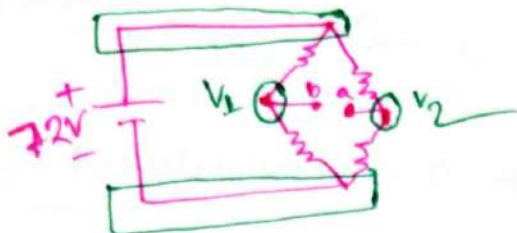

$$\frac{V_1 - 72}{6} + \frac{V_2 - 0}{3} = 0$$

$$\frac{V_1 - 72 + 2V_2}{6} = 0$$

$$2V_1 - 72 = 0$$

$$V_1 = 24 \text{ Volt}$$

$$\frac{V_2 - 72}{12} + \frac{V_2 - 0}{4} = 0$$

$$\frac{V_2 - 72 + 3V_2}{12} = 0$$

$$\therefore 4V_2 = 72$$


$$V_2 = 18 \text{ Volt}$$

$$\therefore E_{Th} = V_1 - V_2$$

$$= 24 - 18$$

$$= 6 \text{ Volt}$$

$\therefore$ thevenin equivalent :—

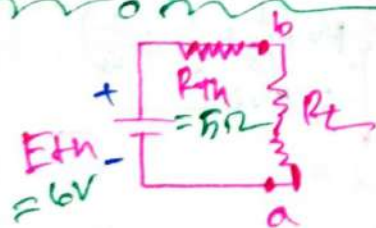

$\therefore R_L = R_{Th} = 5 \Omega$ for maximum power.


$$\therefore P_{max} = \frac{E_{Th}^2}{4R_{Th}}$$

$$= \frac{6^2}{4 \times 5}$$

$$= 1.8 \text{ W}$$


Ans. —

Problem 4.6.2

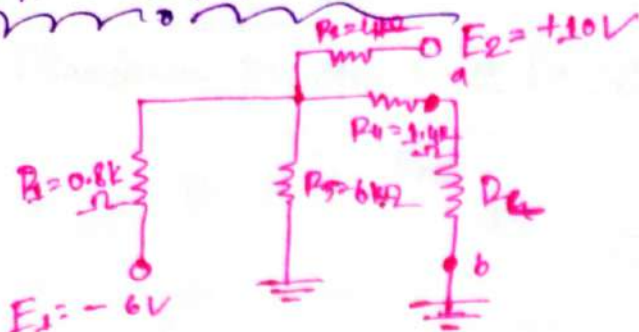


⇒ Find the value of R_L for maximum power to R_L and determine the maximum power to R_L

⇒ 1st Step

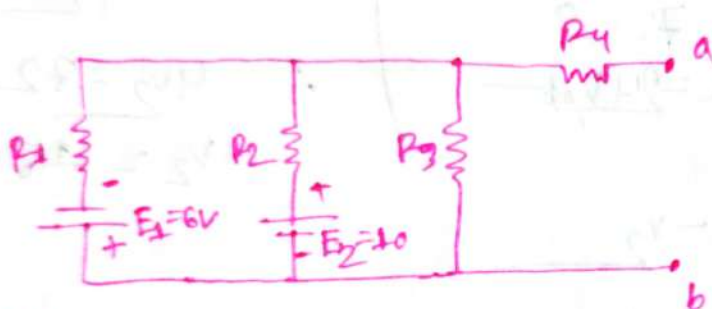

⇒ for R_{th}

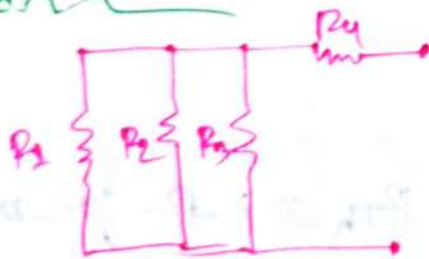


⇒

$$R' = \left(\frac{1}{0.8} + \frac{1}{4} + \frac{1}{6} \right)^{-1} = 0.6k$$

$$\therefore R_{th} = 0.6k + 1.4k = 2k$$

⇒ for E_{th} using superposition principle

E_1 only

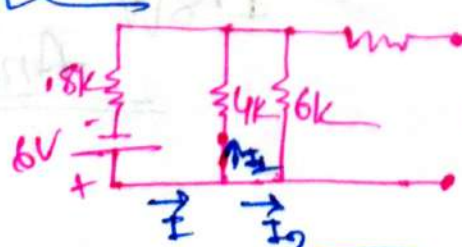

$$R' = \left(\frac{1}{4} + \frac{1}{6} \right)^{-1} = 2.4k$$

TOPIC NAME : _____

DAY : _____

TIME : _____



DATE : / /

$$I = \frac{E}{R' + R_2} = \frac{6V}{(2.4 + 0.8)k} = 1.875mA$$

$$I_2 = \frac{R'}{R_3} \times I = \frac{2.4k}{6k} \times 1.875mA = 0.75mA$$

$$\therefore I_2' = \text{Anticlockwise} = 0.75mA$$

For E_2 only:-

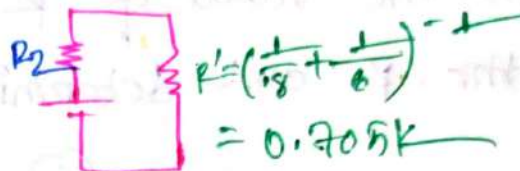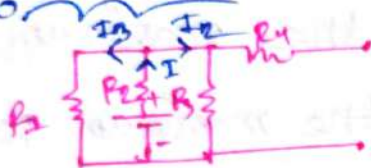

$$\therefore I = \frac{E}{R' + R_2} = \frac{10}{(0.705k + 4)k} = 2.125mA$$

$$I_2'' = \frac{R'}{R_3} \times I = \frac{0.705k}{6k} \times 2.125mA = 0.249mA$$


$$I_2 = \text{Clockwise} = 0.249mA$$

$$\therefore \text{Effective } I_2 = (I_2' - I_2'') = (0.75 - 0.249)mA$$

$$\therefore \text{Voltage } V_3 = V_C = R_{TH} = I_2 \times R_3 = 0.5mA$$

$$= 0.5mA \times 6k = 3V$$

Thermin Equivalent:-

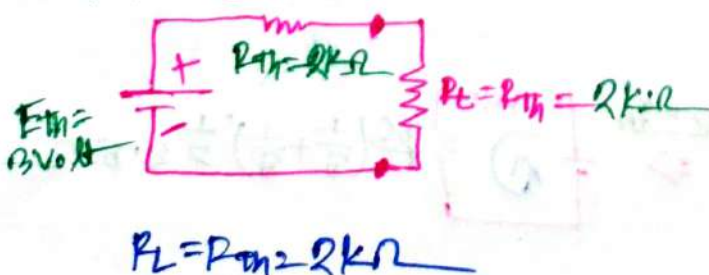


$$\therefore P_{Lmax} = \frac{E_{Th}^2}{4R_{Th}} = \frac{3^2}{(4 \times 2)k} = 1.125mW$$

TOPIC NAME : _____

DAY : _____

TIME : _____ DATE : / /


Problem: Q.5.21

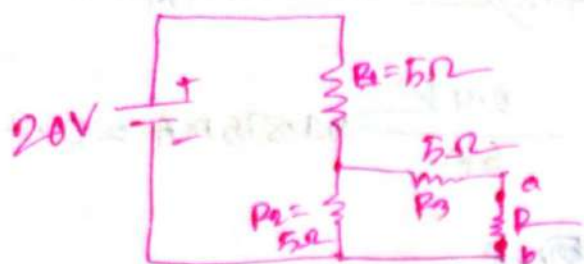


- ① Find the Norton equivalent of terminal a and b.
- ② Find the value of R for the maximum power to R and determine the maximum power to R .

①

1st Step!

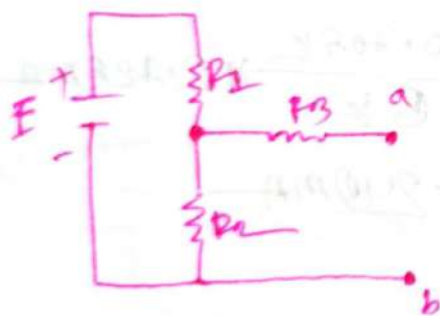


For $R_{th} = R_N$:

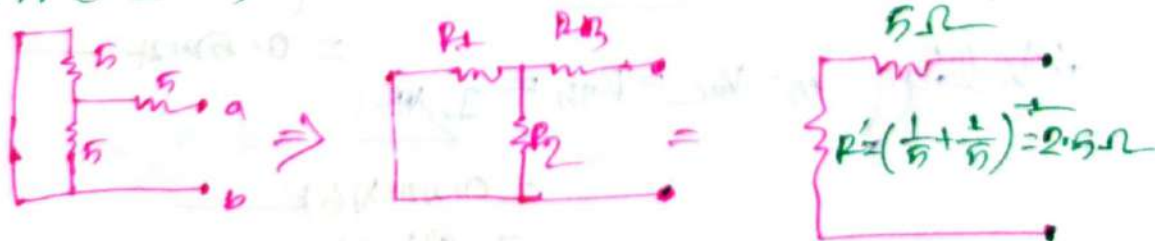

$$\therefore R_N = 5 + 2.5 = 7.5 \Omega$$

For I_N :

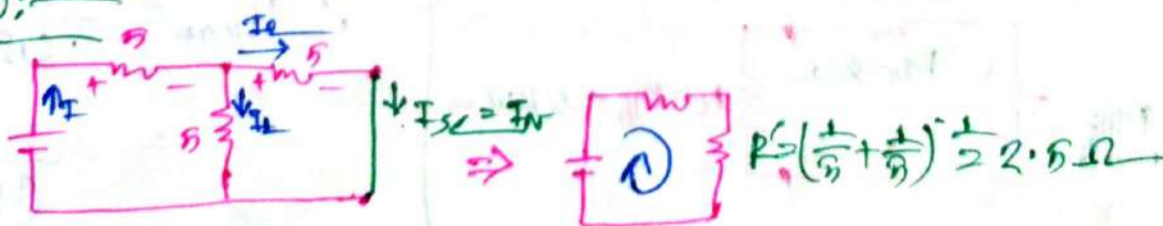

TOPIC NAME : _____

DAY : _____

TIME : _____ DATE : / /


$$1. R_T = 2.5 + 5 = 7.5 \Omega$$

$$\therefore I_s = \frac{E}{R_T} = \frac{20}{7.5} = 2.667 \text{ A}$$

$$\therefore I_2 = \frac{R'}{R_3} = \frac{2.5}{5} \times 2.667 = 1.333 \text{ A}$$

$$\therefore I_2 = I_{sc} = I_N = 1.333 \text{ A}$$

Norton equivalent:-

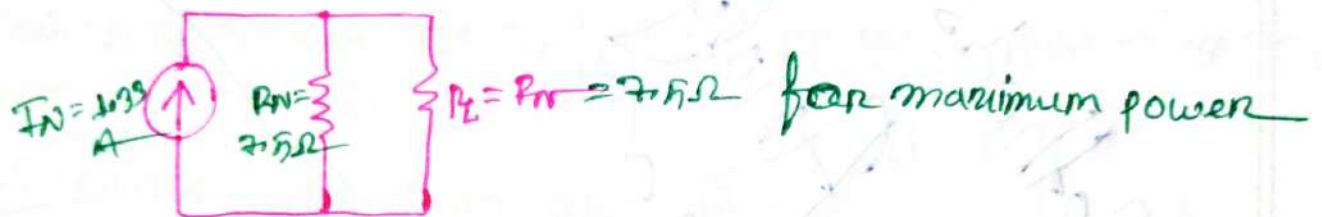

$$\therefore R_L = R_N = 7.5 \Omega$$

$$\begin{aligned} \therefore P_{\text{max}} &= \frac{I_N^2 R_N}{4} \\ &= \frac{(1.333)^2 \times 7.5}{4} \\ &= 0.333 \text{ W} \end{aligned}$$

Ans:-

TOPIC NAME : _____

DAY : _____

TIME : _____ DATE : / /


Methods of Analysis Geoog

DAY: _____

TIME : DATE : / /

KVL for mesh/Loop Analysis:-

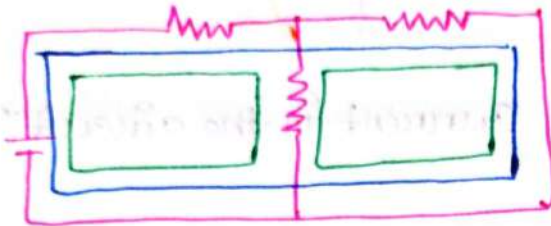$\Rightarrow$ my 2nd diff circuit is close path.



→ ଉଦାହରଣ ସାହାଯ୍ୟ, - ଡିଜିଟାଲ circuit ଯେ ଖୋଲି ଦିଅନ୍ତୁ ୩ଟି

→ Mesh-২টি circuit-এ যে মূল্যটা পাওয়া গিয়েছিল তাই -
- কোনা মূল্য কনট্রোল করে না।

$\therefore$ जाल - (grid/mesh) - 2065 2 टि.

Notes—

⇒ All meshes are loops but not all loops are meshes.

For mesh Analysis:-

1st step:-

Detect all meshes.

2nd step:- Assume Current for each meshes.


3rd step:- Assume that, either all current in clockwise or all current in anticlockwise.

4th Step:- Now, label the current as $I_1, I_2, \dots$ etc

5th step: - Write equation for each mesh. Num of eq = Num of meshes
6th step: - Then solve it.

6th step: - Then solve the equation

Problem:-

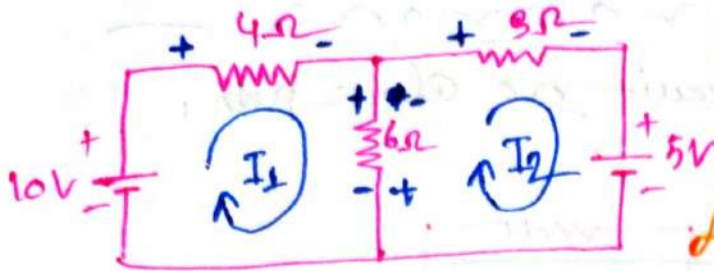

Note:-

⇒ When we are writing mesh 1's equation $I_1 \supset I_2$

⇒ When we are writing mesh 2's equation $I_2 \supset I_1$

⇒ Determine the mesh current in the circuit?

⇒ for I_1 :-

$$-10 + I_1 \cdot 4 + (I_1 - I_2) \cdot 6 = 0$$

$$-10 + 4I_1 + 6I_1 - 6I_2 = 0$$

$$10I_1 - 6I_2 = 10 \quad \text{--- (1)}$$

⇒ for I_2 :-

$$3I_2 + 5 + 6(I_2 - I_1) = 0$$

$$3I_2 + 5 + 6I_2 - 6I_1 = 0$$

$$\therefore -6I_1 + 9I_2 = -5 \quad \text{--- (2)}$$

$$\textcircled{1} \times 6 \quad \text{---} \quad \textcircled{2} \times 10 \Rightarrow$$

$$60I_1 - 36I_2 = 60$$

$$-60I_1 + 90I_2 = -50$$

$$54I_2 = 10$$

$$\therefore I_2 = 0.185A$$

$$\therefore I_1 = \frac{10 + I_2 \times 6}{10} = \frac{10 + 6 \times 0.185}{10} = 1.11A$$

$$\therefore I_1 = 1.11A$$

$$I_2 = 0.185A$$

① + ② $\times 4 \Rightarrow$
non

$$4I_1 + 9I_2 = 5$$

$$-4I_1 + 4I_2 = 4$$


$$\hline 7I_2 = 9$$

$$\therefore I_2 = 1.285 \text{ A}$$

$$\therefore I_1 = 0.285 \text{ A}$$

Ans:—

problem:—
non

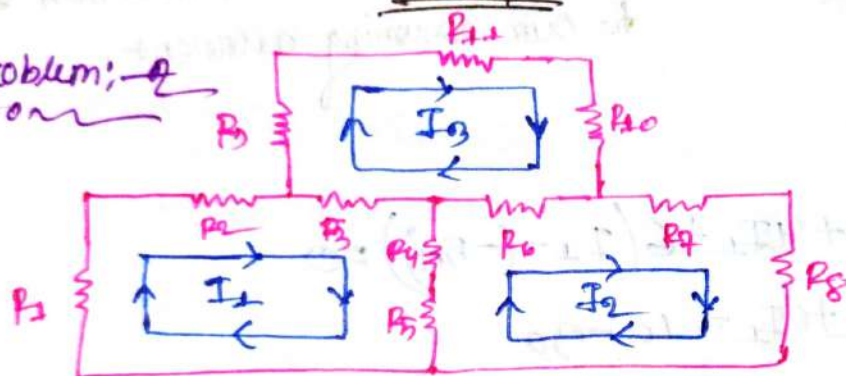

$\Rightarrow$ Write the loop equation for the following circuit
 $\Rightarrow$ For I_1 :—
non

$$I_1 R_1 + I_1 R_2 + (I_1 - I_3) R_3 + (I_1 - I_2) R_4 + (I_1 - I_2) R_5 = 0$$

$$\Rightarrow I_1 R_1 + I_1 R_2 + I_1 R_3 + I_1 R_4 - I_3 R_3 - I_2 R_4 + I_1 R_5 - I_2 R_5 = 0$$

$$\Rightarrow I_1 (R_1 + R_2 + R_3 + R_4 + R_5) - I_2 (R_4 + R_5) - I_3 R_3 = 0 \quad \text{--- (1)}$$

$\Rightarrow$ For I_2 :—
non

$$I_2 R_7 + I_2 R_8 + (I_2 - I_1) R_9 + (I_2 - I_1) R_4 + (I_2 - I_3) R_6 = 0$$

$$I_2 R_7 + I_2 R_8 + I_2 R_9 - I_1 R_9 + I_2 R_4 - I_1 R_4 + I_2 R_6 - I_3 R_6 = 0$$

$$I_2 (R_7 + R_8 + R_9 + R_4 + R_6) - I_1 (R_4 + R_9) - I_3 R_6 = 0 \quad \text{--- (2)}$$

TOPIC NAME : _____

DAY : _____

TIME : _____


DATE : / /

For I_3 :-
non

$$I_3 R_9 + I_3 R_{10} + I_3 R_{11} + (I_3 - I_2) R_6 + (I_3 - I_1) R_3 = 0$$

$$I_3 (R_9 + R_{10} + R_{11} + R_6 + R_3) - I_2 R_6 - I_1 R_3 = 0 \quad \text{--- (ii)}$$

problem:-
non

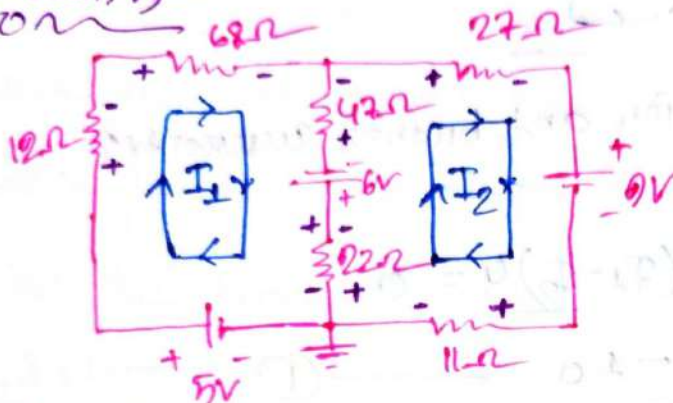

Find the current I_1 and I_2

For I_1 :-
non

$$-5 + 12I_1 + 68I_1 + (I_1 - I_2)47 - 6 + (I_1 - I_2)22 = 0$$

$$-5 + 12I_1 + 68I_1 + 47I_1 - 47I_2 - 6 + 22I_1 - 22I_2 = 0$$

$$I_1(12 + 68 + 47 + 22) - I_2(47 + 22) = 11$$

$$140I_1 - 69I_2 = 11 \quad \text{--- (i)}$$

For I_2 :-
non

$$22I_2 + 0 + 11I_2 + (I_2 - I_1)22 + 6 + (I_2 - I_1)47 = 0$$

$$I_2(22 + 11 + 22 + 47) - I_1(22 + 47) = -15$$


$$-69I_1 + 102I_2 = -15 \quad \text{--- (ii)}$$

Now Solve the equation:-

$$\therefore I_1 = 0.0106A$$

$$I_2 = -0.1310A$$

Problems 8.13:—

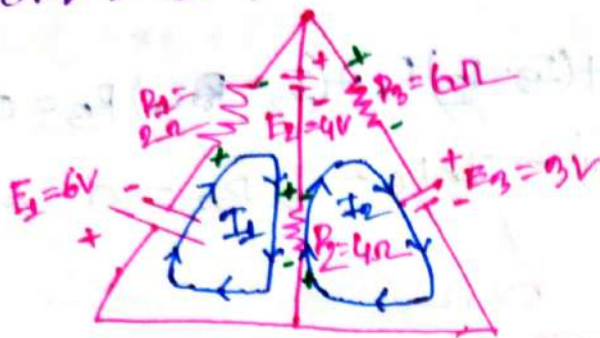

⇒ Find the mesh equation and branch currents?

⇒ For I_1 :—

$$6 + 2I_1 + 4 + (I_1 - I_2)4 = 0$$

$$6I_1 - 4I_2 = -10 \quad \text{--- (1)}$$

⇒ For I_2 :—

$$3 + 4(I_2 - I_1) - 4 + 6I_2 = 0$$

$$-4I_1 + 10I_2 = 1 \quad \text{--- (2)}$$

① × 4 + ② × 6 =

$$24I_1 - 16I_2 = -40$$


$$-24I_1 + 60I_2 = 6$$

$$44I_2 = -34$$

$$\therefore I_2 = -0.772 \text{ A}$$

$$\therefore I_1 = -2.18 \text{ A}$$
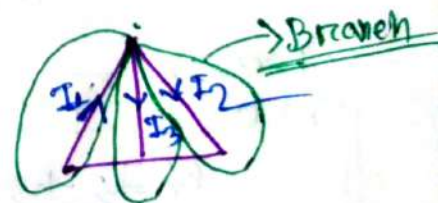
$$\therefore I_3(I_1 - I_2) = (-2.18 + 0.772) = -1.4072 \text{ A}$$




TOPIC NAME : _____

DAY : _____

TIME : _____

DATE : / /

Problem: _____
non

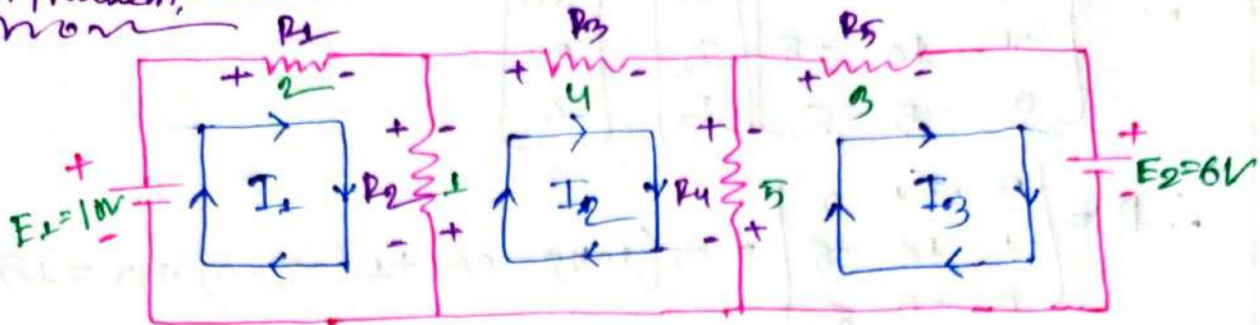

- ① Write the mesh equation for the each loop of the networks.
- ② Solve for the loop current.
- ③ Find the current of each branch.

⇒ For I_1 : ——— ①
non

$$-10 + 2I_1 + (I_1 - I_2) = 0$$

$$3I_1 - I_2 = 10 \quad \text{————— ①}$$

⇒ For I_2 : ———
non

$$(I_2 - I_1) + 4I_2 + (I_2 - I_3)5 = 0$$

$$-I_1 + 10I_2 - 5I_3 = 0 \quad \text{————— ②}$$

⇒ For I_3 : ———
non

$$(I_3 - I_2)5 + 3I_3 + 6 = 0$$

$$8I_3 - 5I_2 = -6 \quad \text{————— ③}$$

we have: ———
non

$$3I_1 - I_2 = 10V \quad \text{————— ①}$$

$$-I_1 + 10I_2 - 5I_3 = 0V \quad \text{————— ②}$$

$$-5I_2 + 8I_3 = -6V \quad \text{————— ③}$$

TOPIC NAME : _____

DAY : _____

TIME : _____ DATE : / /

$$\therefore \begin{bmatrix} 3 & -1 & 0 \\ -1 & 10 & -5 \\ 0 & -5 & 8 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 10 \\ 0 \\ -6 \end{bmatrix}$$

$$\therefore D = \begin{vmatrix} 3 & -1 & 0 \\ -1 & 10 & -5 \\ 0 & -5 & 8 \end{vmatrix} = 3(10 \times 8 - 25) + 1(-8 - 0) + 0 = 157$$

$$D_1 = \begin{vmatrix} 10 & -1 & 0 \\ 0 & 10 & -5 \\ -6 & -5 & 8 \end{vmatrix} = 10(80 - 25) + 1(0 - 30) + 0 = 520$$

$$D_2 = \begin{vmatrix} 3 & 10 & 0 \\ -1 & 0 & -5 \\ 0 & -6 & 8 \end{vmatrix} = 3(0 - 30) - 10(-8 + 0) + 0 = -10$$

$$D_3 = \begin{vmatrix} 3 & -1 & 10 \\ -1 & 10 & 0 \\ 0 & -5 & -6 \end{vmatrix} = 3(-60) + 1(6 - 0) + 10(5 - 0) = -124$$

$$\therefore I_1 = \frac{D_1}{D} = \frac{520}{157} = 3.31 \text{ A}$$

$$I_2 = \frac{D_2}{D} = \frac{-10}{157} = -0.0636 \text{ A}$$

$$I_3 = \frac{D_3}{D} = \frac{-124}{157} = -0.7898 \text{ A}$$

(III)

We have:
non

$$I_1 = 3.31 \text{ A}$$


$$I_2 = -0.0636 \text{ A}$$

$$I_3 = -0.7898 \text{ A}$$

$$\therefore I_4 = (I_1 - I_2) \\ = (3.31 + 0.0636 \text{ A}) \\ = 3.403 \text{ A}$$

$$I_5 = I_2 - I_3 \\ = (-0.0636 + 0.7898) \\ = 0.7262 \text{ A}$$

problem 41 —
mom

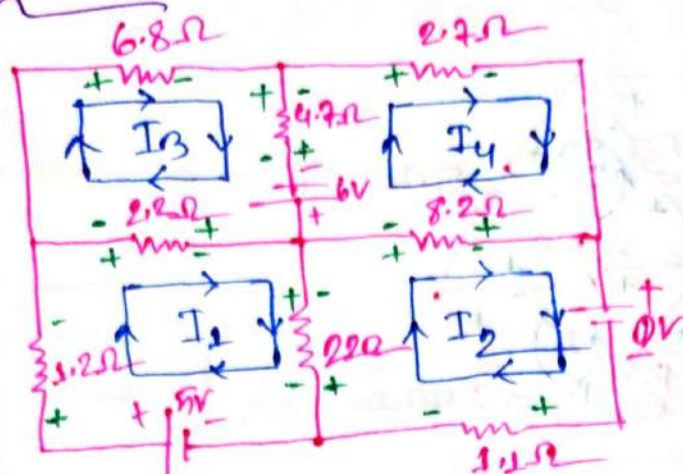

⇒ write the mesh equation for the every branch! —

⇒ For I_1 ! —
mom

$$-5 + 1.2I_1 + (I_1 - I_3)2.2 + (I_1 - I_2)22 = 0$$

$$I_1(1.2 + 2.2 + 22) - 2.2I_3 - 22I_2 = 0 + 5$$

$$25.4I_1 - 22I_2 - 2.2I_3 = 5 \quad \text{--- (I)}$$

⇒ For I_2 ! —
mom

$$0 + 1.1I_2 + (I_2 - I_1)22 + 8.2(I_2 - I_4) = 0$$

$$I_2(1.1 + 22 + 8.2) - 22I_1 - 8.2I_4 = -0$$

$$-22I_1 + 31.3I_2 - 8.2I_4 = -0 \quad \text{--- (II)}$$

⇒ For I_3 ! —
mom

$$6.8I_3 + 4.7(I_3 - I_4) - 6 + 2.2(I_3 - I_1) = 0$$

$$-2.2I_1 + 13.7I_3 - 4.7I_4 = 6 \quad \text{--- (III)}$$


⇒ For I_4 ! —
mom

$$2.7I_4 + 8.2(I_4 - I_2) + 6 + 4.7(I_4 - I_3) = 0$$

$$-8.2I_2 - 4.7I_3 + 15.6I_4 = -6 \quad \text{--- (IV)}$$

Ans:

problems 5(—
mon

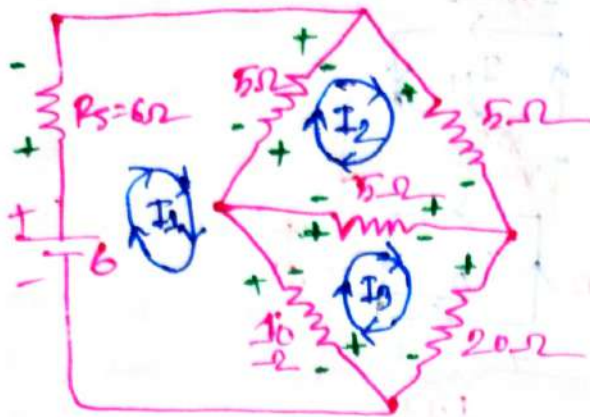

⇒ Write the Loop equation!—
mon

⇒ For I_1 !—
mon

$$-6 + 6I_1 + 5(I_1 - I_2) + 10(I_1 - I_3) = 0$$

$$I_1(6 + 5 + 10) - 5I_2 - 10I_3 = 6$$

$$21I_1 - 5I_2 - 10I_3 = 6 \quad \text{--- (i)}$$

⇒ For I_2 !—
mon

$$5I_2 + 5(I_2 - I_3) + 5(I_2 - I_1) = 0$$

$$-5I_1 + 15I_2 - 5I_3 = 0 \quad \text{--- (ii)}$$

⇒ for I_3 !—
mon

$$20I_3 + 10(I_3 - I_1) + 5(I_3 - I_2) = 0$$

$$-10I_1 - 5I_2 + 35I_3 = 0 \quad \text{--- (iii)}$$

TOPIC NAME : _____

DAY : _____

TIME : _____

DATE : / /


Nodal Analysis:

Branch:

⇒ Any element of a circuit

Node:

⇒ Meeting point of two or more branches.

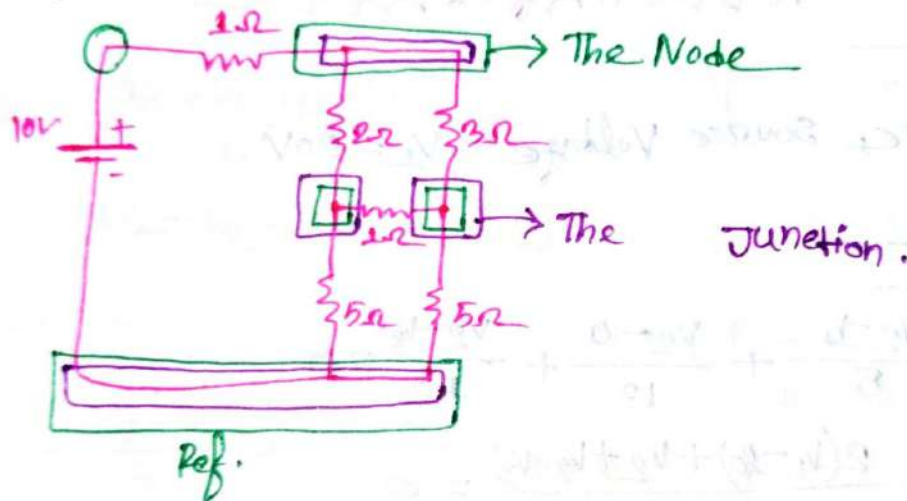

Junction:

⇒ Meeting point of three or more branches


For Nodal Analysis:

Step 1: — Identify each node with labelling.

Step 2: — Write equation for each node using KCL.

Step 3: — Solve the equation to find the unknown node voltage.

#problem 1:-
mon

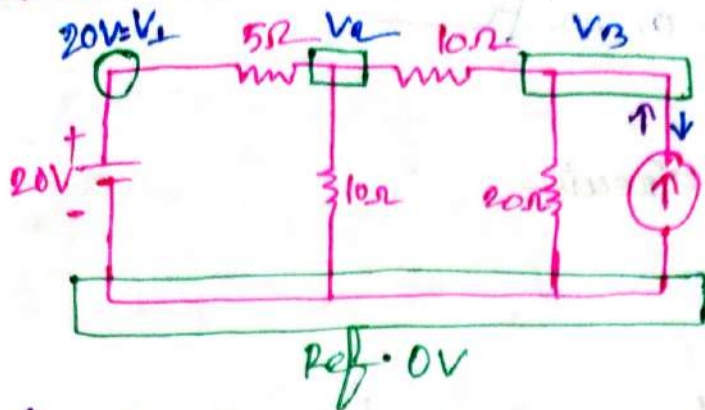

Notes:-

- ① Assumption: Current leaves from node.
- ② Leaving Current is positive
- ③ Entering Current is negative
- ④ Node Voltage is highest in his own node equation.

⇒ Find the V_2 , V_3 using node analysis:-
mon

⇒ For V_1 :-
mon

here, source voltage = $V_1 = 20V$

⇒ For V_2 :-
mon

$$\Rightarrow \frac{V_2 - V_1}{5} + \frac{V_2 - 0}{10} + \frac{V_2 - V_3}{10} = 0$$

$$\Rightarrow \frac{2(V_2 - 20) + V_2 + V_2 - V_3}{10} = 0$$

$$\therefore 2V_2 + V_2 + V_2 - V_3 = 40$$

$$4V_2 - V_3 = 40 \quad \text{--- (1)}$$

⇒ For V_3 :-
mon

$$\frac{V_3 - V_2}{10} + \frac{V_3 - 0}{20} - 5 = 0$$

$$\Rightarrow \frac{2(V_3 - V_2) + V_3 - 100}{20} = 0$$

$$\Rightarrow 2V_3 + V_3 - 2V_2 = 100$$

$$\Rightarrow -2V_2 + 3V_3 = 100 \quad \text{--- (2)}$$

Solve the equation:-
mon


$$\frac{V_2}{V_3} = \frac{12}{48}$$

TOPIC NAME : _____

DAY : _____

TIME : _____ DATE : / /

Problem 2

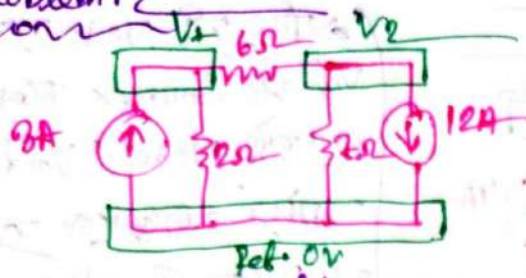

⇒ Find the Node Voltages:—

⇒ For V_1 :—

$$-3 + \frac{V_1 - V_2}{6} + \frac{V_1 - 0}{2} = 0$$

$$\Rightarrow \frac{-18 + V_1 - V_2 + 3V_1}{6} = 0$$

$$\therefore 4V_1 - V_2 = 18 \quad \text{--- (1)}$$

⇒ For V_2 :—

$$\frac{V_2 - V_1}{6} + \frac{V_2 - 0}{2} + 12 = 0$$

$$\Rightarrow \frac{2(V_2 - V_1) + 6V_2 + 504}{42} = 0$$

$$\Rightarrow 2V_2 - 2V_1 + 6V_2 = -504$$


$$\Rightarrow -2V_1 + 8V_2 = -504 \quad \text{--- (2)}$$

⇒ Now Solve the equations:—

$$\therefore V_1 = -6 \text{ Volt}$$

$$V_2 = -42 \text{ Volt}$$


Special Case:-

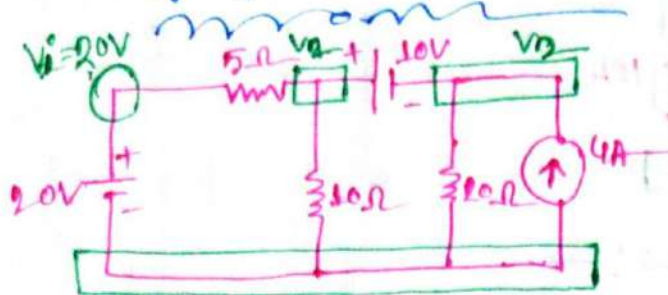

ଯଦି କୌଣସି Node ଉପରେ Voltage Source ଥାଏ ତାହାକୁ SuperNode କୁହାଯାଏ।
ଏହି SuperNode ଉପରେ KCL ନିୟମ ପ୍ରଯୋଗ କରାଯାଏ।
ଏହାକୁ SuperNode କୁହାଯାଏ।

⇒ Determine the Node Voltage:-

⇒ Draw the Super Node:-

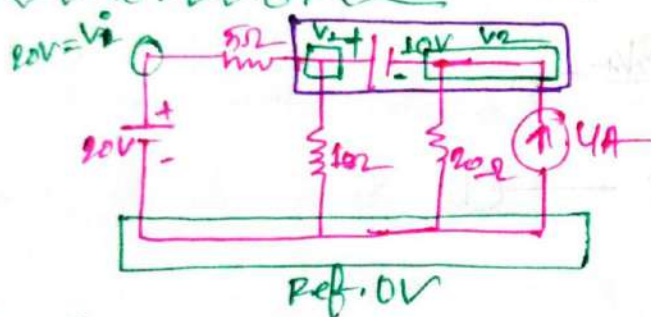

⇒ For SuperNode:-

SuperNode ଉପରେ KCL ପ୍ରଯୋଗ କରାଯାଏ।
ଏହାକୁ SuperNode କୁହାଯାଏ।
ଏହାକୁ SuperNode କୁହାଯାଏ।

$$\frac{V_1 - 0}{5} + \frac{V_2 - 0}{10} + \frac{V_3 - 0}{20} - 4 = 0$$

$$\Rightarrow \frac{4(V_1 - 20) + 2V_2 + V_3 - 80}{20} = 0$$

$$\Rightarrow 6V_1 + V_2 = 160 \quad \text{--- (1)}$$

⇒ Now! - For the eq:-

$$V_1 - V_2 = 10 \quad \text{--- (2)}$$

Solve the equation:-

$$\therefore V_1 = 24.28V$$

$$V_2 = 14.28V$$


TOPIC NAME : _____

DAY: _____

TIME: DATE: / /

DATE: / /

#prove me 3! —
mom

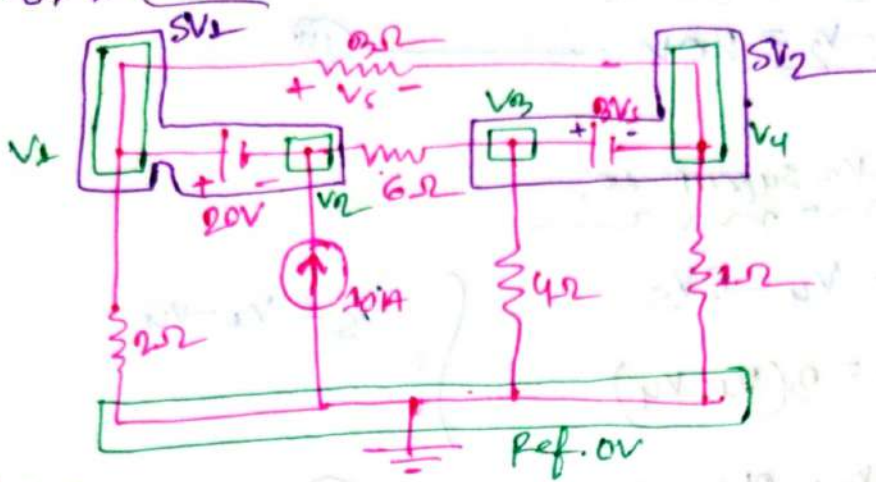

⇒ Find the Node Voltage! —

⇒ For Super Node 11—

$$\frac{v_1 - 0}{2} + \frac{v_1 - v_4}{3} + \frac{v_2 - v_3}{6} - 10 = 0$$

$$\Rightarrow \frac{3v_1 + 2(v_1 - v_4) + v_2 - v_3 - 60}{6} = 0$$

$$\Rightarrow 5V_1 + V_2 - V_3 - 2V_4 = 60 \quad \text{--- (1)}$$

For Super Node 2: —

$$\frac{V_4 - V_1}{3} + \frac{V_4 - 0}{1} + \frac{V_3 - V_2}{6} + \frac{V_3 - 0}{4} = 0$$

$$\Rightarrow \frac{2(v_4 - v_1) + 6v_4 + v_3 - v_2 + 1.5v_3}{6} = 0$$

$$\Rightarrow -2v_1 - v_2 + 2.5v_3 + 8v_4 = 0 \quad \text{--- (11)}$$

For V_1 and V_2 Supernode:—

$$V_1 - V_2 = 20V \quad \text{--- (i)}$$

For V_2 and V_3 Supernode:—

$$V_3 - V_4 = 3V_2$$

$$\therefore V_3 - V_4 = 3(V_1 - V_2)$$

$$V_5 = V_1 - V_4$$

$$3V_1 - V_3 - 2V_4 = 0 \quad \text{--- (iv)}$$

from one equation:—

$$V_1 - V_2 = 20V$$

$$\therefore V_1 = 20 + V_2$$

Put the value of V_1 in eq (iv) (i), (ii) =

$$6V_2 - V_3 - 2V_4 = -40 \quad \text{--- (v)}$$

$$-3V_2 + 2.5V_3 + 8V_4 = 40 \quad \text{--- (vi)}$$

$$3V_2 - V_3 - 2V_4 = -60 \quad \text{--- (vii)}$$

Now solve the equation:—


$$\therefore V_2 = 6.667V$$

$$V_3 = 173.333V$$

$$V_4 = -46.667$$


$$V_1 = 20 + V_2 \\ = 26.667V$$

problem:- 8.20

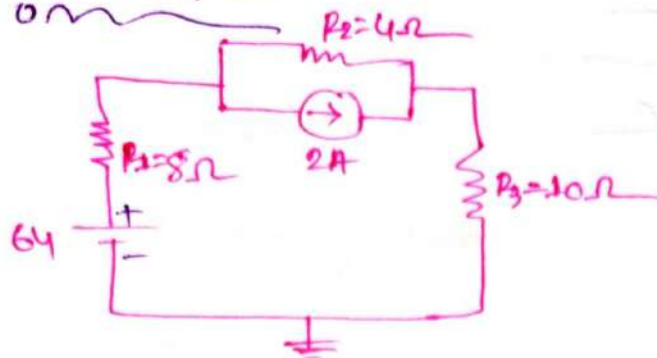

⇒ Applying Nodal analysis in the network

⇒ 1st Redraw the circuit:

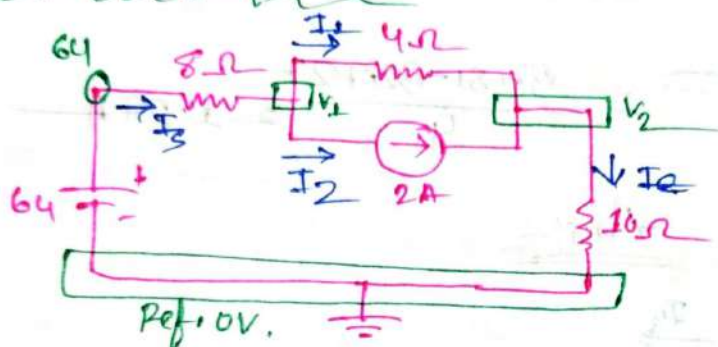

For V_1 —
now

$$\frac{V_1 - 64}{8} + \frac{V_1 - V_2}{4} + 2 = 0$$

$$\Rightarrow \frac{V_1 - 64 + 2V_1 - 2V_2 + 16}{8} = 0$$

$$\Rightarrow 3V_1 - 2V_2 = 48 \quad \text{--- (I)}$$

For V_2 —
now

$$\frac{V_2 - 0}{10} + \frac{V_2 - V_1}{4} - 2 = 0$$

$$\Rightarrow \frac{2V_2 + 5(V_2 - V_1) - 40}{20} = 0$$

$$\Rightarrow 2V_2 + 5V_2 - 5V_1 = 40$$

$$\Rightarrow -5V_1 + 7V_2 = 40 \quad \text{--- (II)}$$

Solve two equation:—

$$\therefore V_1 = 37.8181V$$

$$V_2 = 32.727V$$

For I_s :—


$$I_s = \frac{64 - 37.8181}{8} = 3.272 \text{ A} = I_e$$

For I_1 :—

$$I_1 = \frac{V_1 - V_2}{4} = \frac{37.81 - 32.727}{4} = 1.27A$$

Ans:—

#problem! 8.21

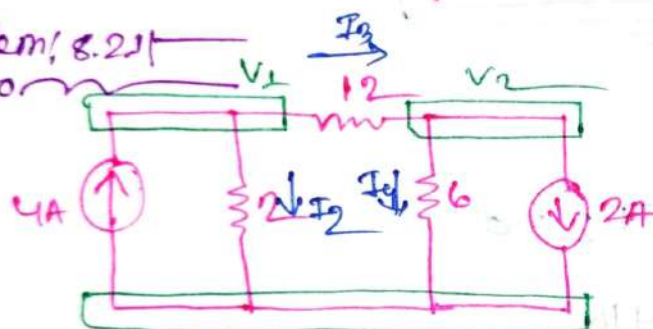

⇒ Determine the Node Voltage

⇒ For V_1 :—

$$\frac{V_1 - 0}{2} + \frac{V_1 - V_2}{12} - 4 = 0$$

$$\Rightarrow 6V_1 + V_1 - V_2 = 48$$

$$\Rightarrow 7V_1 - V_2 = 48 \quad \text{--- (1)}$$

⇒ For V_2 :—

$$\frac{V_2 - V_1}{12} + \frac{V_2}{6} + 2 = 0$$

$$V_2 - V_1 + 2V_2 = -24$$

$$-V_1 + 3V_2 = -24 \quad \text{--- (2)}$$

Solve the equation:

$$\therefore V_1 = 6V$$

$$V_2 = -6V$$


$$\therefore I_3 = \frac{V_1 - V_2}{12} = \frac{(6 - (-6))}{12} = 1A$$

$$I_2 = \frac{V_1}{2} = \frac{6}{2} = 3A$$

$$I_4 = \frac{V_2}{6} = \frac{-6}{6} = -1A$$

Ans:

problem 8.24:

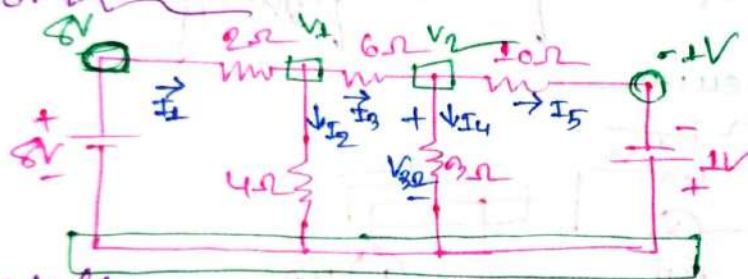

Find the voltage across the 3Ω resistor:

For V_1 :

$$\frac{V_1 - 6}{2} + \frac{V_1 - 0}{4} + \frac{V_1 - V_2}{6} = 0$$

$$\Rightarrow \frac{6V_1 - 48 + 3V_1 + 2V_1 - 2V_2}{12} = 0$$

$$\Rightarrow 11V_1 - 2V_2 = 48 \quad \text{--- (I)}$$

For V_2 :

$$\frac{V_2 - V_1}{6} + \frac{V_2 - (-1)}{10} + \frac{V_2 - 0}{3} = 0$$

$$\Rightarrow \frac{5V_2 - 5V_1 + 3V_2 + 3 + 10V_2}{30} = 0$$

$$\Rightarrow -5V_1 + 18V_2 = -3 \quad \text{--- (II)}$$


⇒ Solve the equation! —
mon

$$V_1 = 4.56V$$

$$V_2 = 1.101V$$


$$\therefore V_{0.2} = V_2 - 0 = 1.101V$$

#problem! —
mon

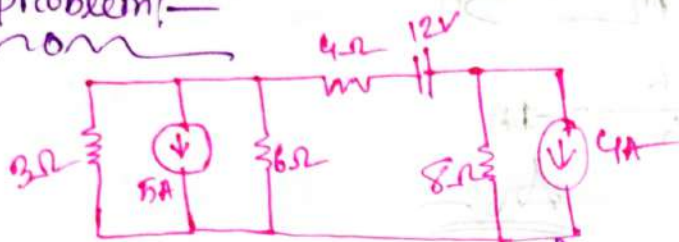

⇒ Write the nodal equations for the following circuit

⇒ Re Draw the circuit: —
mon

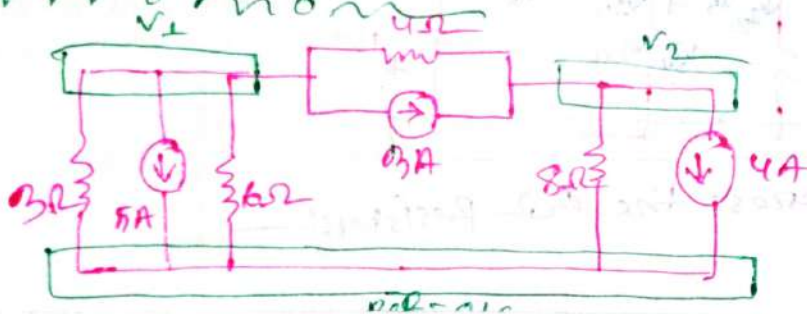

For V_1 —
mon

$$\frac{V_1}{3} + 5 + \frac{V_1}{6} + \frac{V_1 - V_2}{4} + 3 = 0$$

$$\Rightarrow \frac{4V_1 + 60 + 2V_1 + 3V_1 - 3V_2 + 36}{12} = 0$$

$$\Rightarrow 9V_1 - 3V_2 = -96 \dots \dots \dots (I)$$

For V_2 —
mon

$$\frac{V_2 - V_1}{4} + \frac{V_2}{8} + 4 - 3 = 0$$

$$\Rightarrow \frac{2V_2 - 2V_1 + 8 + V_2}{8} = 0$$

$$\Rightarrow -2V_1 + 3V_2 = -8 \dots \dots \dots (II)$$

Capacitors

No 10!

Capacitor:

⇒ A Capacitor consists of two conducting plates separated by an insulator (or dielectric)

Capacitance:

⇒ Capacitance is a measure the ability of a capacitor to store charge on its plates.

Relationship among the
Applied Voltage ($E = V$), the charge (Q) and
The Capacitance C :

⇒ Capacitance is the ratio of the charge (Q) in one plate of a capacitor to the difference Voltage between the two plates.

$$\therefore C = \frac{Q}{V}$$

C = Capacitance of capacitor (F)

Q = charge (C)

V = Voltage (V)

SI Unit $C = V^{-1}$

Common Unit Name is Farad (F)

Problem: 3:—
non

⇒ Find the Capacitance of a parallel plate capacitor if $1200 \mu\text{C}$ of charge are deposited on its plates when 10V are applied across the plates.

⇒ In given:—
non

$$Q = 1200 \mu\text{C} = 1200 \times 10^{-6} \text{C}$$

$$V = 10 \text{V}$$

we know:
non

$$C = \frac{Q}{V} = \frac{1200 \times 10^{-6}}{10} = 1.2 \times 10^{-6} \text{F} \\ = 120 \mu\text{F}$$

Ans:—

problem: 4:—
non

⇒ How much charge is deposited on the plates of a $0.15 \mu\text{F}$ Capacitor if 45V are applied across the Capacitor.

⇒ In given:—
non

$$C = 0.15 \mu\text{F}$$

$$V = 45\text{V}$$

we know:
non

$$C = \frac{Q}{V}$$

$$\therefore Q = CV = 0.15 \mu \times 45 = 6.75 \mu\text{C}$$

Ans:—

Capacitance Based on physical Dimension: —

$$C = \epsilon \times \frac{A}{d}$$

A = Surface Area of each plate

d = Distance between plate.

ϵ = permittivity

$$C = \epsilon_0 \times \epsilon_r \times \frac{A}{d}$$

$$\epsilon_0 = 8.85 \times 10^{-12}$$

ϵ_r = relative permittivity.

$$C = \epsilon_r C_0$$
$$C_0 = \epsilon_0 \frac{A}{d}$$

C_0 = Capacitance consider at air.

C = Capacitance for any other dielectric material.

Symbol of Capacitance: —

(ii)



Fixed

(i)



Variable.

Transients in Capacitive Network

We know, —

$$q = CV$$

$$\therefore i = \frac{dq}{dt} \text{ with respect to time.}$$


$$i = \frac{dq}{dt} = \frac{d(CV)}{dt} = C \frac{dV}{dt}$$

$$V = \frac{1}{C} \int_{t_0}^t i \, dt + V(t_0)$$

∴ Energy Storage by a Capacitor


$$W_C = \frac{1}{2} CV^2 \text{ [J]}$$

Charging and Discharging in a Capacitor

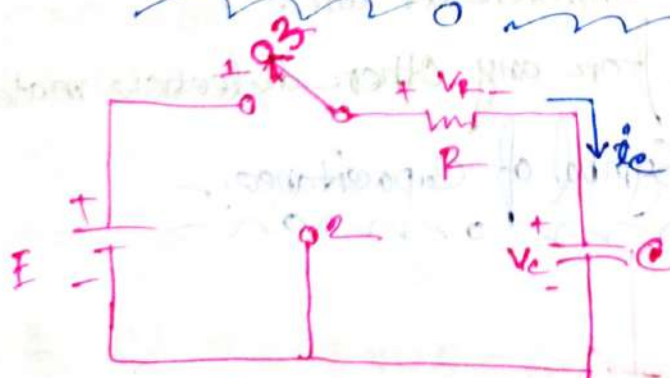

Stored Phase.

☒ Charging phase:—

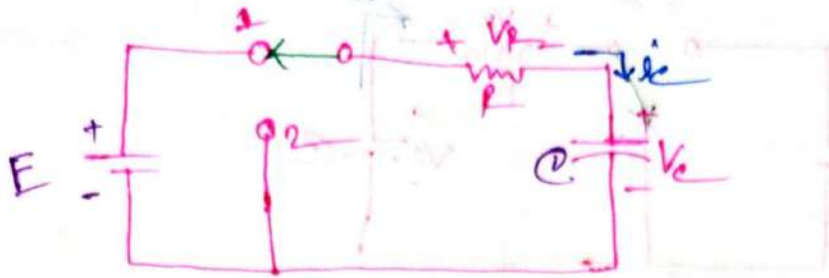

Charging phase—

Applying KVL:—

$$E = V_R + V_C$$

$$= R i_c + V_C$$

$$= RC \frac{dV_C}{dt} + V_C \quad \text{--- (1)}$$

From eq (1) =

$V_C = E(1 - e^{-\frac{t}{\tau}})$	
$i_c = \frac{E}{R} e^{-\frac{t}{\tau}}$	
$V_R = E e^{-\frac{t}{\tau}}$	
$\tau = RC$	

Unit

Volt, V

Ampere, A

Volt, V

Second, s

τ = time constant.


V_C = Voltage Across Capacitance

i_c = Current Across Capacitance

V_R = Voltage Across Resistor

$T = 5\tau$ = Total charging time.

Discharging phase:

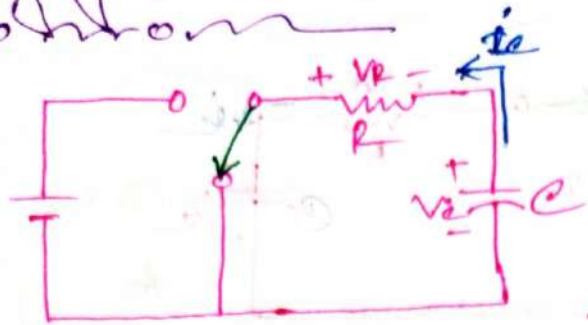

Applying KVL:

$$V_R = V_C \quad R i_C = E$$

$$\therefore E = R C \frac{dV_C}{dt} \quad \text{--- (1)}$$

From eq (1) →

$V_C = E e^{-\frac{t}{\tau}}$
$i_C = -\frac{E}{R} e^{-\frac{t}{\tau}}$
$V_R = -E e^{-\frac{t}{\tau}}$
$\tau = RC$

V_C = Voltage of Conductor / Voltage across capacitance

i_C = Current Across Capacitance

V_R = Voltage of Resistor / Voltage across


Resistance.

τ = time constant

$t = \tau = \text{Total time / Total Discharging time.}$

At the instant of switch is closed:-

$\Rightarrow$ At time $t=0$

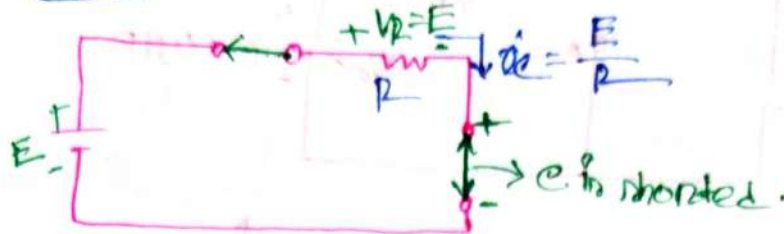


$$V_C = 0$$

$$i_C = \frac{E}{R}$$

$$V_R = E$$

Steady-State Condition:-

$\Rightarrow$ At time $t = \infty$:-

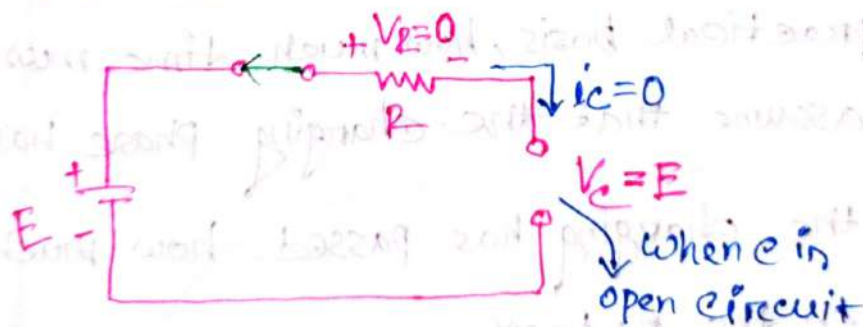


$$\therefore V_C = E$$

$$V_R = 0$$

$$i_C = 0$$

problems 10.6:—

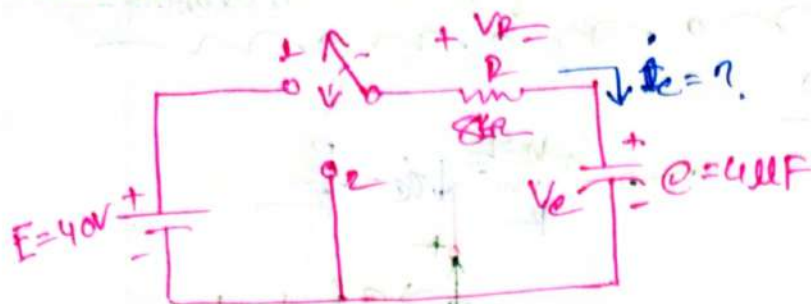

- Find the mathematical expression for the transient behaviour of V_C , i_R and V_R if switch is close at $t = 0$ s
- plot the waveform of V_C versus the time constant of the network.
- plot the waveform of i_R and V_R versus the time constant of the network.
- what is the value of V_C at time $t = 20$ ms?
- On a practical basis, how much time must pass before we can assume that the charging phase has passed.
- When the charging has passed how much charge is seating on the plates?

⇒ is given:—

$$\left. \begin{array}{l} R = 8k\Omega \\ V_C = ? \\ C = 4\mu F \end{array} \right\} E = 40V$$

we know:—

$$\tau = RC = 8k \times 4\mu = 32ms$$

we know.

(a)


For charging:

$$V_c = E(1 - e^{-\frac{t}{\tau}})$$
$$= 40(1 - e^{-\frac{t}{32\text{ms}}}) \text{ V}$$


$$i_c = \frac{E}{R} e^{-\frac{t}{\tau}}$$
$$= \frac{40}{8\text{k}} e^{-\frac{t}{32\text{ms}}}$$
$$= 5\text{mA} e^{-\frac{t}{32\text{ms}}} \text{ A}$$

$$V_R = E e^{-\frac{t}{\tau}}$$
$$= 40 e^{-\frac{t}{32\text{ms}}} \text{ V}$$


(b)

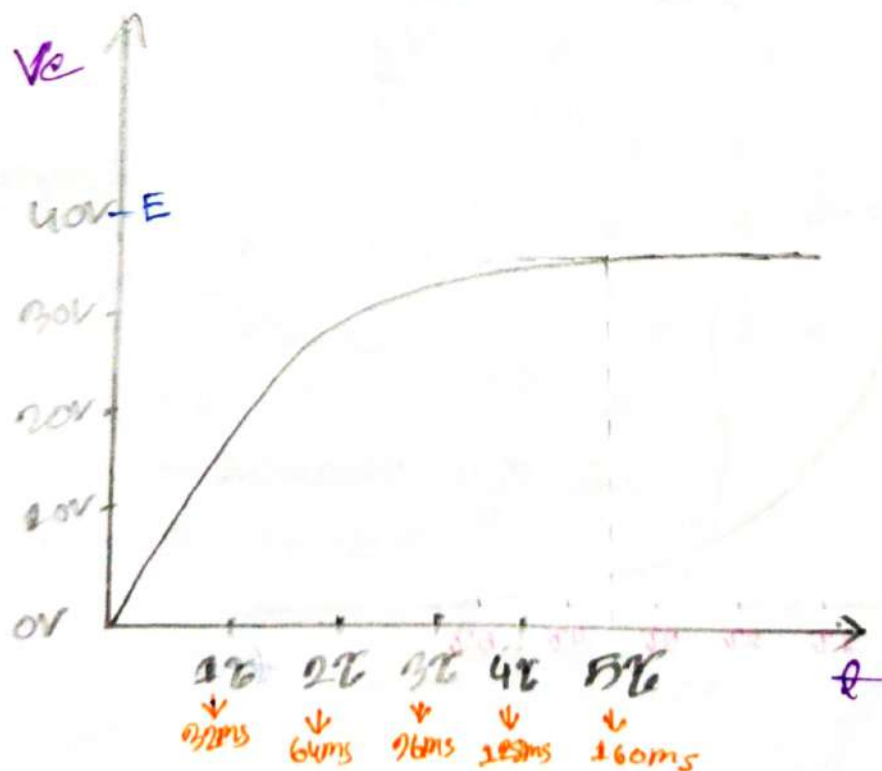

①

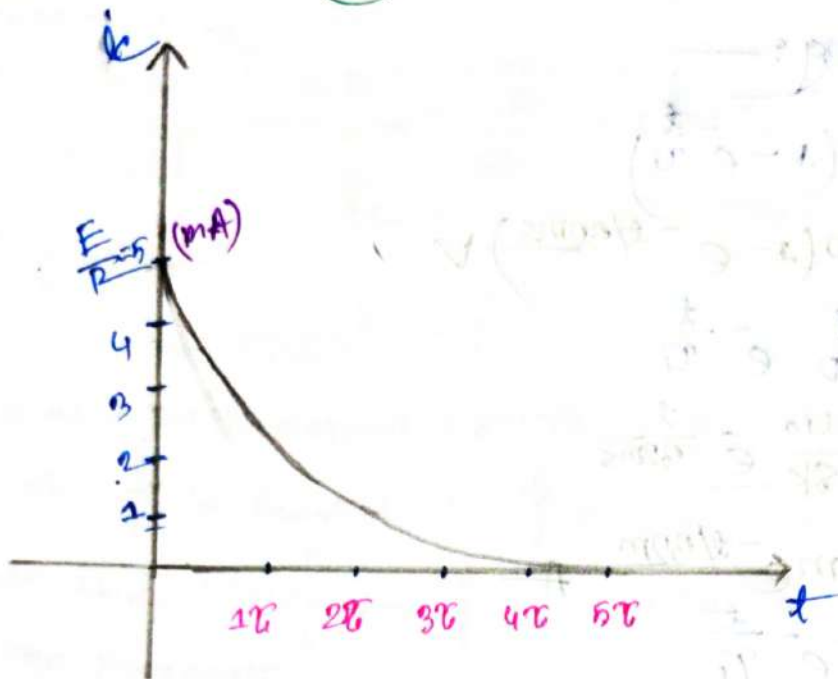

②

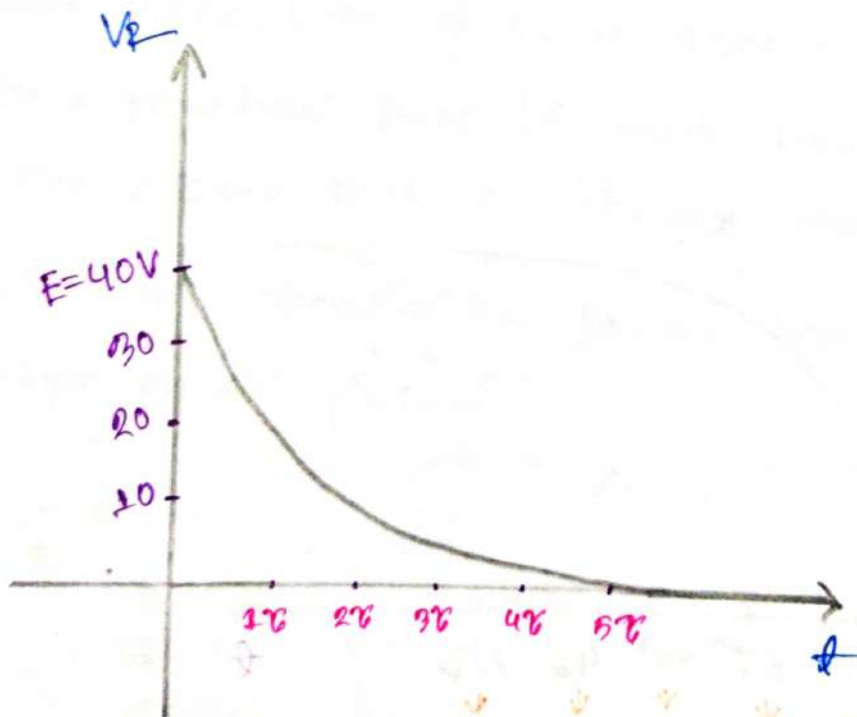

(1)

In given:-
nom

$$t = 20 \text{ ms}, E = 40 \text{ V}$$

we know:-
nom

$$V_c = E \left(1 - e^{-\frac{t}{\tau}} \right)$$

$$= 40 \left(1 - e^{-\frac{20 \text{ ms}}{32 \text{ ms}}} \right)$$

$$= 18.589 \text{ Volt}$$

$$\tau = RC$$

$$= 8 \text{ k} \times 4 \mu$$

$$= 32 \text{ ms}$$

(2)

we know:-
nom

$$\text{Total charging time } t = 5\tau$$

$$= 5 \times 32$$

$$= 160 \text{ ms}$$

$$= 0.16 \text{ s}$$

(3)

we know:-
nom

$$C = \frac{Q}{V_{\text{max}}}$$

$$\therefore Q = V_{\text{max}} \times C$$

$$= 40 \times 40$$

$$= 1600 \text{ } \mu\text{C}$$

$$I_{\text{max}} = 5\tau$$

$$V_{\text{max}} = E \left(1 - e^{-\frac{I_{\text{max}}}{\tau}} \right)$$

$$= E \left(1 - e^{-\frac{5\tau}{\tau}} \right)$$

$$= 40 (1 - e^{-5})$$


$$= 39.73$$

$$\approx 40 \text{ V}$$

Ans:-
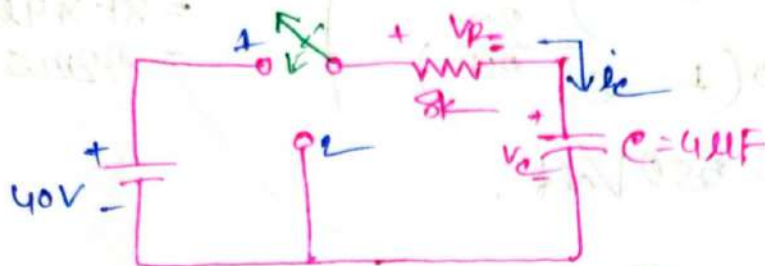
#problem 10.7!

Plot the waveforms of V_c and I_c resulting from switching between contacts 1 and 2 in the following figure every 5 time constant.



For charging:
is given:

$$E = 40V; R = 8k; C = 4\mu F$$

We know:

$$\tau = RC = 8k \times 4\mu = 32ms$$

$$\therefore V_c = E(1 - e^{-t/\tau})$$

$$= 40(1 - e^{-t/32m}) \text{ Volt}$$

$$I_c = \frac{E}{R} e^{-t/\tau}$$

$$= 40/8k \times e^{-t/32m}$$

$$= 5mA e^{-t/32m} \text{ A}$$

$$V_c = E e^{-t/\tau}$$

$$= 40 \times e^{-t/32m} \text{ Volt}$$


For Discharging:

$$V_c = E e^{-t/\tau_c} = 40 e^{-t/32\text{ms}} \text{ Volt}$$


$$i_c = -\frac{E}{R} e^{-t/\tau_c} = -5\text{mA} e^{-t/32\text{ms}} \text{ A}$$

$$V_R = -E e^{-t/\tau_c} = -40 e^{-t/32\text{ms}} \text{ Volt}$$


graph for V_c

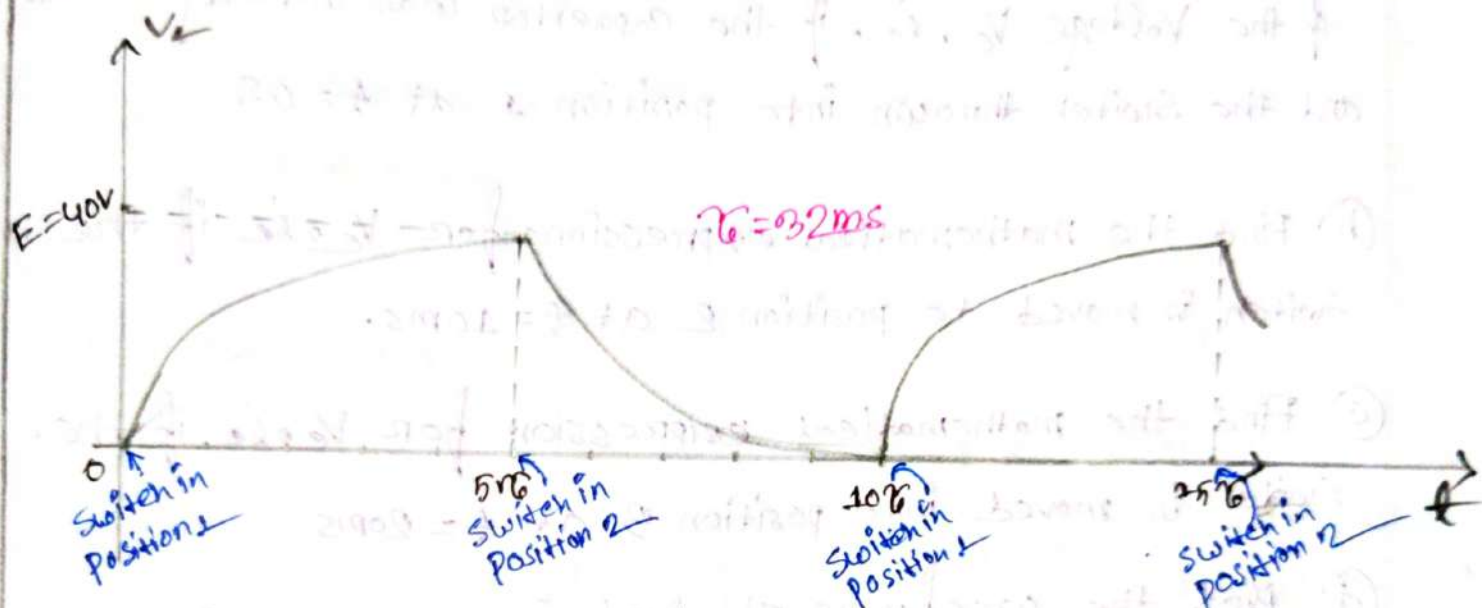

graph for i_c

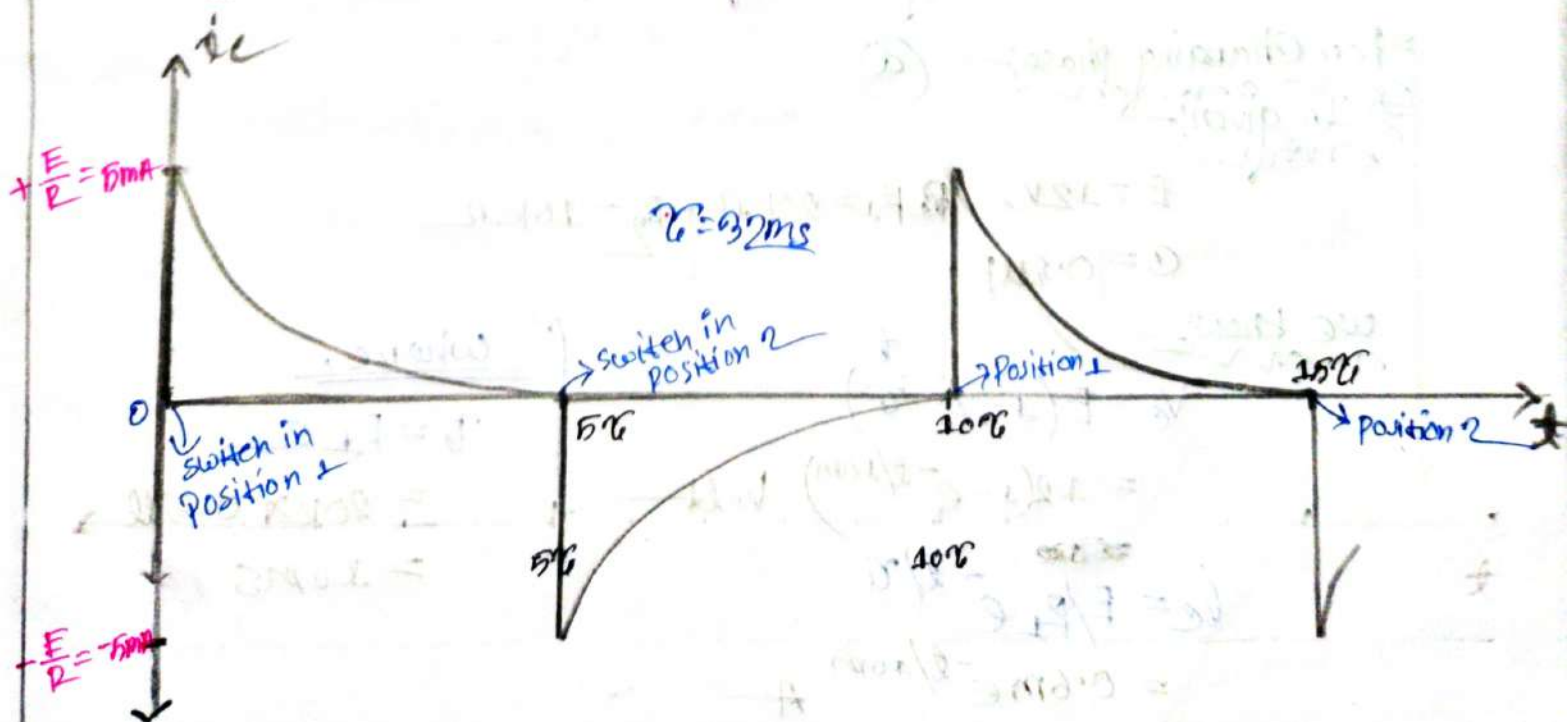

problems 10.8:-

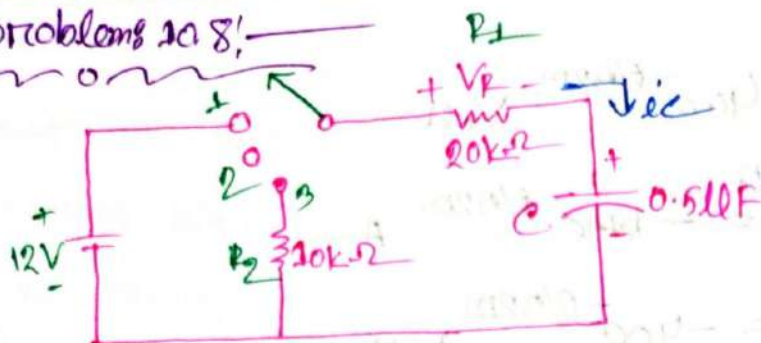

- Find the mathematical expression for the transient of the Voltage V_C , i.e., if the capacitor was initially uncharged and the switch thrown into position 1 at $t = 0$ s
- Find the mathematical expressions for V_C , i.e. if the switch is moved to position 2 at $t = 10$ ms.
- Find the mathematical expression for V_C , i.e. if the switch is moved into position 3 at $t = 20$ ms
- Plot the waveforms obtained in parts (a)-(c) on the same time axis using the defined polarities.

For charging phase:-
 In given
 work

$$E = 12V,$$

$$R_1 = 20k\Omega, R_2 = 10k\Omega$$

$$C = 0.5\mu F$$

we know:-
 work

$$V_C = E(1 - e^{-\frac{t}{\tau}})$$

$$= 12(1 - e^{-t/10\text{ms}}) \text{ Volt}$$

$$i_C = E/R_1 e^{-t/\tau}$$

$$= 0.6\text{mA} e^{-t/10\text{ms}} \text{ A}$$

where,

$$\tau = R_1 C$$

$$= 20k\Omega \times 0.5\mu F$$

$$= 10\text{ms}$$

For Storage phase:—

$$V_c = E(1 - e^{-\frac{t}{\tau}})$$

$$V_c = 40(1 - e^{-10\text{ms}/10\text{ms}})$$

$$V_c = 7.585 \text{ V.}$$

$$i_c = \frac{E}{R} e^{-\frac{t}{\tau}}$$

$$i_c = 0.6 \text{ mA} e^{-\frac{10\text{ms}}{10\text{ms}}}$$

$$i_c = 0.20 \times 10^{-4} \text{ A}$$

For Discharging phase:—

$$V_c = E e^{-\frac{t}{\tau'}}$$

$$V_c = 12 e^{-\frac{20\text{ms}}{15\text{ms}}}$$

$$V_c = 12 e^{-\frac{t}{15\text{ms}}}$$

$$i_c = -\frac{E}{R_1 + R_2} e^{-\frac{t}{\tau'}}$$

$$i_c = -0.4 \text{ mA} e^{-\frac{t}{15\text{ms}}}$$

$$\tau' = (R_1 + R_2) C$$

$$= 30 \text{ k}\Omega \times 0.5 \mu\text{F}$$

$$= 15 \text{ ms}$$

⇒ if $C = 0.05 \mu F$ then calculate all the question again.

⇒ is given:—
now

$$\begin{aligned} E &= 12V \\ C &= 0.05 \mu F \end{aligned} \quad \left. \begin{aligned} R_1 &= 20k\Omega \\ R_2 &= 10k\Omega \end{aligned} \right\}$$

(a)

For charging phase:—

$$V_c = E(1 - e^{-\frac{t}{\tau}})$$

$$\therefore V_c = 12(1 - e^{-t/1m}) \text{ V}$$

$$i_c = \frac{E}{R_1}(e^{-t/\tau})$$

$$= \frac{12}{20k} \times (e^{-t/1m})$$

$$= 0.6 \text{ mA } e^{-t/1m}$$

$$\begin{aligned} \tau &= R_1 C \\ &= 20k \times 0.05 \mu F \\ &= 1 \text{ ms} \end{aligned}$$

(b)

For Storage phase:—

The 10 ms time is equal to 10τ . that means the capacitor is fully charged. At this movement the value of V_c and i_c is fixed.

$$V_c = 12V$$

$$i_c = 0A$$

For Discharging phase:—

$$V_c = E e^{-t/\tau'}$$

$$= 12 e^{-t/1.5ms}$$

$$i_c = \frac{-E}{R_1 + R_2} e^{-t/\tau'}$$

$$= \frac{-12}{30k} e^{-t/1.5ms}$$

$$= -0.4 e^{-t/1.5ms}$$

$$\tau' = (R_1 + R_2)C$$



$$= 30k \times 0.05\mu$$

$$= 1.5ms$$


$$5\tau' = 5 \times 1.5$$

$$= 7.5ms$$

For V_c graph:—

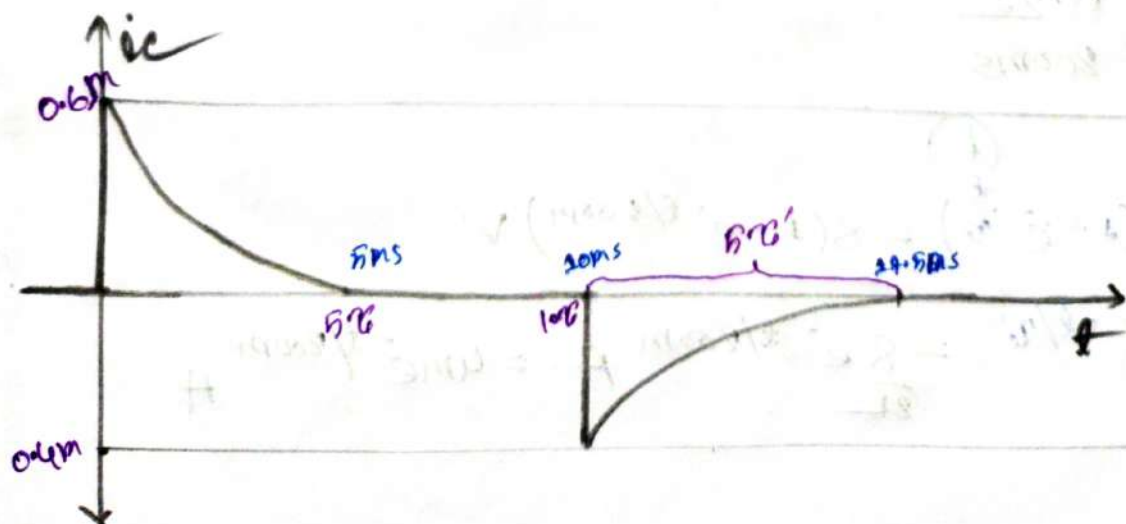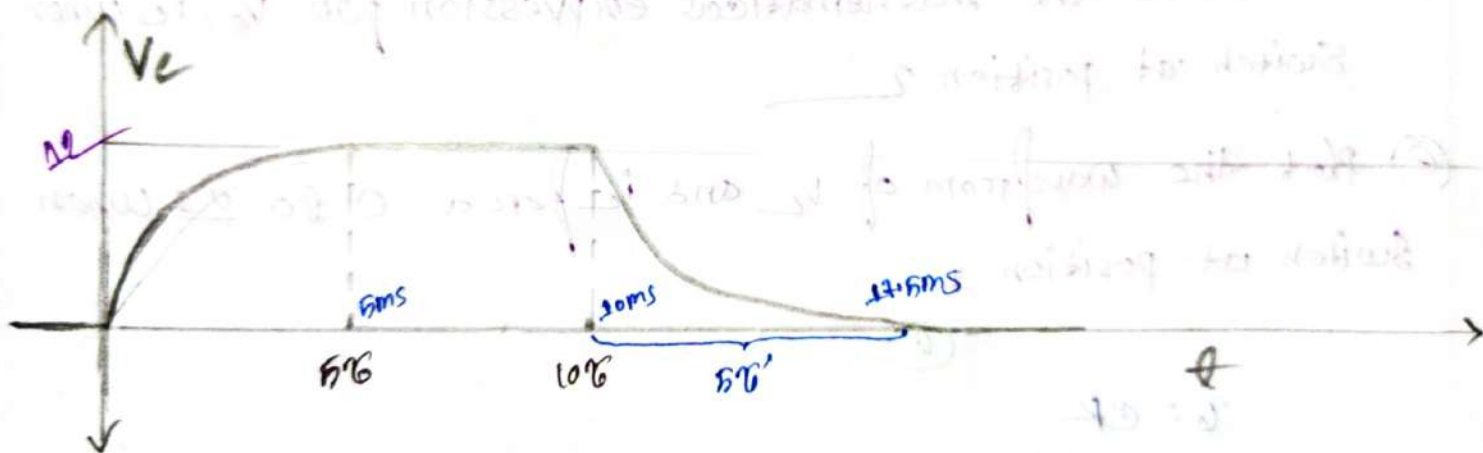

Problem: 27:—
nom

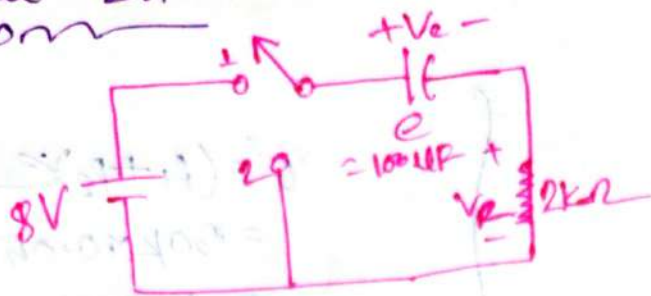

- Determine the time constant.
- Find the mathematical expression for V_c , i_c after switch at position 1.
- Determine the magnitude of V_c , i_c instant the switch is thrown into position 2 at $t = 1s$.
- Determine the mathematical expression for V_c , i_c when switch at position 2.
- Plot the waveform of V_c and i_c for a 0 to 2s when switch at position 1.

(a)

$$\begin{aligned} \tau &= CR \\ &= 100\mu F \times 2k \\ &= 0.2s \\ &= 200ms \end{aligned}$$

(b)

$$V_c = E(1 - e^{-t/\tau}) = 8(1 - e^{-t/200ms}) V$$

$$i_c = \frac{E}{R} e^{-t/\tau} = \frac{8}{2k} e^{-t/200ms} A = 4me^{-t/200ms} A$$

③

$$V_c = E(1 - e^{-t/\tau})$$


$$= 8(1 - e^{-1/0.2})$$

$$= 7.06V$$

$$i_c = \frac{E}{R} e^{-t/\tau}$$

$$= 0.004 e^{-1/0.2}$$

$$= 2.605 \times 10^{-5} A$$

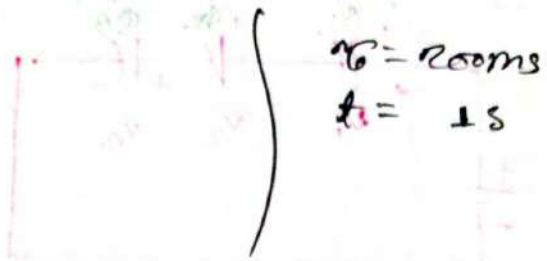

④

$$V_c = E e^{-t/\tau}$$




$$= 8 e^{-t/0.2} V$$

$$i_c = -\frac{E}{R} e^{-t/\tau}$$


$$= -\frac{8}{2k} e^{-t/0.2}$$

$$= 0.004 e^{-t/0.2}$$

$$= 4mA e^{-t/200ms} A$$

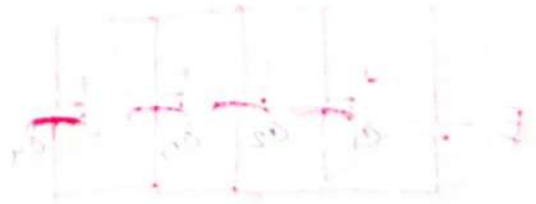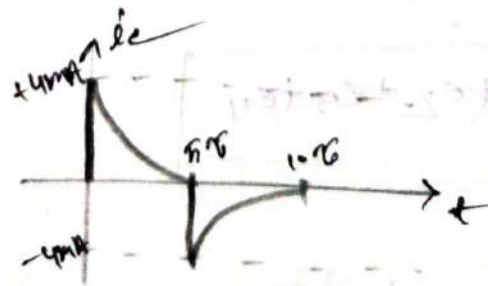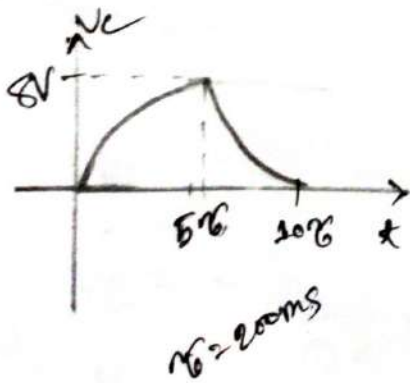


Capacitors In Series

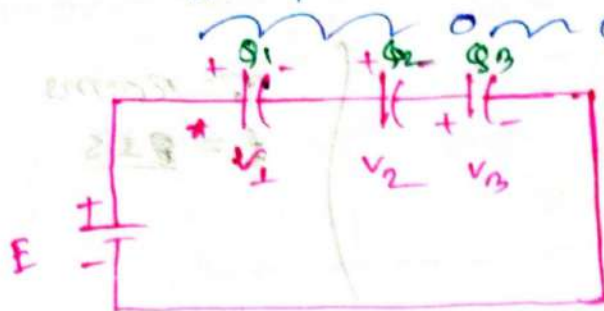


$$\frac{1}{C_T} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$

For 2 Capacitors

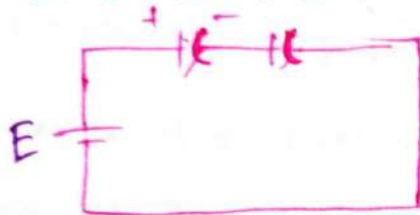


$$C_T = \frac{C_1 C_2}{C_1 + C_2}$$

Capacitors in Parallel

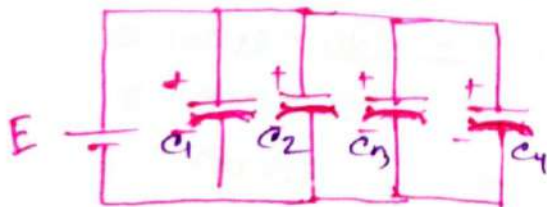

$$C_T = C_1 + C_2 + C_3 + C_4$$

#problem: 10.1A

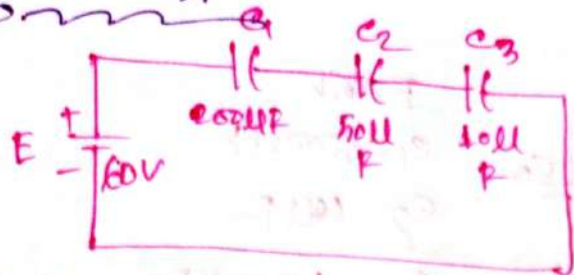

- Find the total capacitance.
- Determine the charge on each plate.
- Find the voltage across the capacitor.

we know:-

①

$$C_T = \left(\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} \right)^{-1}$$

$$= \left(\frac{1}{200\mu} + \frac{1}{50\mu} + \frac{1}{10\mu} \right)^{-1}$$

$$= 8\mu F$$

we know:-

②

$$C = \frac{Q}{V} \quad \left\{ \begin{array}{l} Q_T = Q_1 = Q_2 = Q_3 \end{array} \right.$$

$$\therefore Q_T = C_T E$$

$$= 8\mu \times 60$$

$$= 480\mu F$$


③

$$V_1 = \frac{Q_1}{C_1} = \frac{480\mu}{200\mu} = 2.4V$$

$$V_2 = \frac{Q_2}{C_2} = \frac{480}{50} = 9.6V$$

$$V_3 = \frac{Q_3}{C_3} = \frac{480}{10} = 48V$$

problem: 10.16:—
no

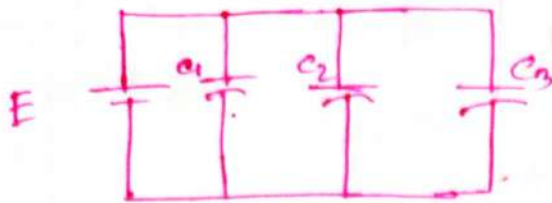

$$E = 48V$$

$$C_1 = 800\mu F$$

$$C_2 = 60\mu F$$

$$C_3 = 1200\mu F$$

- Find the total capacitance.
- Determine the charge of each plate.
- Find the total charge.

we know—
no

(a)

$$C_T = C_1 + C_2 + C_3$$

$$= 1200 + 60 + 800$$

$$= 2060\mu F$$

we know—
no

(b)

$$Q_1 = C_1 E = 800\mu F \times 48 = 38.4mC$$

$$Q_2 = C_2 E = 60\mu F \times 48 = 2.88mC$$

$$Q_3 = C_3 E = 1200\mu F \times 48 = 57.6mC$$

(c)


we know—
no

$$Q_T = Q_1 + Q_2 + Q_3$$

$$= 38.4 + 2.88 + 57.6$$

$$= 98.88mC$$

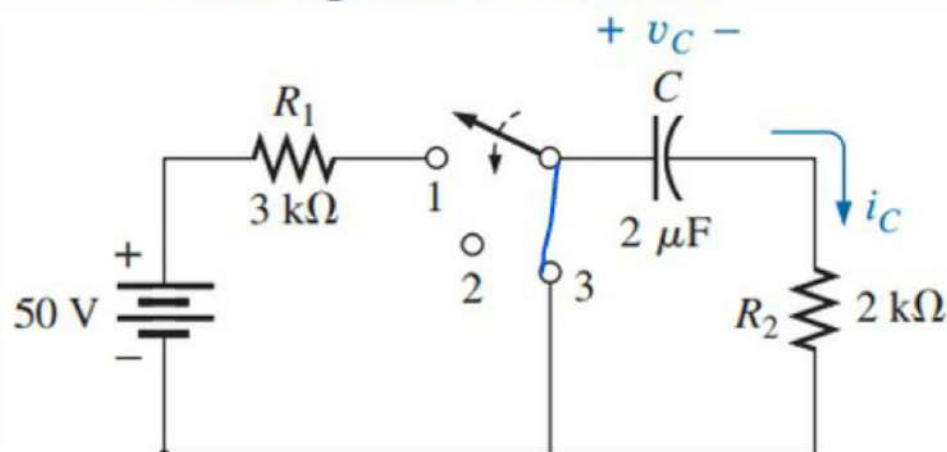28. For the network in Fig. 10.91, composed of standard values:
- Write the mathematical expressions for the voltages v_C and v_{R_1} and the current i_C after the switch is thrown into position 1.
 - Find the values of v_C , v_{R_1} , and i_C when the switch is moved to position 2 at $t = 100$ ms.
 - Write the mathematical expressions for the voltages v_C and v_{R_2} and the current i_C if the switch is moved to position 3 at $t = 200$ ms.
 - Plot the waveforms of v_C , v_{R_2} , and i_C for the time period extending from 0 to 300 ms.



Problem: 28

In given

$$\left. \begin{array}{l} E = 50V \\ R_1 = 3k\Omega \\ R_2 = 2k\Omega \end{array} \right\} \tau = 2\mu F$$

We know

$$\begin{aligned} \tau &= (R_1 + R_2)C \\ &= (3 + 2)k \times 2\mu \\ &= 10ms \end{aligned}$$

$$\begin{aligned} \therefore V_C &= E(1 - e^{-t/\tau}) \\ &= 50(1 - e^{-t/10ms}) \text{ Volt} \end{aligned}$$


$$\begin{aligned} i_C &= \frac{E}{R_1} (e^{-t/\tau}) \\ &= \frac{50}{3k} e^{-t/10ms} \\ &= 10mA e^{-t/10ms} \end{aligned}$$

$$\begin{aligned} V_{R_1} &= E(e^{-t/\tau}) \\ &= (e^{-t/10ms}) \times 30 \\ &= 30 e^{-t/10ms} \end{aligned}$$

$$\begin{aligned} V_{R_2} &= V_2(e^{-t/\tau}) \\ &= 20 e^{-t/10ms} \end{aligned}$$

$$\begin{aligned} V_1 &= IR_1 \\ &= 10mA \times 3k \\ &= 30V \end{aligned}$$
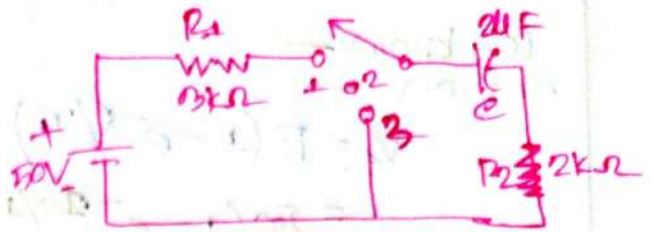
$$\begin{aligned} V_2 &= IR_2 \\ &= 10mA \times 2k \\ &= 20V \end{aligned}$$



(b)

We know —

$$V_c = E(1 - e^{-t/\tau})$$

$$= 50(1 - e^{-20/10})$$

$$= 49.099V = E$$

$$V_{R1} = 0V$$

$$i_c = 0A$$

$\tau = 10ms$
 $5\tau = 100ms$
 $t = 100ms$ that means
 The Capacitor is fully
 charged.

(c)

We know —

$$V_c = E(e^{-t/\tau'})$$

$$= 50e^{-t/4ms} V$$

$$i_c = -\frac{E}{R_2} \times e^{-t/\tau'}$$

$$= -\frac{50}{2k} \times e^{-t/4ms}$$

$$= -25mA e^{-t/4ms}$$

$$V_{R2} = -E e^{-t/\tau'}$$

$$= -50e^{-t/4ms}$$

Ans —

$$\tau' = CR_2$$

$$= 2\mu F \times 2k$$

$$= 4ms$$

#Inductor
Ch^o 11

Inductor:— ~~~~~

⇒ An inductor is a coil of conducting wire.

Inductance:— ~~~~~

⇒ Inductance is the property for which an inductor opposes the change of current flowing through it.


Types of Inductors:— ~~~~~



air-core



Ferromagnetic Core

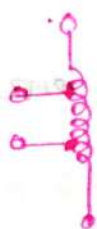

Tapped



Variable

Inductance Based on physical Dimension:— ~~~~~

$$L = \frac{\mu N^2 A}{l}$$

L = Inductance

μ = permeability

N = Number of turns

A = Area

l = length

Unit
Henries (H)
 $\text{Wb/A} \cdot \text{m}$

ℓ

m^2

m

$$L = \frac{\mu_0 \mu_r N^2 A}{l}$$

μ_r = permeability relative

$$\mu_0 = 4\pi \times 10^{-7} \text{ (wb/A.m)}$$

$$L = \mu_r L_0 \quad \text{where } L_0 = \frac{\mu_0 N^2 A}{l}$$

L_0 = inductance at air

L = inductance at any metal core

μ_r = relative permeability

problem: 11.1



① Find the inductance.

② Find the inductance if a metallic core with $\mu_r = 2000$ is inserted in the coil.

⇒ in given: —

$$l = 1 \text{ in} = 0.0254 \text{ m}$$

$$d = \frac{1}{4} \text{ in} = \frac{1}{4} \times 0.0254 = 6.35 \times 10^{-3} \text{ m}$$

$$\therefore R = \frac{d}{2} = 3.175 \times 10^{-3} \text{ m}$$

$$\therefore A = \pi R^2 = 3.1416 \times (3.175 \times 10^{-3})^2 = 3.166 \times 10^{-5} \text{ m}^2$$

$$\mu_0 = 4\pi \times 10^{-7}$$

$$N = 100$$

we know—
now

$$L_0 = \frac{\mu_0 N^2 A}{l}$$

$$= \frac{4\pi \times 10^{-7} \times (100)^2 \times 3.166 \times 10^{-5}}{0.0254}$$

$$= 1.566 \times 10^{-5} \text{ H}$$

(b)

we know—
now

$$L = \mu_r \times L_0$$


$$= 2000 \times 1.566 \times 10^{-5}$$

$$= 31.32 \times 10^{-3} \text{ H}$$

$$= 31.32 \text{ mH}$$

Ans:—

Problems: Q. 504:—

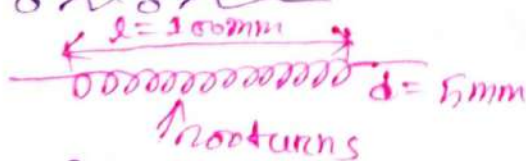

(a) Find the inductance.

⇒ In given:—
now

$$N = 200$$

$$l = 100 \times 10^{-3} \text{ m}$$

$$d = 5 \times 10^{-3} \text{ m}$$

$$\therefore r = 2.5 \times 10^{-3}$$

$$\therefore A = \pi (2.5 \times 10^{-3})^2 = 1.963 \times 10^{-5} \text{ m}^2$$

$$\left. \begin{array}{l} \mu_0 = 4\pi \times 10^{-7} \end{array} \right\}$$

We know—

$$L = \frac{\mu_0 N^2 A}{l}$$

$$= \frac{1.26 \times 10^{-6} \times (200)^2 \times 4\pi \times 10^{-7}}{100 \times 10^{-3}}$$

$$= 0.86 \times 10^{-6} \text{ H}$$

$$= 0.86 \mu\text{H}$$

problem: 3:—

$l = 1.6 \text{ in}$ $N = 200 \text{ turns}$
 $d = 0.2 \text{ in}$ $\mu_r = 500$

① Find the inductance.

⇒ In given:—

$$l = 1.6 \text{ in} = 1.6 \times 0.0254 = 0.04064 \text{ m}$$

$$d = 0.2 \text{ in} = 0.2 \times 0.0254 = 5.08 \times 10^{-3} \text{ m}$$

$$r = 2.54 \times 10^{-3} \text{ m}$$

$$\therefore A = \pi r^2 = \pi (2.54 \times 10^{-3})^2 = 2.026 \times 10^{-5} \text{ m}^2$$

$$\mu_0 = 4\pi \times 10^{-7}$$

$$\mu_r = 500$$

$$N = 200$$

We know—

$$L = \frac{\mu_r \mu_0 N^2 A}{l}$$

$$= \frac{500 \times 4\pi \times 10^{-7} \times (200)^2 \times 2.026 \times 10^{-5}}{0.04064}$$

$$= 12.52 \times 10^{-3} \text{ H}$$

$$= 12.52 \text{ mH}$$

Transients in Inductive Network

⇒ If current is allowed to pass through an inductor, it is found that the voltage across the inductor is directly proportional to the rate change of the current

$$V_L = L \frac{di_L}{dt}$$


$$i_L = \frac{1}{L} \int_0^t V_L dt + i_L(t_0)$$

∴ Energy Storage by an Inductor

$$W_L = \frac{1}{2} L i_L^2$$

R-L Transients:-

The Storage phase:-

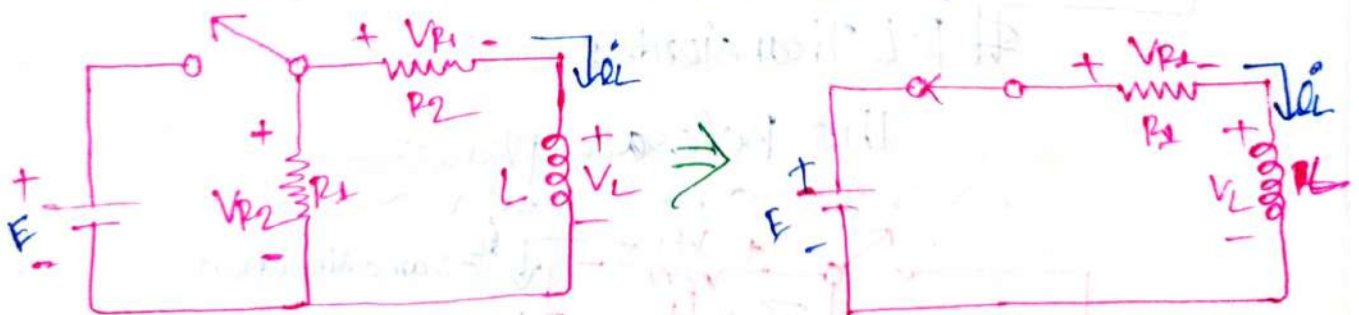

Storage phase for an inductor by closing the switch.

Charging phase: KVL for b circuit

$$E = V_{R_1} + V_L$$

$$= R_1 i_L + V_L$$

$$= R_1 i_L + L \frac{di_L}{dt}$$

$$= L \frac{di_L}{dt} + R_1 i_L \quad \text{--- (9)}$$

from eq (9)

$$V_L = E e^{-t/\tau}$$

$$i_L = \frac{E}{R_1} (1 - e^{-t/\tau})$$

$$V_{R_1} = E (1 - e^{-t/\tau})$$

$$\tau = \frac{L}{R_1} = \frac{L}{R_1}$$

$$V_{R_2} = E$$

Unit
Volt - V

Ampere - A


Volt - V

Seconds - s

Volt - V

R-L Transients:

The Release phase:

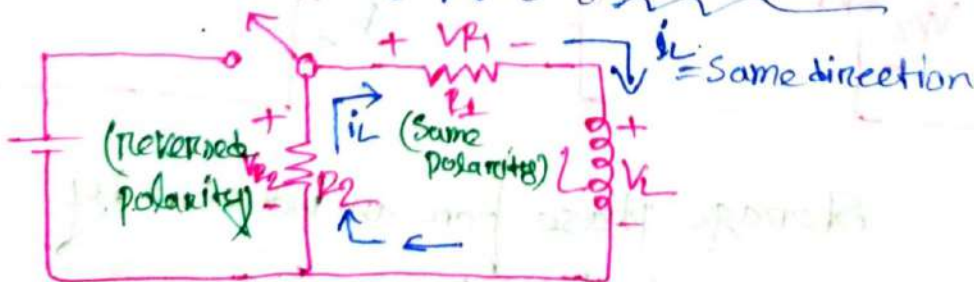

Discharging phase: using KVL

$$V_L = -i_L R_2 + i_L R_1$$

$$L \frac{di_L}{dt} + (R_1 + R_2) i_L = 0 \quad \text{--- (10)}$$

At the moment of switch is open $i_{L0} = \frac{E}{R_1}$ thus:-

$$V_i = (R_1 + R_2) i_{L0} = \left(1 + \frac{R_2}{R_1}\right) E$$

$$V_{L0} = -V_i$$

From eq (1) :-

$$V_L = -V_i e^{-t/\tau'} = \left(1 + \frac{R_2}{R_1}\right) E e^{-t/\tau'}$$

$$i_L = \frac{E}{R_1} e^{-t/\tau'}$$

$$V_{R1} = E e^{-t/\tau'}$$

$$V_{R2} = -\frac{R_2}{R_1} E e^{-t/\tau'}$$

$$\tau' = \frac{L}{R_1 + R_2}$$

After time t :-

$$i_L = I_m e^{-t/\tau'}$$

$$V_i = (R_1 + R_2) I_m$$

$$I_m = \frac{E}{R_1} (1 - e^{-t/\tau'})$$

t = After a time t

V_L = Voltage across to inductance

i_L = Current across to inductance

V_{R1} = Voltage across to Resistor R_1


V_{R2} = Voltage across to Resistor R_2

τ' = time constant

$t_{total} = 5\tau' = \text{total discharging time.}$

At the instance of switch in closed:


At time $t=0$:

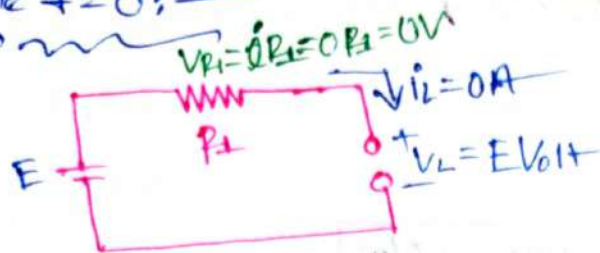

$i_L = 0A$
$V_L = E$
$V_{R_1} = 0V$

Steady-State Condition:

At time $t=\infty$:

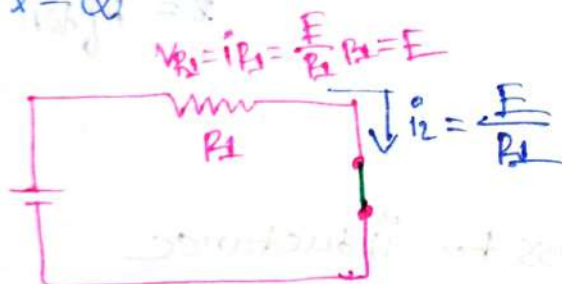


$i_L = \frac{E}{R_1}$

$V_L = 0$

$V_{R_1} = E$

problems 11.3:—

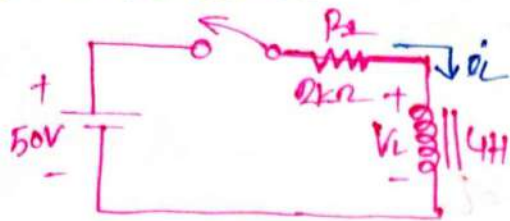

⇒ Find the mathematical expressions for i_L , V_L if the switch is closed at $t=0$ s. Sketch the resulting curves.

⇒ Inquiry:

$$E = 50V$$

$$R_1 = 2k\Omega$$

$$V_L = 8V$$

$$L = 4H$$

We know:

$$V_L = E e^{-t/\tau}$$

$$= 50 e^{-t/2m} V$$

$$i_L = \frac{E}{R_1} (1 - e^{-t/\tau})$$



$$= \frac{50}{2k} (1 - e^{-t/2m})$$

$$= 25m (1 - e^{-t/2m}) A$$


$$V_{R_1} = E (1 - e^{-t/\tau})$$

$$= 50 (1 - e^{-t/2m}) V$$
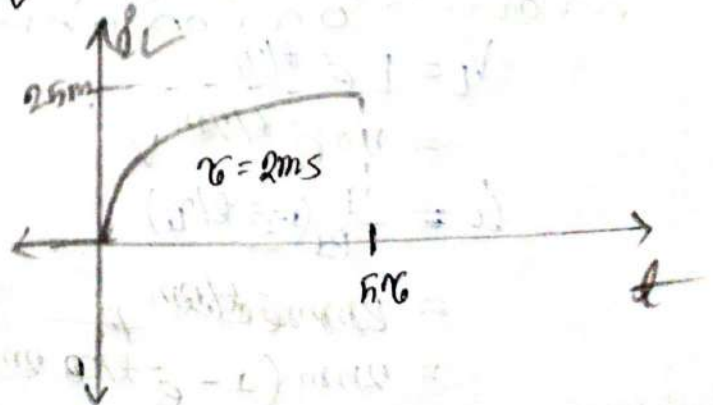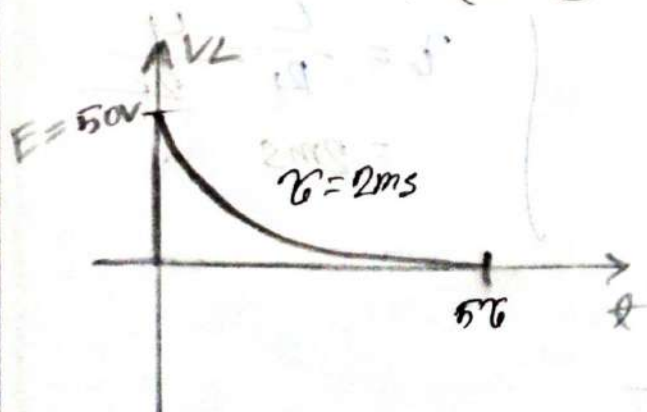
$$\tau = \frac{L}{R_1} = \frac{4H}{2k} = 2ms$$



#problem 11.5:-

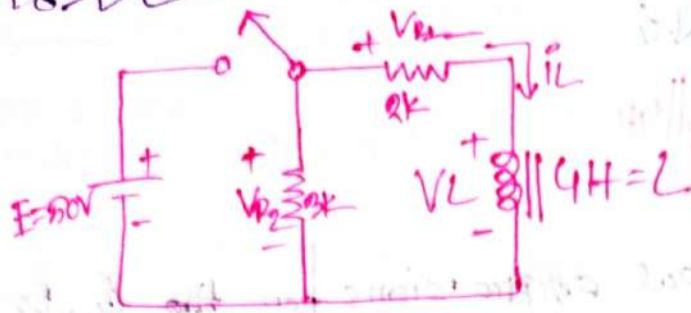

- Resistor R_2 was added to the network
- Find the mathematical Expressions for i_L , V_L , V_{R1} and V_{R2} for rise time constant of the storage phase.
 - Find the mathematical Expression for i_L , V_L , V_{R1} & V_{R2} if the switch is opened after τ constant of the storage phase.
 - Sketch the waveforms for each Voltage and current for both phases.

Given:-

$$\begin{aligned} E &= 50V \\ R_1 &= 2k \\ R_2 &= 3k \end{aligned} \quad \left\{ \begin{aligned} L &= 4H \end{aligned} \right.$$

(a)

We know:- For Storage Phase:-

$$\begin{aligned} V_L &= E e^{-t/\tau} \\ &= 50 e^{-t/2m} V \end{aligned}$$

$$i_L = \frac{E}{R_1} (1 - e^{-t/\tau})$$

$$\begin{aligned} \tau &= \frac{L}{R_1} = \frac{4}{2k} \\ &= 2ms \end{aligned}$$

$$= 25m (1 - e^{-t/2m}) A$$

$$V_{R1} = E(1 - e^{-t/\tau})$$

$$= 50(1 - e^{-t/2m}) V$$

$$V_{R2} = E$$

$$= 50V$$

(b)
we know: For discharging / Release phase:—

$$i_L = \frac{E}{R_1} e^{-t/\tau'}$$

$$= \left(\frac{50}{2} e^{-t/0.8m} \right) A$$

$$\tau' = \frac{L}{R_1 + R_2} = \frac{4}{5k}$$

$$= 0.8ms$$

$$V_L = -V_i e^{-t/\tau'}$$

$$= -\left(1 + \frac{R_2}{R_1}\right) E e^{-t/\tau'}$$

$$= -\left(1 + \frac{3k}{2k}\right) 50 e^{-t/0.8m}$$

$$= (-125 e^{-t/0.8m}) V$$

$$V_{R1} = E e^{-\frac{t}{\tau'}}$$

$$= (50 e^{-t/0.8m}) V$$


$$V_{R2} = -\frac{R_2}{R_1} E e^{-\frac{t}{\tau'}}$$

$$= -\frac{3k}{2k} \times 50 e^{-t/0.8m}$$


$$= (-75 e^{-t/0.8m}) V$$

①


⇒ For V_L :

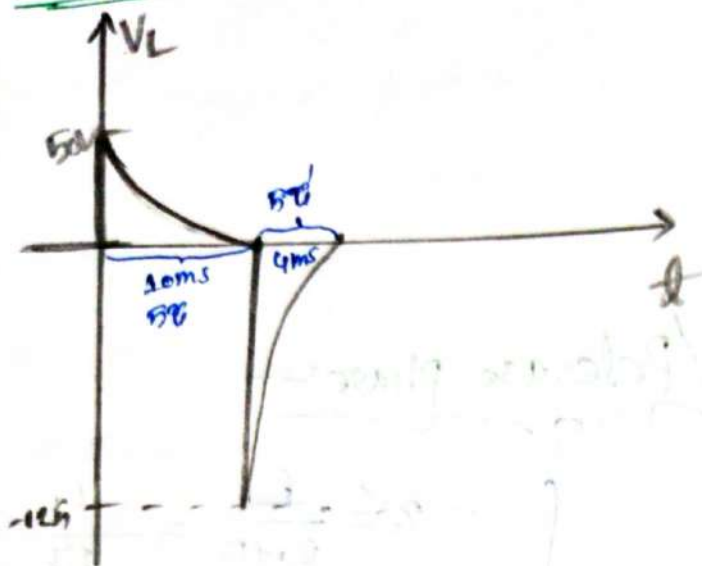


⇒ For i_L :

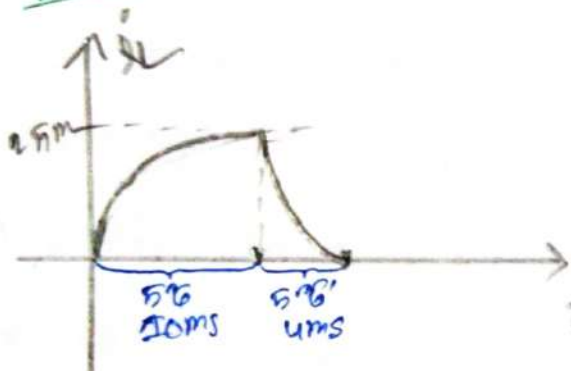


⇒ For V_{R1} :

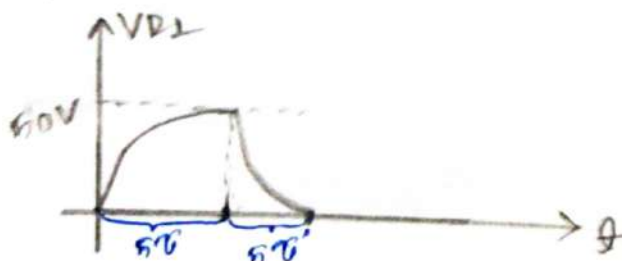

⇒ For V_{R2} :

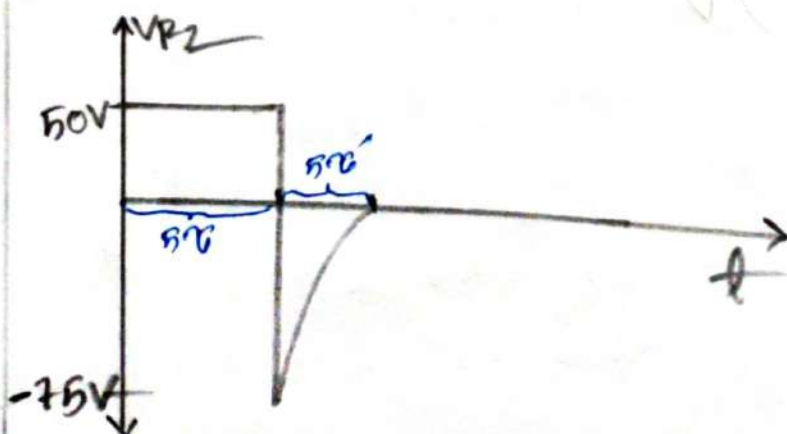

problem 12: —

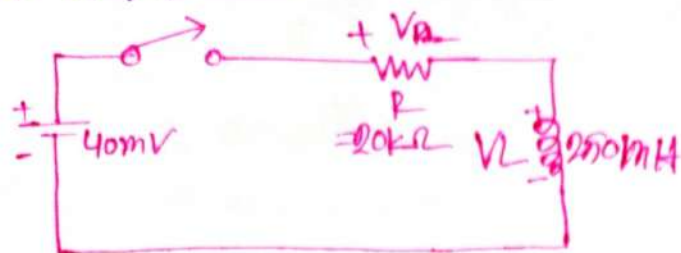

- (a) Determine the time constant
- (b) Write the mathematical Expression for the i_L After Switch is closed.
- (c) Repeat part (b) for V_L and V_R .
- (d) Determine i_L and V_L at 1, 3, and 5 time constant
- (e) Sketch the waveforms of i_L , V_L , and V_R .

⇒ In given: —

$$\begin{aligned} L &= 250 \text{ mH} \\ R &= 20 \text{ k}\Omega \end{aligned} \quad E = 40 \text{ mV}$$

(a)

We know: —

$$\tau = \frac{L}{R} = \frac{250 \text{ m}}{20 \text{ k}} = 12.5 \times 10^{-6} = 12.5 \mu\text{s}$$

(b)

$$\begin{aligned} i_L &= \frac{E}{R} (1 - e^{-t/\tau}) \\ &= \frac{40 \text{ m}}{20 \text{ k}} (1 - e^{-t/12.5 \mu}) \\ &= (2 \text{ mA} (1 - e^{-t/12.5 \mu})) \text{ A} \end{aligned}$$

(c)

$$V_L = E e^{-\frac{t}{\tau}}$$

$$= (40 \text{ mV}) e^{-\frac{t}{12.5 \mu\text{s}}}$$

$$V_{R1} = E(1 - e^{-t/\tau})$$

$$= 40 \text{ mV} (1 - e^{-t/12.5 \mu\text{s}})$$

at $t = 0^+$

$$i_L = \frac{E}{R_1} (1 - e^{-\frac{t}{\tau}})$$

$$= 2 \text{ A} (1 - e^{-\frac{t}{\tau}})$$

$$= 1.264 \text{ A}$$

$$V_L = E e^{-t/\tau}$$

$$= 40 \text{ mV} e^{-t/\tau}$$

$$= 14.715 \text{ mV}$$

At $t = 3\tau$

$$i_L = \frac{E}{R_1} (1 - e^{-t/\tau})$$

$$= 2 \text{ A} (1 - e^{-3\tau/\tau})$$

$$= 1.9 \text{ A}$$

$$V_L = E e^{-3\tau/\tau}$$

$$= 40 \text{ mV} e^{-3}$$

$$= 1.00 \text{ mV}$$

At $t = 5\tau$:

$$i_L = \frac{E}{R_1} (1 - e^{-5\tau/\tau})$$

$$= 2\mu (1 - e^{-5})$$




$$= 1.08 \times 10^{-6}$$

$$= 1.08 \mu A$$


$$V_L = E e^{-5\tau/\tau}$$

$$= 40m e^{-5}$$

$$= 260.51 \mu V$$

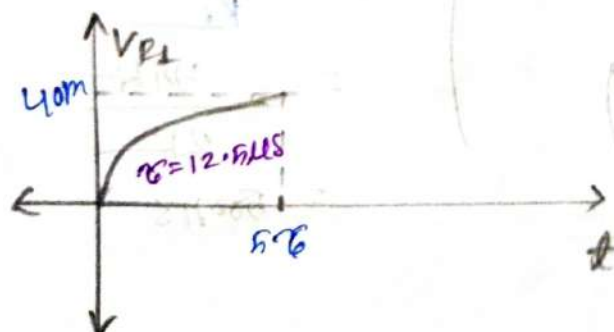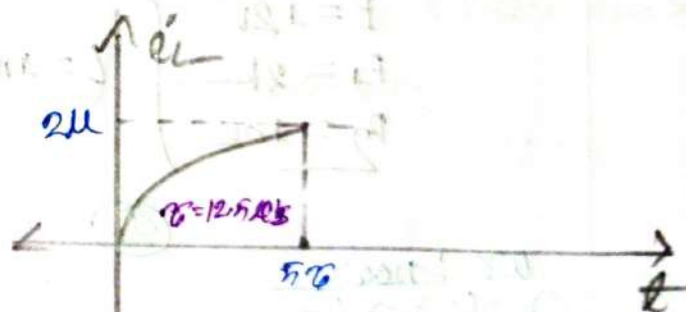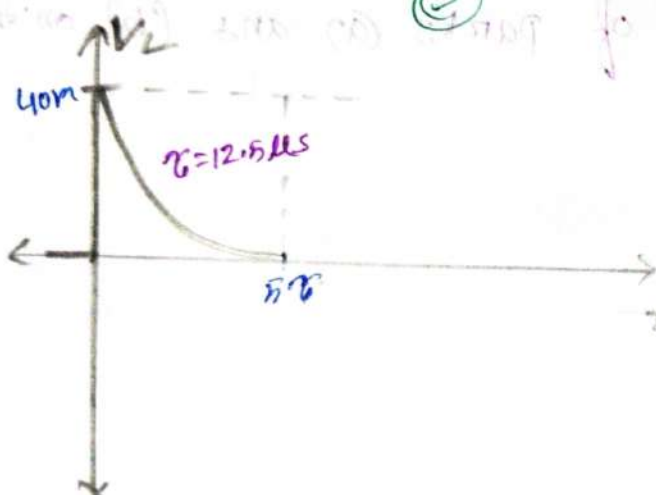

Problem 20: —

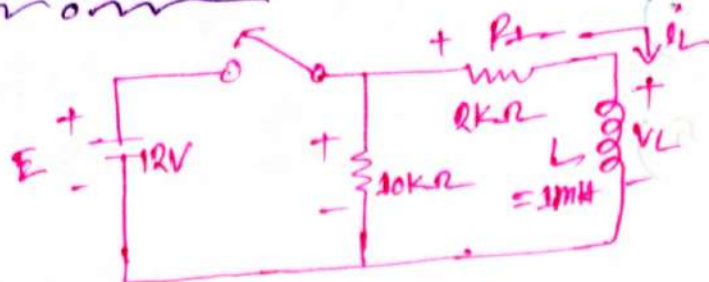

- Determine the mathematical expression for the current i_L and V_L following the closing of the switch.
- Repeat (a) part if the switch is opened at $t = 1\text{ms}$
- Sketch the waveforms of parts (a) and (b) on the same set of axes.

⇒ is given —

$$\left. \begin{array}{l} E = 12V \\ R_1 = 2k \\ R_2 = 10k \end{array} \right\} L = 3mH$$

(a)

we know —

$$\begin{aligned} i_L &= \frac{E}{R_1} (1 - e^{-t/\tau}) \\ &= \frac{12}{2k} (1 - e^{-t/500n}) \\ &= 6m (1 - e^{-t/500n}) A \end{aligned}$$

$$\begin{aligned} \tau &= \frac{L}{R_1} \\ &= \frac{3mH}{2k} \\ &= 500nS \end{aligned}$$

$$\begin{aligned} V_L &= E e^{-t/\tau} \\ &= (12 e^{-t/500n}) V \end{aligned}$$

⑥

we know:-

$$I_m = \frac{E}{R_1} (1 - e^{-t/\tau})$$

$$= 6m (1 - e^{-1\mu/500n})$$

$$= 5.187mA$$

$$\tau = 500ns$$

$$\tau' = \frac{1mH}{2k+10k}$$

$$= 83.33ns$$

Now:-

For Release & Charge Phase:-

$$i_L = I_m e^{-t/\tau'}$$

$$= 5.187mA e^{-t/83.33n}$$

Again:-

$$V_L = -V_i e^{-t/\tau'}$$


$$V_L = -62.244V e^{-t/83.33n}$$

$$V_i = (R_1 + R_2) I_m$$

$$= (10+2)k \times 5.187mA$$

$$= 62.244$$

⑦

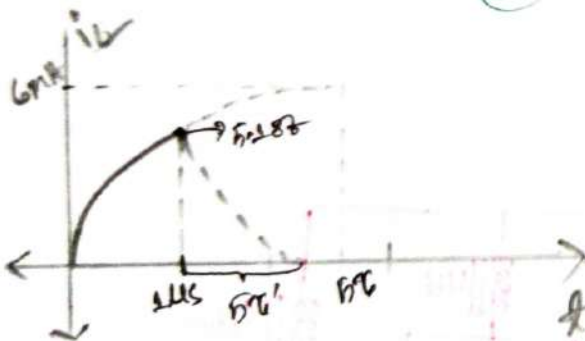

$t \uparrow V_L$

10V

-62.24V


1μs

5τ'

5τ


t

Inductors in Series

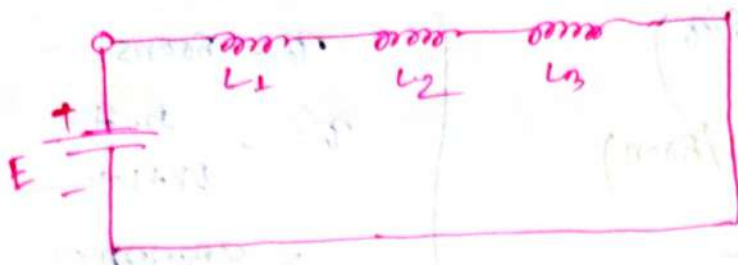



$$L_T = L_1 + L_2 + L_3$$

Inductors in parallel

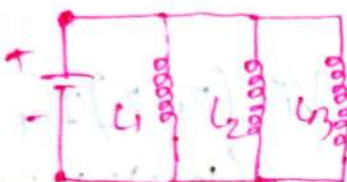

$$\frac{1}{L_T} = \frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3}$$

problem: 03h:-

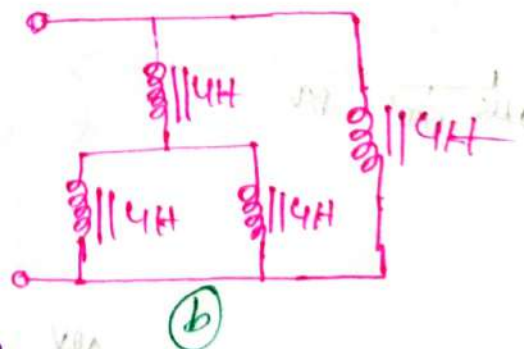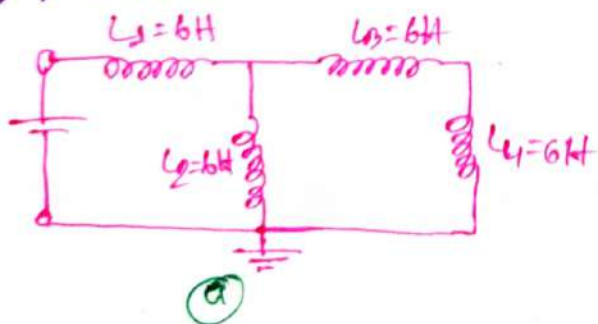

⇒ Find the total inductance?

(a)

$$L' = 6 + 6 = 12H$$

$$L'' = \left(\frac{1}{12} + \frac{1}{6} \right)^{-1} = 4H$$

$$\therefore L_T = 6H + 4H$$

$$= 10H$$

Ans:-

(b)

$$L' = \left(\frac{1}{4} + \frac{1}{4} \right)^{-1} = 2H$$

$$L'' = 2H + 4H = 6H$$

$$\therefore L_T = \left(\frac{1}{6} + \frac{1}{4} \right)^{-1} = 2.4H$$

Ans:-

Sinusoidal
Alternative
Waveforms:
Ch 10

Wave-Forms! —

⇒ A waveform is a graphized representation of a signal in the form of a wave. It shows how the amplitude (strength or intensity) of the signal varies with time.

Magnitude of Induced Voltage! —

$$e(t) = Blv \sin(\omega t) = E_m \sin(\omega t)$$

Where, $E_m = Blv$ is constant

E_m = maximum Voltage.


B = flux density

l = effective length of conductor

v = conductor velocity.

Note — The average value of AC quantity is zero.

Some Definition Related To waveforms! —

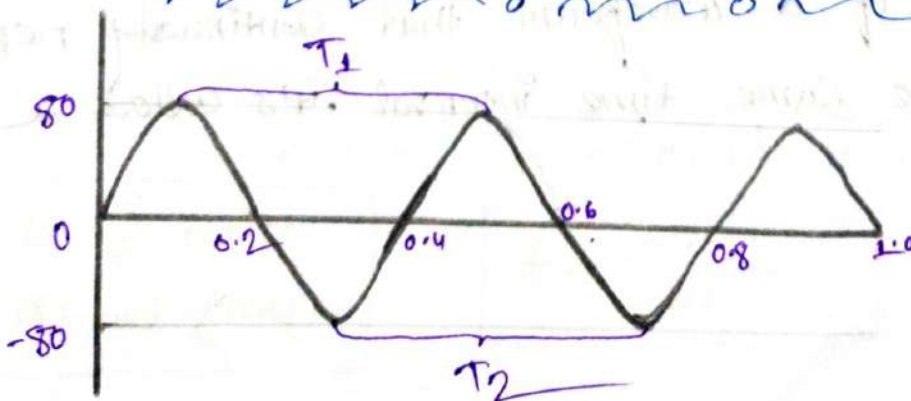

Instantaneous Value:-

⇒ The magnitude of a waveform at any instant of time is called instantaneous value.

Peak or Crest or Amplitude or Maximum Value:-

⇒ The maximum instantaneous value attained by an alternating quantity during positive and negative half-cycle is called its amplitude or peak or crest maximum value. denote by $E_m / I_m / V_m$

here, $E_m = 80 \text{ V}$

Peak-to-Peak Value:-

⇒ The full voltage between positive and negative peaks of the waveform, that is the peak-to-peak. denote by $E_{p-p}, V_{p-p}, I_{p-p}$

here, $E_{p-p} = 160 \text{ V}$

Cycle:-

⇒ The portion of a waveform that continually repeats itself after the same time interval it's called a cycle.



Periodic waveform: Time period:-

⇒ Time to complete one cycle, denote by T .

Frequency:-

⇒ Number of cycle per second, denote by f .

Relation between Frequency and Time period:-

$$f = \frac{1}{T} \text{ Hz}$$

$$T = \frac{1}{f} \text{ s}$$

Relation between Degree and Radian:-

$$\text{Radians} = \left(\frac{\pi}{180^\circ} \right) \times (\text{Degree})$$

$$\text{Degree} = \left(\frac{180^\circ}{\pi} \right) \times (\text{radians})$$

Angular Frequency or Velocity

$$\omega = \frac{\alpha}{t} \text{ rad/s}$$
$$\alpha = \omega t \text{ [rad]}$$

$$t = \frac{\alpha \text{ [rad]}}{\omega} \text{ s}$$

Relation among Angular Frequency, Frequency and Time Period:

$$\omega = \frac{2\pi}{T} \text{ rad/s} = 2\pi f \text{ rad/s}$$

$$T = \frac{2\pi}{\omega} \text{ s}$$

$$f = \frac{\omega}{2\pi} \text{ Hz}$$

Problem 19.2

⇒ Find the period of periodic waveform with a frequency of
 (a) 60 Hz. (b) 1000 Hz.

⇒ In given:-

$$f = 60 \text{ Hz}$$

We know:-

$$T = \frac{1}{f} = \frac{1}{60} = 16.67 \text{ ms}$$

(b)

In given:-

$$f = 1000 \text{ Hz}$$

We know:-

$$T = \frac{1}{f} = \frac{1}{1000} = 1 \text{ ms}$$

General Format of Mathematical Equation For the Sinusoidal Voltage or Current with 0° Initial Angle: -

Induced EMF: -

$$e(t) = E_m \sin \alpha = E_m \sin \omega t = E_m \sin 2\pi f t = E_m \sin \frac{2\pi}{T} t \quad V$$

Voltage Drop: -

$$V(t) = V_m \sin \alpha = V_m \sin \omega t = V_m \sin 2\pi f t = V_m \sin \frac{2\pi}{T} t \quad V$$


Current: -

$$i(t) = I_m \sin \alpha = I_m \sin \omega t = I_m \sin 2\pi f t = I_m \sin \frac{2\pi}{T} t \quad A$$

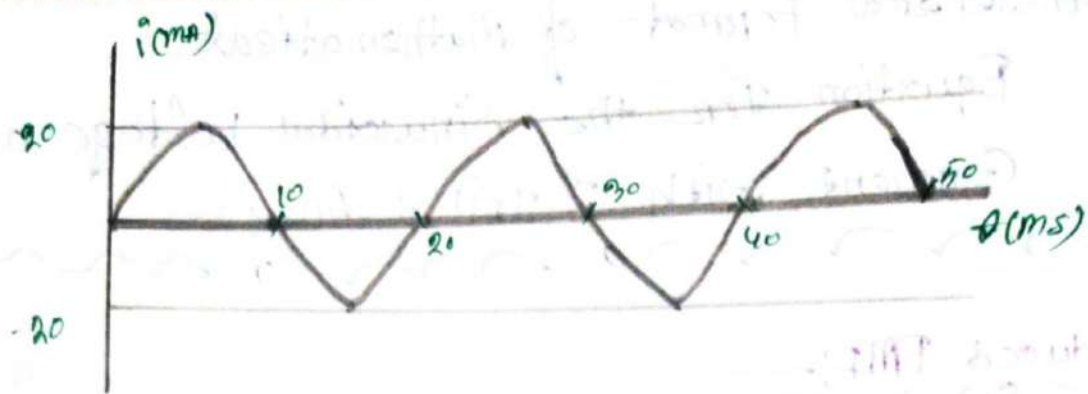problems: -

⇒ For the sinusoidal wave form

- What is the peak value?
- What is the instantaneous value of 10ms and at 20ms?
- What is the peak-to-peak value of the wave form?
- What is the period of the waveform?
- How many cycle are shown.
- What is the frequency of wave form.
- What is the value of angular frequency
- Write the instantaneous equation of the waveform.



⇒

(a)
The peak value $I_m = 20 \text{ mA}$

(b)

In given:-
now

$$\begin{aligned} I_m &= 20 \text{ mA} \\ T &= 10 \text{ ms} \\ f_1 &= 15 \text{ ms} \\ f_2 &= 20 \text{ ms} \end{aligned}$$

$$f = \frac{1}{T} = \frac{1}{20 \text{ ms}} = \frac{100 \text{ Hz}}{2}$$

$$\begin{aligned} \omega &= 2\pi f = 2\pi \times \frac{100 \text{ Hz}}{2} \\ &= \frac{200\pi}{2} \\ &= 100\pi \end{aligned}$$

We know:-
now

For t_1 :-
now

$$\begin{aligned} i_1(t) &= I_m \sin \omega t_1 \\ &= 20 \times \sin \left(100\pi \times \frac{180}{\pi} \times \frac{1}{2} \times 10^{-3} \right) \\ &= -20 \text{ mA} \end{aligned}$$

For t_2 :-
now

$$\begin{aligned} i_2(t) &= I_m \sin \omega t_2 \\ &= 20 \times \sin \left(100\pi \times \frac{180}{\pi} \times \frac{1}{2} \times 20 \times 10^{-3} \right) \\ &= 0 \text{ mA} \end{aligned}$$

(c)

The peak to peak value is $I_{p-p} = 20 - (-20)$
 $= 40 \text{ mA}$

(d)

The period of waveform $T = 20 \text{ ms}$

(e)

There are 2.5 cycles.

(f)

We know—

$$f = \frac{1}{T} = \frac{1}{20 \text{ ms}} = 50 \text{ Hz}$$

$$\therefore T = \frac{1}{f} = \frac{1}{50} = 20 \text{ ms}$$

(g)

We know—

$$\omega = 2\pi f = 2\pi \times 50 = 100\pi = 314.16 \text{ rad/s}$$

(h)

$\therefore$ The instantaneous—


$$i(t) = 20 \sin 314.16 t$$

General Formate of Mathematical Equations
for the Sinusoidal Voltage/Current with
Phase Angle:—

Induced EMF:—


When θ_e is positive:—
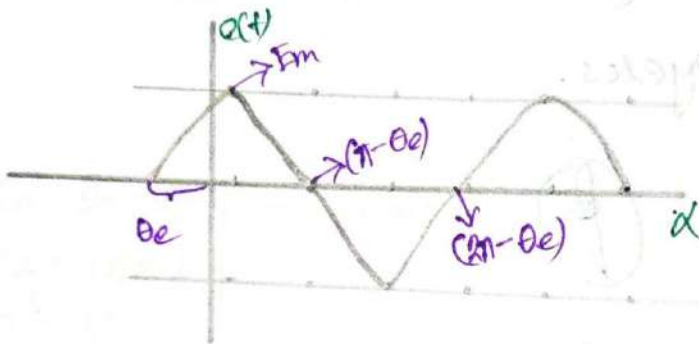
$$e(t) = E_m \sin(\alpha + \theta_e) = E_m \sin(\omega t + \theta_e) \quad V$$



When θ_e is negative:—
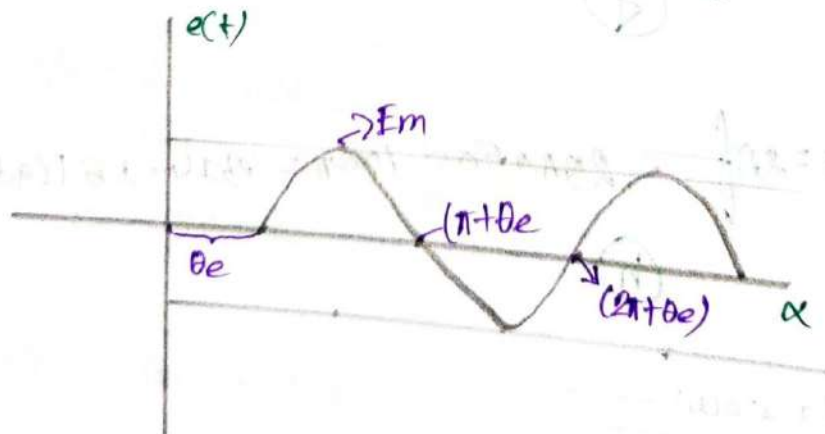
$$e(t) = E_m \sin(\alpha - \theta_e) = E_m \sin(\omega t - \theta_e) \quad V$$



Note:—

The

Other two are the same.

Initial Angle:-

$$\boxed{\text{Initial Angle} = -\text{Phase Angle}}$$

denote by θ_{eo}

$$\boxed{\theta_{eo} = -\theta_e}$$

Convention of $\sin \theta$:-

$\Rightarrow$ To identify the phase angle from an equation at first $+\cos$, $-\cos$ and $-\sin$ convert to $+\sin$.

$$\begin{aligned}\cos \alpha &= \sin(\alpha + 90^\circ) \\ -\cos \alpha &= \sin(\alpha - 90^\circ) \\ -\sin \alpha &= \sin(\alpha \pm 180^\circ)\end{aligned}$$

Problem 1:-

Identify the peak to peak value, angular frequency and phase angle and find the initial angle for the waveform.

$$e(t) = -160 \cos(400t - 20^\circ) \text{ V}$$

$\Rightarrow$ 1st convert the waveform into $\sin$:-

$$\begin{aligned}e(t) &= 160 \sin(400t - 20^\circ - 90^\circ) \\ &= 160 \sin(400t - 110^\circ)\end{aligned}$$

$$\therefore E_{p-p} = 2E_m = 160 \times 2 = 320 \text{ V}$$

$$\omega = 400 \text{ rad/s}$$

$$\text{Phase Angle } \theta_e = -110^\circ$$

$$\text{Initial } \theta_{eo} = -\theta_e = -(-110) = 110^\circ$$

phase Difference and phase Relation Between Two waveforms:—

Conditions:—

- ① The must be same type waveforms.
- ② Their frequency or angular frequency or time period must be same.

$$\text{Angle Difference} = \text{Voltage angle} - \text{Current Angle.}$$

$$\text{Phase Difference} = |\text{Angle Difference}|$$

Case 1:—

⇒ If Angle Difference = Voltage Angle - Current Angle = 0°

Phase Relation: $V(t)$ and $i(t)$ are in phase.

The starting points of $v(t)$ and $i(t)$ are same.

Case 2:—

⇒ Angle Difference $> 0^\circ$

Phase relation: $V(t)$ leads $i(t)$ or $i(t)$ lags $V(t)$

Case 3:—

Angle Difference $< 0^\circ$

phase relation: $V(t)$ lags $i(t)$ or $i(t)$ leads $V(t)$

problems 10.12

⇒ What is

- ① the phase difference.
- ② the phase relationship between the sinusoidal waveforms of the following sets?

$$i(t) = -15 \cos(\omega t + 150^\circ) \text{ A}$$

$$v(t) = 10 \sin(\omega t - 20^\circ) \text{ V}$$

⇒ 1st convert $i(t)$:—

$$i(t) = 15 \sin(\omega t + 150 - 90^\circ)$$

$$= 15 \sin(\omega t + 60^\circ) \text{ A}$$

In given—

$$v(t) = 10 \sin(\omega t - 20^\circ) \text{ V}$$

We know—

$$\begin{aligned} \text{Angle Diff} &= \text{Voltage Angle} - \text{Current Angle} \\ &= -20^\circ - 60^\circ \end{aligned}$$

$$\begin{aligned} \text{Phase Diff} &= -80^\circ \\ &= |\text{Angle Diff}| \\ &= |-80^\circ| \\ &= 80^\circ \end{aligned}$$

②

Angle Diff $< 0^\circ$

So,

$v(t)$ lags $i(t)$ by 80° or
 $i(t)$ leads $v(t)$ by 80°

Ans:-